



Chapter 9

- Sinusoidal Steady-State Analysis



Outline

- Equivalent impedance
 - Series impedance
 - Parallel impedance
- General AC phasor analysis
- AC Power

Impedance and Admittance

Resistor	$\mathbf{Z} = R$	$\mathbf{Y} = 1 / R$
Inductor	$\mathbf{Z} = j \omega L$	$\mathbf{Y} = 1 / j \omega L$
Capacitor	$\mathbf{Z} = 1 / j \omega C$	$\mathbf{Y} = j \omega C$

Impedance is
voltage/current

$$\mathbf{Z} = R + jX$$

R = resistance = $\text{Re}(\mathbf{Z})$

X = reactance = $\text{Im}(\mathbf{Z})$

阻抗 (电阻+电抗)

Admittance is
current/voltage

$$\mathbf{Y} = \frac{1}{\mathbf{Z}} = G + jB$$

G = conductance = $\text{Re}(\mathbf{Y})$

B = susceptance = $\text{Im}(\mathbf{Y})$


导纳 (电导+电纳)



Equivalent Impedance

- The phasors also follow the KCL and KVL
- The phasors of I and V of $R/L/C$ follow the same relationship as resistors in the time domain.
- The impedance can be combined in the same way as resistors to obtain equivalent impedance
- The voltage distribution rule for the series RLC connections still hold.
- The current distribution rule for the parallel RLC connections still hold.

Equivalent Series Impedance

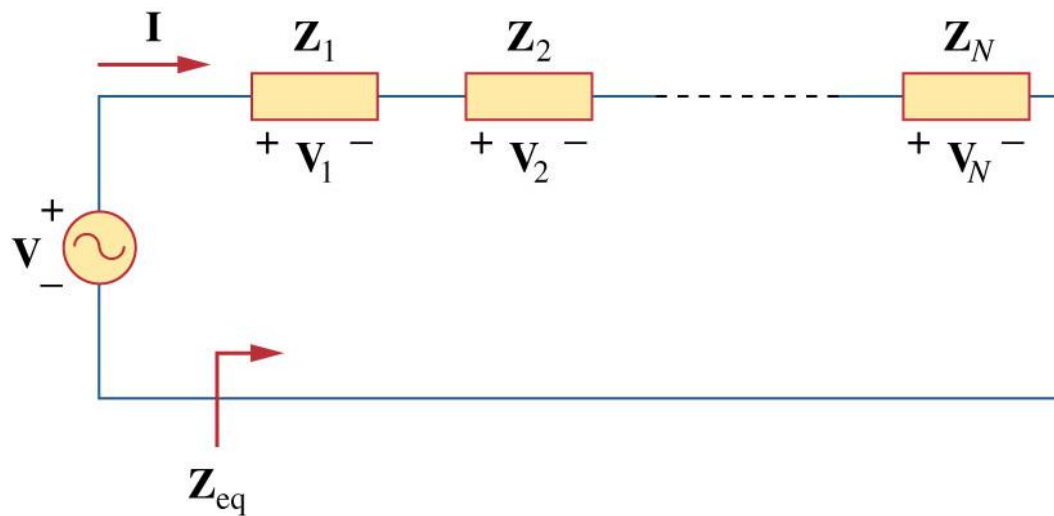

$$Z_{eq} = Z_1 + Z_2 + Z_3 + \cdots + Z_N$$

$$V_i = \frac{Z_i}{Z_{eq}} V$$

Impedance combination for RLC Circuit



(a) RL




(b) RC



(c) LC

Impedance combination for RLC Circuit

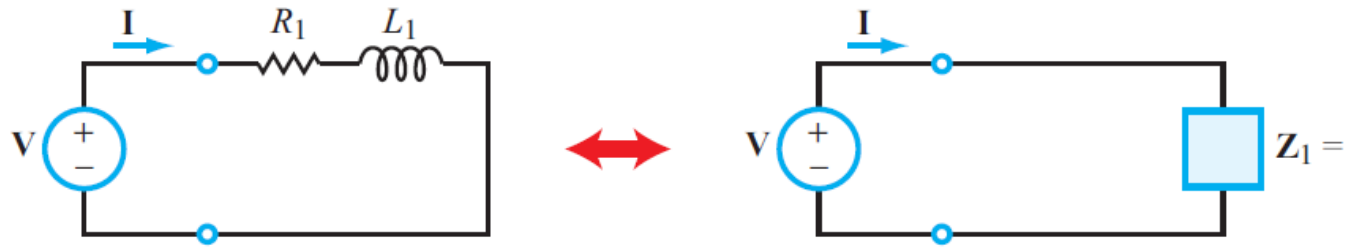

(a) RL



(b) RC




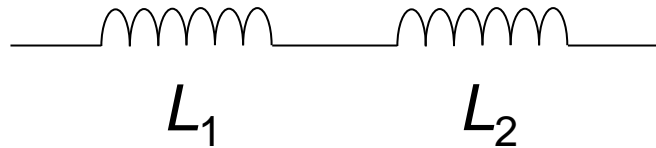(c) LC




Series L and Series C

Find the total impedance of the following circuits.
What are the equivalent inductance and capacitance?



$$\mathbf{Z}_{eq} = j\omega(L_1 + L_2) = j\omega L_{eq}$$

$$L_{eq} = (L_1 + L_2)$$

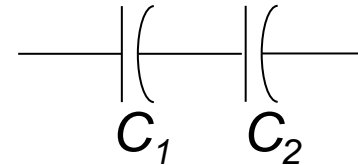


$$\mathbf{Z}_{eq} = \frac{1}{j\omega C_1} + \frac{1}{j\omega C_2} = \frac{1}{j\omega C_{eq}}$$

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

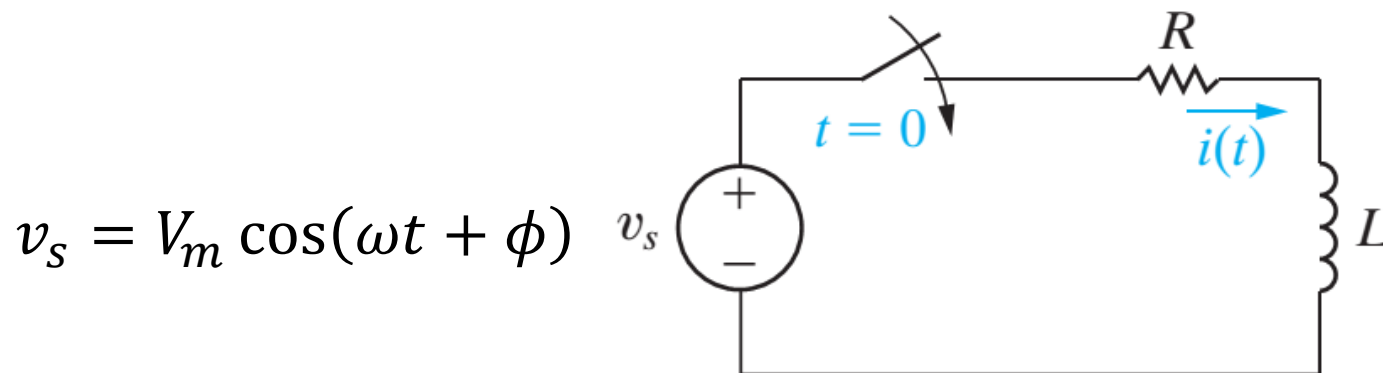Exercise I

Find the current in the following circuit using phasor analysis.






Solution Using Phasor

$$I = \frac{V_m e^{j\phi}}{R + j\omega L} = \frac{V_m e^{j\phi}}{\sqrt{R^2 + (\omega L)^2} e^{j\theta}} = \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} e^{j(\phi - \theta)}, \text{ where } \theta = \text{atan}\left(\frac{L\omega}{R}\right).$$

Therefore, the steady state solution is

$$i = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi - \theta)$$

Solution from time domain analysis

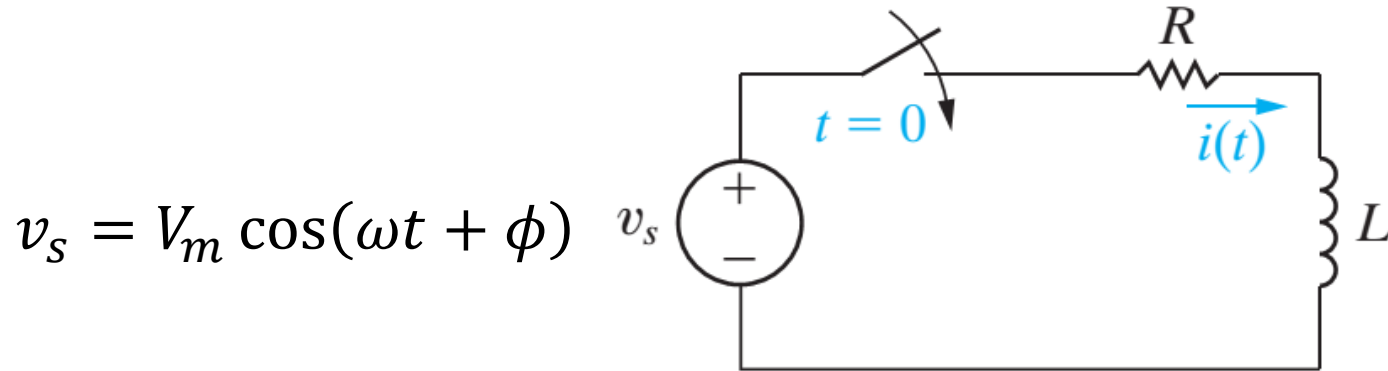

$$i = \left[\frac{-V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\phi - \theta) e^{-(R/L)t} \right] + \left[\frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi - \theta) \right]$$


Transient response

Steady-state response

$$\theta = \text{atan}\left(\frac{L\omega}{R}\right)$$

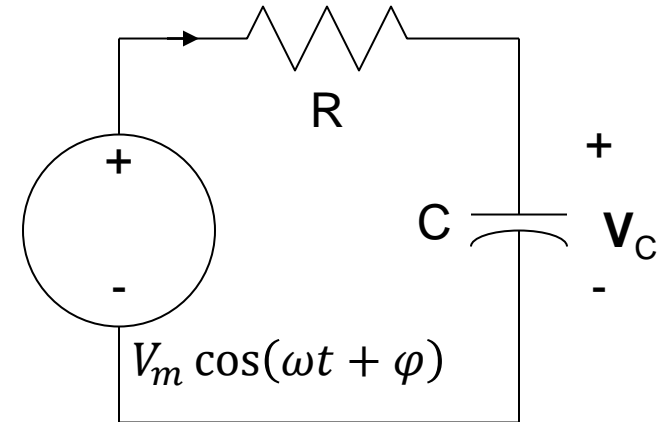Exercise II

Find V_C in the following circuit using phasor analysis.



Solution: In phasor domain,


$$\begin{aligned} V_C &= V_m e^{i\varphi} \frac{\frac{1}{i\omega C}}{R + \frac{1}{i\omega C}} = V_m e^{i\varphi} \frac{1}{i\omega RC + 1} = \frac{V_m e^{i\varphi}}{\sqrt{1 + (\omega RC)^2} e^{i\theta}} \\ &= \frac{V_m}{\sqrt{1 + (\omega RC)^2}} e^{i(\varphi - \theta)}, \text{ where } \theta = \text{atan}(\omega RC) \end{aligned}$$

Transforming V_C back to the time domain, we have

$$V_C(t) = \frac{V_m}{\sqrt{1 + (\omega RC)^2}} \cos(\omega t + \varphi - \theta)$$

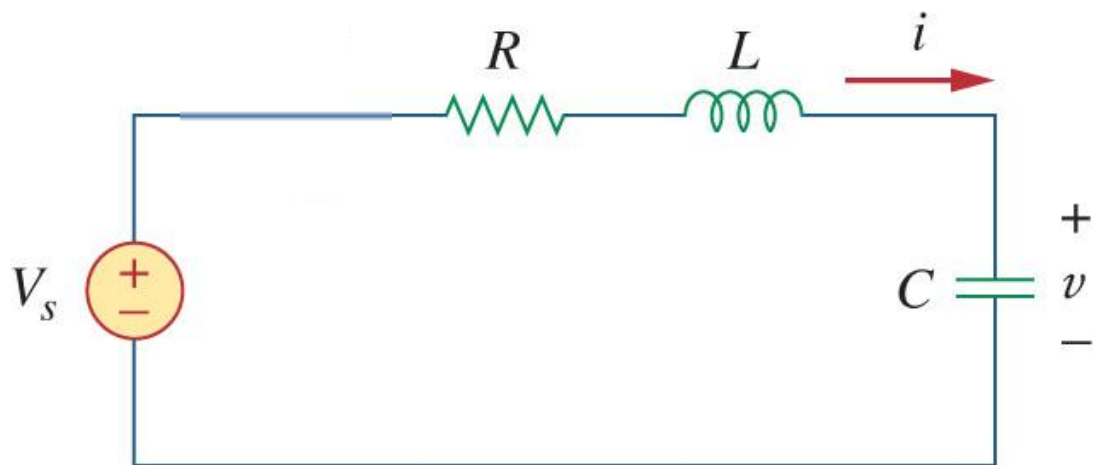Exercise III

- Using the phasor approach, determine the voltage $v(t)$ in the series RLC circuit.



Solution: Using the voltage divider formula,

$$v_p = \frac{\frac{1}{j\omega C}}{R + jL\omega + \frac{1}{j\omega C}} V_{s,p} = \frac{V_{s,p}}{1 + jRC\omega - LC\omega^2}.$$



Solution from the second order equation


$$\frac{d^2 v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{v}{LC} = \frac{V_s}{LC}$$

$$\left(-\omega^2 + \frac{R}{L} j\omega + \frac{1}{LC} \right) v_p = \frac{V_{s,p}}{LC}$$

$v_p = \frac{V_{s,p}}{1 + jRC\omega - LC\omega^2}$, same as the result obtained using the voltage divider formula.

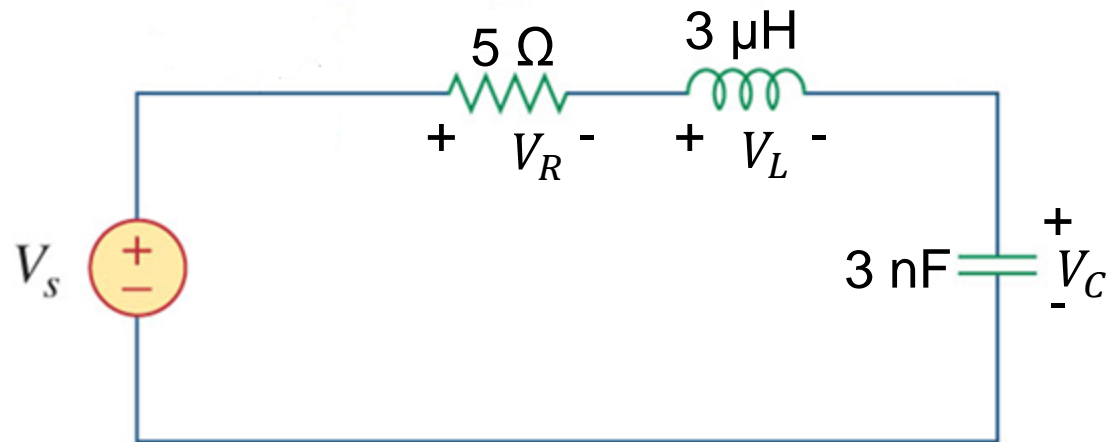Exercise IV

- Calculate the voltages across R/L/C, if $V_s = 50 \cos 2\pi f t$ V where $f = 1.68$ MHz.



Using the voltage divider formula,


$$V_R = \frac{R}{R + jL\omega + \frac{1}{j\omega C}} 50 = 50.0 \angle -1^\circ \text{ V},$$

$$V_C = \frac{\frac{1}{j\omega C}}{R + jL\omega + \frac{1}{j\omega C}} 50 = 315.7 \angle 89^\circ \text{ V},$$

$$V_L = \frac{jL\omega}{R + jL\omega + \frac{1}{j\omega C}} 50 = 316.6 \angle -91^\circ \text{ V}$$

Parallel Combination

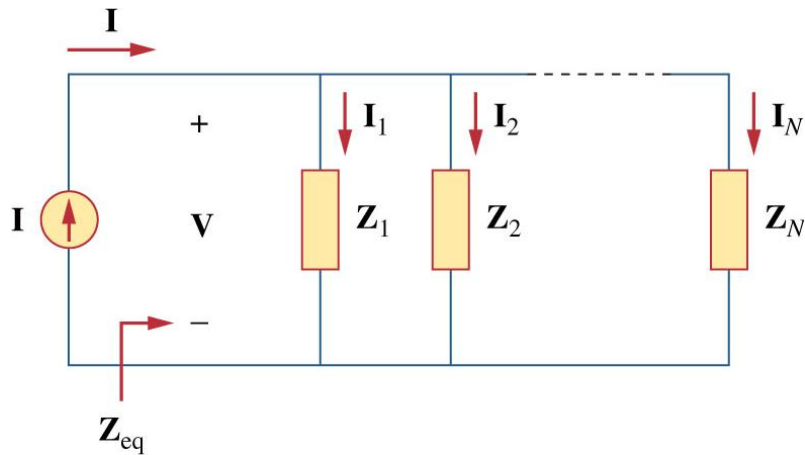- Likewise, elements combined in parallel will combine in the same fashion as resistors in parallel:



$$\frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \dots + \frac{1}{Z_N}$$

$$Y_{eq} = Y_1 + Y_2 + Y_3 + \dots + Y_N$$


$$I_1 = \frac{Y_1}{Y_1 + \dots + Y_N} I$$

$$I_2 = \frac{Y_2}{Y_1 + \dots + Y_N} I$$

.....


Parallel Inductor and Parallel Capacitor

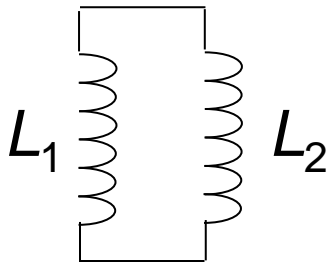Find the total impedance of the following circuits.
What are the equivalent inductance and capacitance?



$$\mathbf{Z}_{eq} = j\omega \frac{L_1 L_2}{(L_1 + L_2)} = j\omega L_{eq}$$

$$L_{eq} = \frac{L_1 L_2}{(L_1 + L_2)}$$

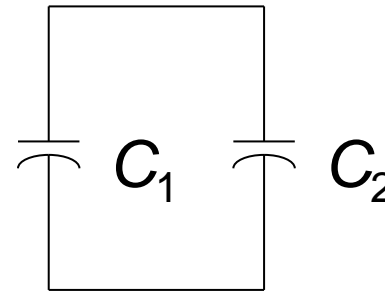


$$\mathbf{Z}_{eq} = \frac{1}{j\omega(C_1 + C_2)} = \frac{1}{j\omega C_{eq}}$$

$$C_{eq} = C_1 + C_2$$

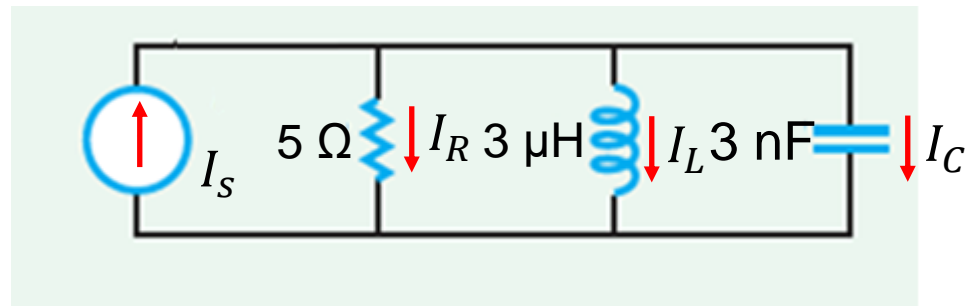Exercise V

- Calculate the currents into the R/L/C elements in the circuit shown below, if $I_S = 5 \cos 2\pi f t$ mA and $f = 1.68$ MHz.



Using the current divider formula,


$$I_R = \frac{\frac{1}{R}}{\frac{1}{R} + j\omega C + \frac{1}{j\omega L}} 5 = 5.0 \angle 0^\circ \text{ mA}$$

$$I_C = \frac{j\omega C}{\frac{1}{R} + j\omega C + \frac{1}{j\omega L}} 5 = 90.0 \angle 90^\circ \text{ mA}$$

$$I_L = \frac{\frac{1}{j\omega L}}{\frac{1}{R} + j\omega C + \frac{1}{j\omega L}} 5 = 90.0 \angle -90^\circ \text{ mA}$$

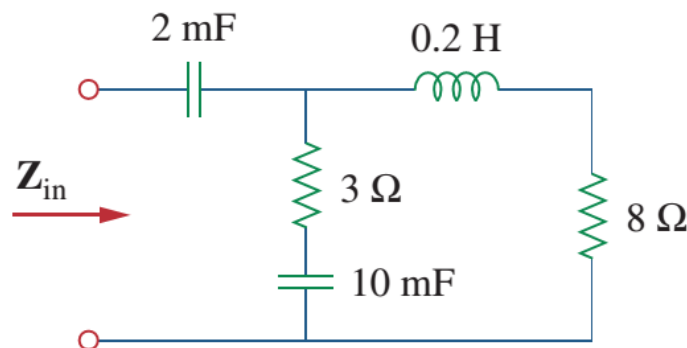Exercise

- Find the input impedance of the circuit below. $\omega = 50$ rad/s.



Solution:

$$\begin{aligned}
 Z &= \frac{1}{j0.002 \cdot 50} + \frac{(j0.2 \cdot 50 + 8)(3 + \frac{1}{j0.01 \cdot 50})}{(j0.2 \cdot 50 + 8) + (3 + \frac{1}{j0.01 \cdot 50})} \\
 &= -j10 + \frac{(j10 + 8)(3 - j2)}{11 + j8} \\
 &= 3.22 - j11.1 = 11.5 \angle -73.8^\circ \Omega
 \end{aligned}$$

AC Phasor Analysis General Procedure


Step1: Transform power sources into phasor domain

$$\begin{aligned} v_s(t) &= 12 \sin(\omega t - 45^\circ) \\ &= 12 \cos(\omega t - 45^\circ - 90^\circ) = 12 \cos(\omega t - 135^\circ) \text{ V.} \end{aligned}$$

$$V_s = 12e^{-j135^\circ} \text{ V.}$$

Step 2: Calculate R/L/C impedance

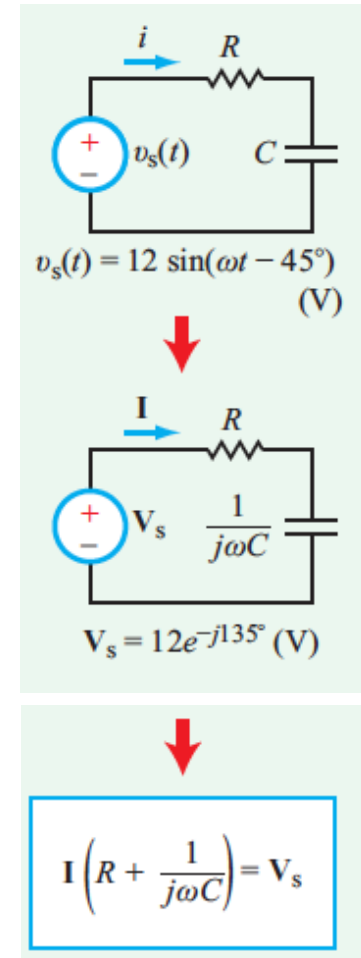Step 3: Derive circuit equations for I and V phasors using KCL/KVL.





AC Phasor Analysis General Procedure

Step 4: Solve for the I/V phasors.

$$\mathbf{I} = \frac{12e^{-j135^\circ}}{R + \frac{1}{j\omega C}} = \frac{j12\omega C e^{-j135^\circ}}{1 + j\omega RC}.$$

Using the specified values, namely $R = \sqrt{3} \text{ k}\Omega$, $C = 1 \text{ }\mu\text{F}$,
and $\omega = 10^3 \text{ rad/s}$,

$$\mathbf{I} = \frac{j12 \times 10^3 \times 10^{-6} e^{-j135^\circ}}{1 + j10^3 \times \sqrt{3} \times 10^3 \times 10^{-6}} = \frac{j12e^{-j135^\circ}}{1 + j\sqrt{3}} \text{ mA}.$$

$$\mathbf{I} = \frac{12e^{-j135^\circ} \cdot e^{j90^\circ}}{2e^{j60^\circ}} = 6e^{j(-135^\circ+90^\circ-60^\circ)} = 6e^{-j105^\circ} \text{ mA}.$$

Step 5: Transform the solutions back to the time domain.

To return to the time domain, we apply the fundamental relation between a sinusoidal function and its phasor counterpart, namely

$$i(t) = \Re[\mathbf{I}e^{j\omega t}] = \Re[6e^{-j105^\circ} e^{j\omega t}] = 6 \cos(\omega t - 105^\circ) \text{ mA}.$$




$$\mathbf{I} = \frac{\mathbf{V}_s}{R + \frac{1}{j\omega C}}$$




$$\begin{aligned} i(t) &= \Re[\mathbf{I}e^{j\omega t}] \\ &= 6 \cos(\omega t - 105^\circ) \\ &\quad (\text{mA}) \end{aligned}$$

Nodal Analysis

- Example---Find i_x

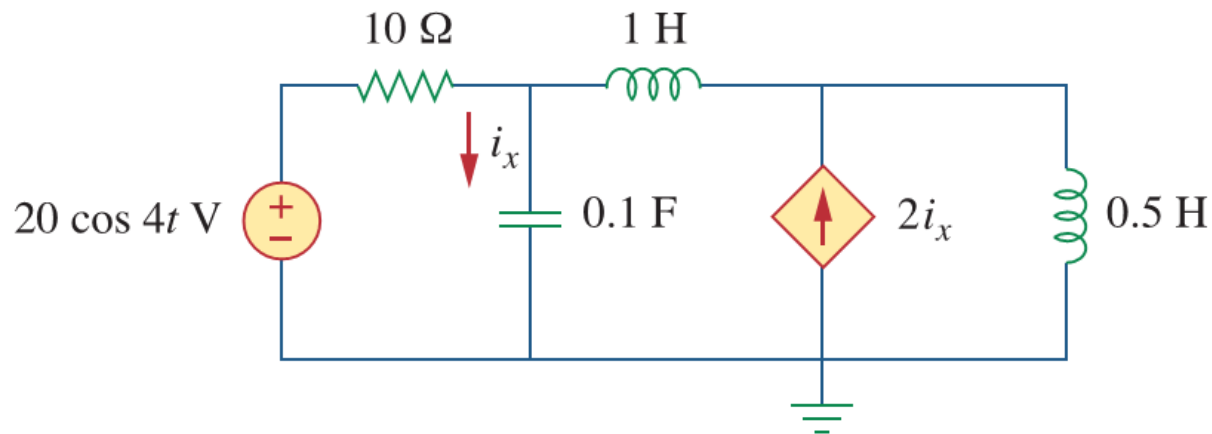

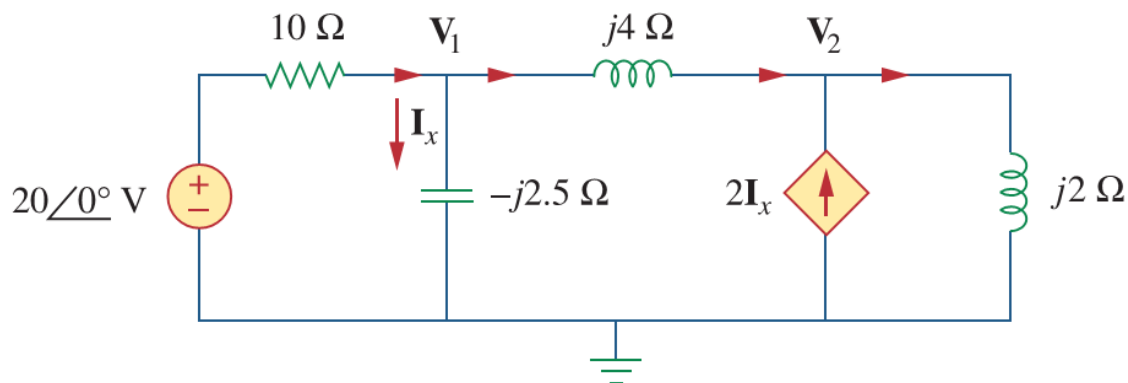


$$\begin{aligned} \frac{20 - V_1}{10} &= \frac{V_1}{-j2.5} + \frac{V_1 - V_2}{j4} \\ 2\frac{V_1}{-j2.5} + \frac{V_1 - V_2}{j4} &= \frac{V_2}{j2} \end{aligned} \quad \Rightarrow \quad \begin{bmatrix} \frac{1}{10} + j\frac{2}{5} - j\frac{1}{4} & j\frac{1}{4} \\ j\frac{4}{5} - j\frac{1}{4} & j\frac{1}{4} + j\frac{1}{2} \end{bmatrix} \begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} 2 \\ 0 \end{pmatrix}$$


$$i_x = V_1 / (-j2.5)$$

$$i_x = 7.59 \cos(4t + 108.4^\circ) \text{ A}$$

Branch Current Analysis

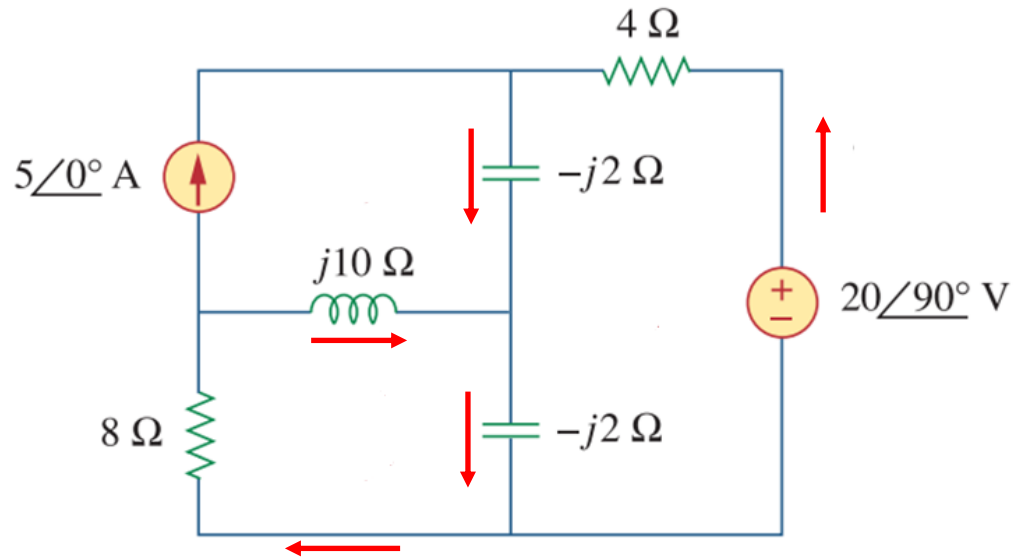

Branch Current Analysis

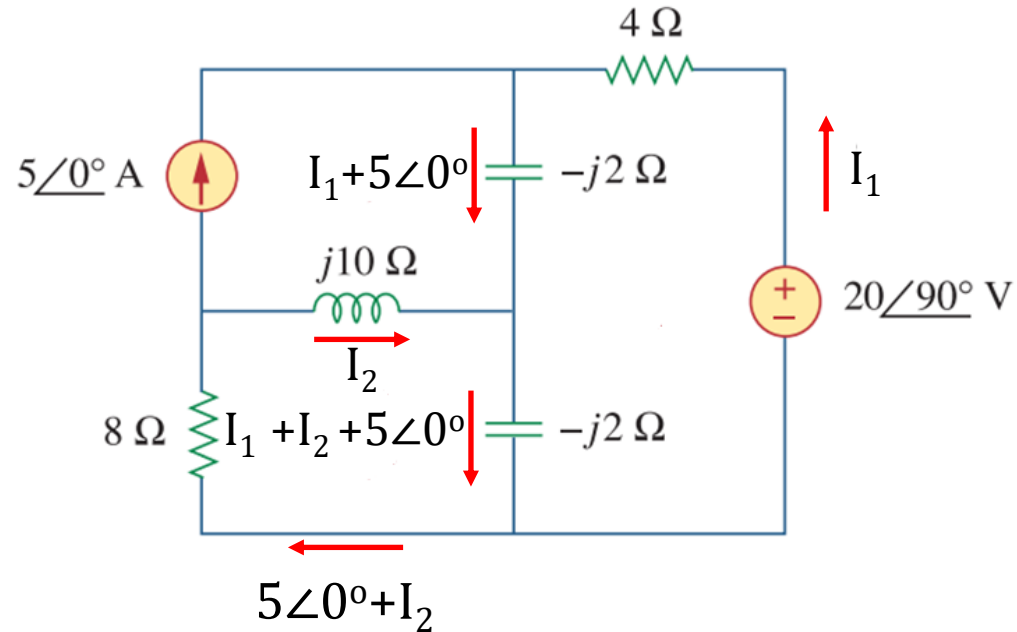

Using KVL, we have

$$-j20 + 4I_1 - j2(I_1 + 5) - j2(I_1 + I_2 + 5) = 0$$


$$j10I_2 - j2(I_1 + I_2 + 5) + 8(5 + I_2) = 0$$




$$I_1 = 6.12\angle 145^\circ \text{ A}$$

$$I_2 = 4.16\angle 135^\circ \text{ A}$$

Superposition-Example

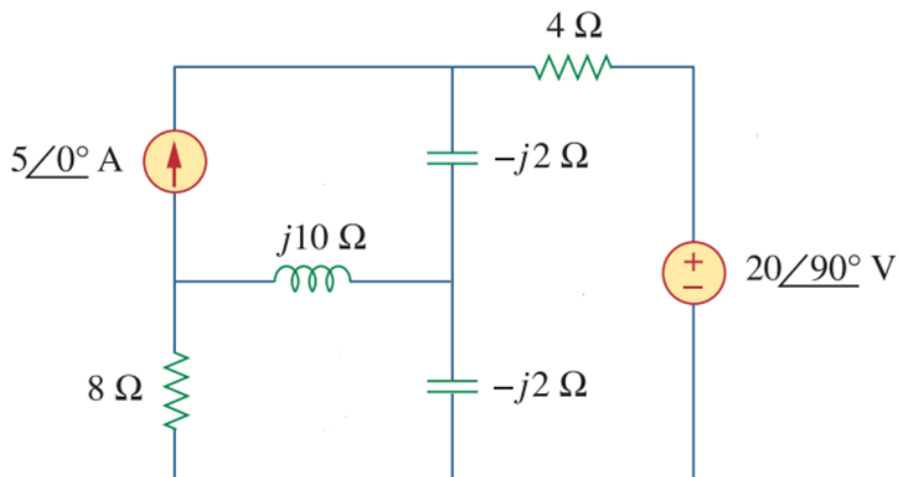


||

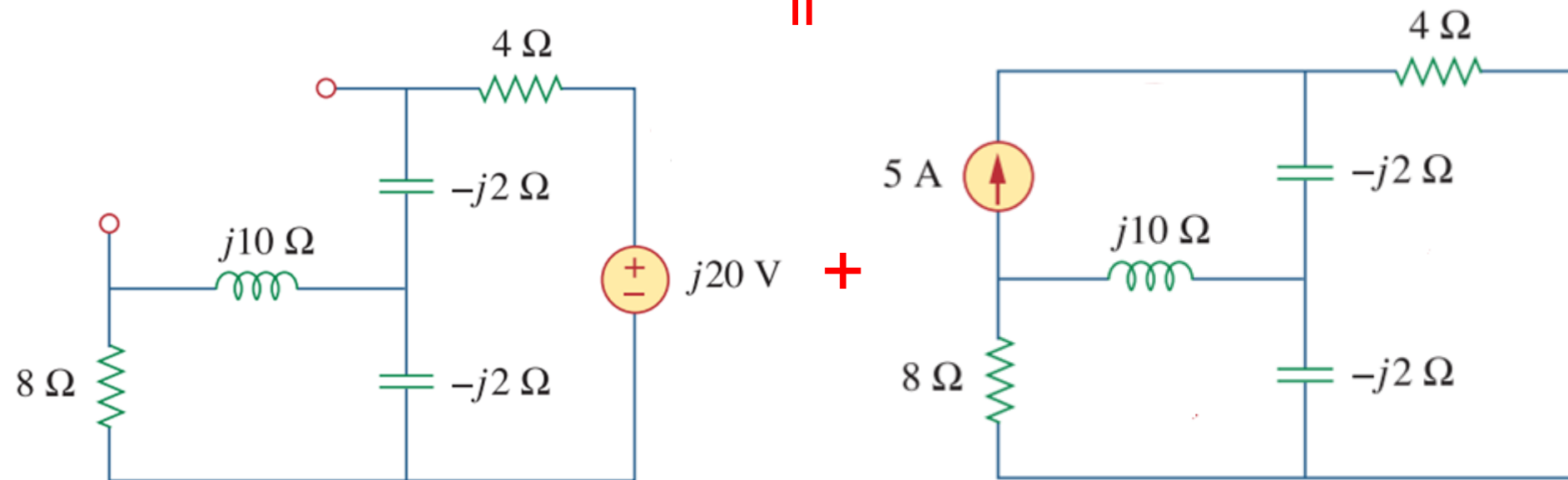

Delta-Wye Transformation in Phasor Domain

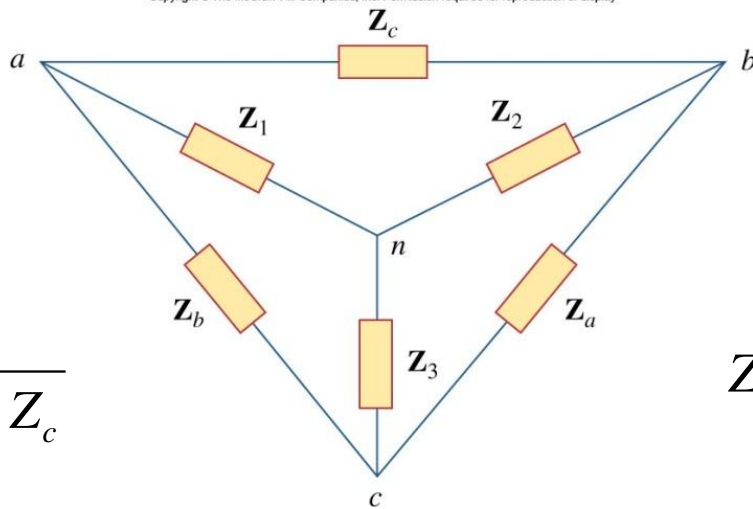Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



$$Z_1 = \frac{Z_b Z_c}{Z_a + Z_b + Z_c}$$

$$Z_2 = \frac{Z_c Z_a}{Z_a + Z_b + Z_c}$$

$$Z_3 = \frac{Z_a Z_b}{Z_a + Z_b + Z_c}$$


$$Z_a = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_1}$$

$$Z_b = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_2}$$

$$Z_c = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_3}$$




Thevenin Equivalent

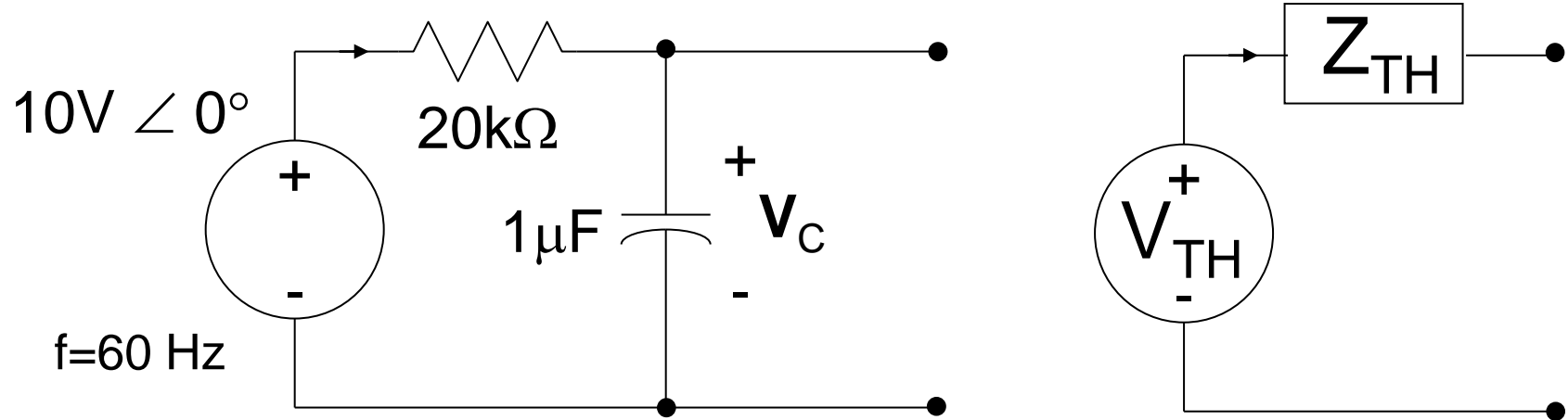



Thevenin Equivalent Solution

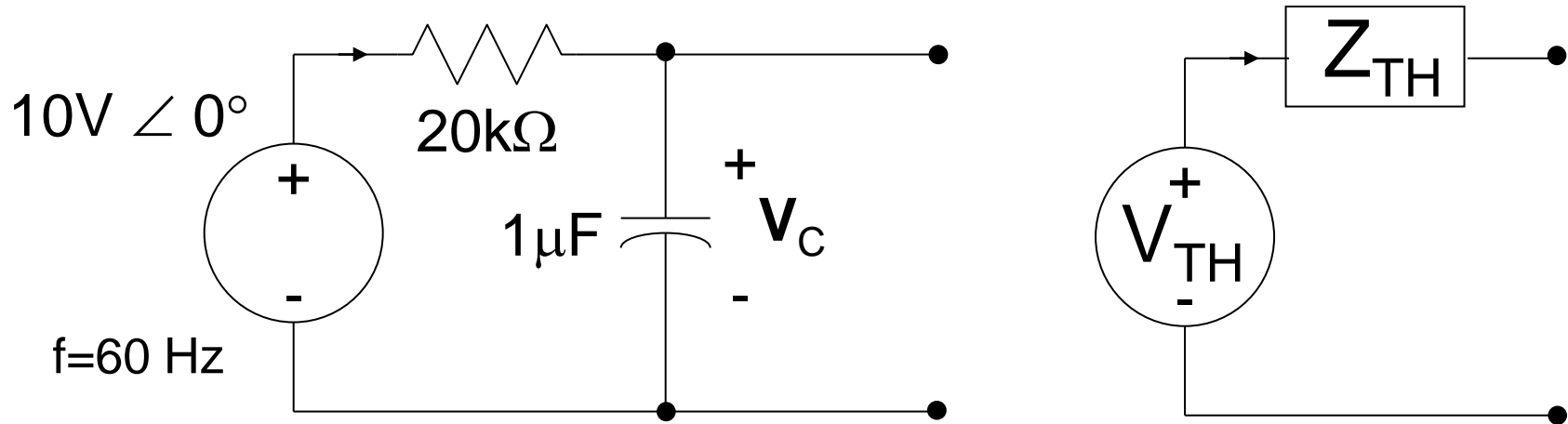


$$\mathbf{Z}_R = R = 20\text{k}\Omega = 20\text{k}\Omega \angle 0^\circ$$

$$\mathbf{Z}_C = 1/j(2\pi f \times 1\mu\text{F}) = 2.65\text{k}\Omega \angle -90^\circ$$

$$\mathbf{V}_{TH} = \mathbf{V}_{OC} = 10\text{V} \angle 0^\circ \left(\frac{2.65\text{k}\Omega \angle -90^\circ}{2.65\text{k}\Omega \angle -90^\circ + 20\text{k}\Omega \angle 0^\circ} \right) = 1.31 \angle -82.4^\circ \text{ V}$$

$$\mathbf{Z}_{TH} = \mathbf{Z}_R || \mathbf{Z}_C = \left(\frac{20\text{k}\Omega \angle 0^\circ \cdot 2.65\text{k}\Omega \angle -90^\circ}{2.65\text{k}\Omega \angle -90^\circ + 20\text{k}\Omega \angle 0^\circ} \right) = 2.62 \angle -82.4^\circ \text{ k}\Omega$$

Source transformation/Norton

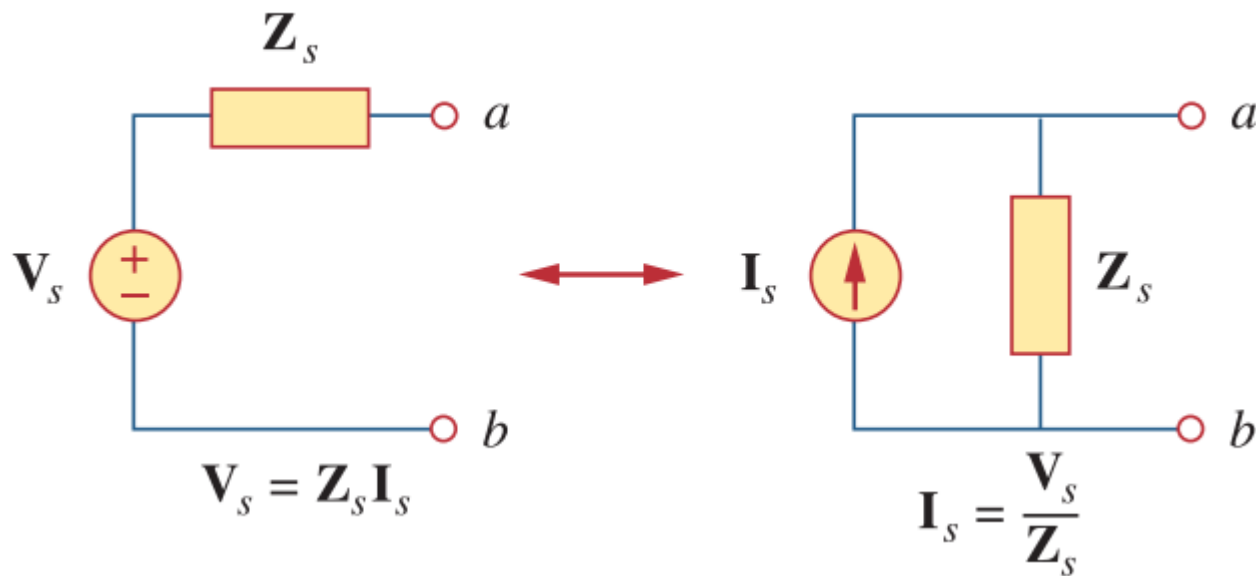


$$V_s = Z_s I_s \quad \Leftrightarrow \quad I_s = \frac{V_s}{Z_s}$$



AC Op Amp Circuits

- Op amps are also applicable in AC circuits.
- The ideal op-amp model assumes very large (>10000) open-loop gain which is true at dc and low frequencies.
- The range of frequencies over which the gain is very large depends on the specific op-amp design.

Wien-bridge Oscillator

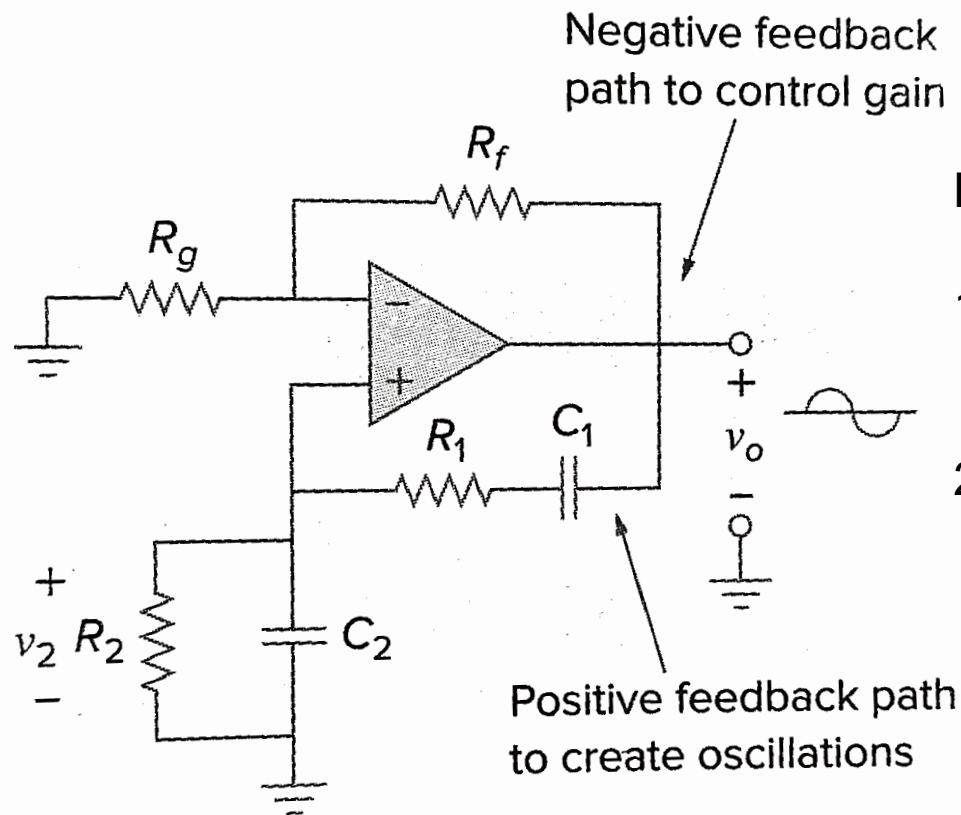

Barkhausen criteria:

1. The overall gain must be unity or greater.
2. The overall phase shift (from input to output and back to the input) must be zero.

From: Alexander & Sadiku, Fundamentals of Electric Circuits

Wien-bridge Oscillator

$$R_2 \parallel \frac{1}{j\omega C_2} = \frac{R_2 \frac{1}{j\omega C_2}}{\frac{1}{j\omega C_2} + R_2} = \frac{R_2}{1 + j\omega C_2 R_2}$$

$$\frac{V_2}{V_0} = \frac{\frac{R_2}{1 + j\omega C_2 R_2}}{\frac{R_2}{1 + j\omega C_2 R_2} + R_1 - j \frac{1}{\omega C_1}} = \frac{\omega C_1 R_2}{\omega(C_1 R_2 + C_1 R_1 + C_2 R_2) + j(\omega^2 C_1 R_1 C_2 R_2 - 1)}$$


Condition 2: $\omega^2 C_1 R_1 C_2 R_2 - 1 = 0$

If $R_1=R_2=R$ and $C_1=C_2=C$, then $\omega = \frac{1}{CR}$, $\frac{V_2}{V_0} = \frac{1}{3}$.

Condition 1: $A(V_+ - V_-) \geq V_0 \rightarrow \frac{V_+}{V_0} - \frac{V_-}{V_0} \geq \frac{1}{A} \sim 0$

$$\frac{1}{3} - \frac{R_g}{R_g + R_f} \geq 0 \rightarrow 1 + \frac{R_f}{R_g} \geq 3, \frac{R_f}{R_g} \geq 2$$

AC Power in Time Domain: Instantaneous

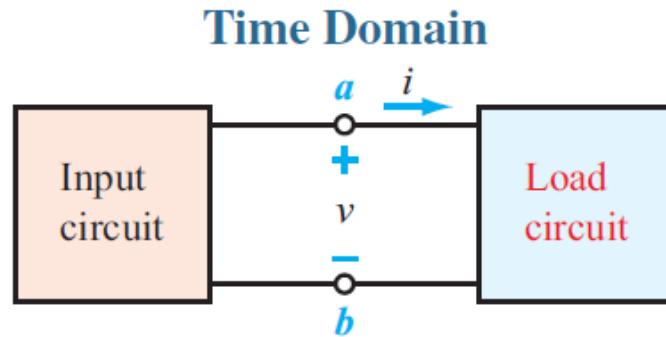

$$v(t) = V_m \cos(\omega t + \theta_v) \quad i(t) = I_m \cos(\omega t + \theta_i)$$

Instantaneous power:
power at any instant of time.

$$p(t) = v(t)i(t) = V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$$

$$p(t) = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$




AC power

- Average power formula
- Power formula in terms of RMS values of current and voltage
- Maximum power transfer

AC Power in Time Domain: Instantaneous


$$\theta_v = 0$$

$$\theta_i = 0$$

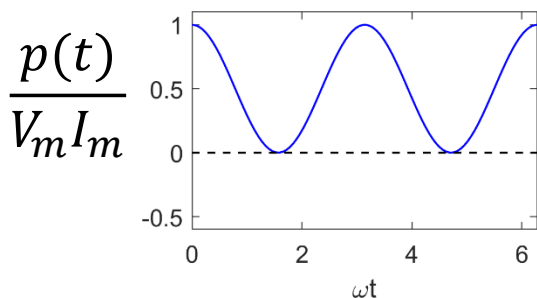


$$\theta_v = 0$$

$$\theta_i = 30^\circ$$

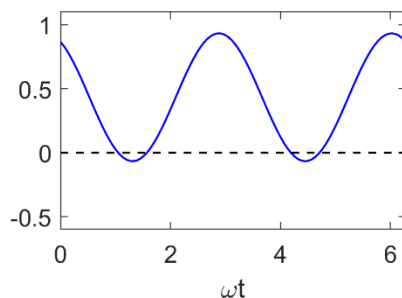


$$\theta_v = 0$$

$$\theta_i = 60^\circ$$

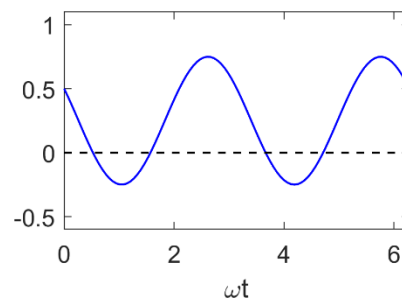

$$\theta_v = 0$$

$$\theta_i = 90^\circ$$

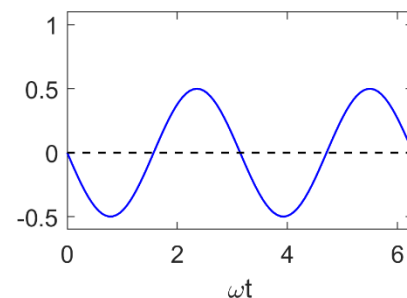

$$p(t) = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$

$$= \frac{1}{2} V_m I_m [\cos(\theta_v - \theta_i) + \cos(2\omega t + 2\theta_i) \cos(\theta_v - \theta_i) - \sin(2\omega t + 2\theta_i) \sin(\theta_v - \theta_i)]$$

$$= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) [1 + \cos(2\omega t + 2\theta_i)] - \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i) \sin(2\omega t + 2\theta_i)$$


≥ 0 ; 电源向负载输出

时正时负; 负载与电源之间来回交换

Average Power

$$v(t) = V_m \cos(\omega t + \theta_v) \quad i(t) = I_m \cos(\omega t + \theta_i)$$
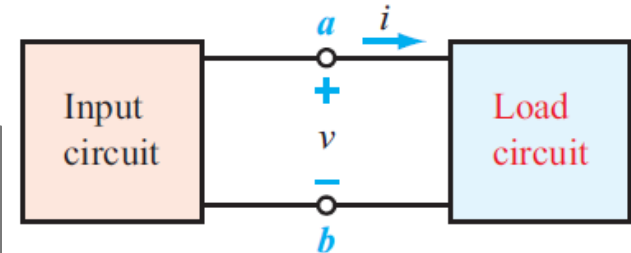
$$p(t) = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$



Average (or real) power (unit: watts)

The **average power**, in watts, is the average of the instantaneous power over one period.

$$\begin{aligned} P_{\text{real}} &= \frac{1}{T} \int_0^T p(t) dt = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = \frac{1}{2} \text{Re}\{VI^*\} \\ &= \frac{1}{2} \text{Re}\left\{\frac{VV^*}{Z^*}\right\} = \frac{V_m^2}{2} \text{Re}\left\{\frac{1}{Z^*}\right\} = \frac{V_m^2}{2|Z|^2} \text{Re}\{Z\} \\ &= \frac{1}{2} \text{Re}\{II^*Z\} = \frac{I_m^2}{2} \text{Re}\{Z\} \end{aligned}$$

$$I = \frac{V}{Z}$$



Complex Power

Real power: $P_{\text{real}} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = \frac{1}{2} \text{Re}\{VI^*\}$

Reactive power: $P_{\text{reactive}} = \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i) = \frac{1}{2} \text{Im}\{VI^*\}$

Complex power: $P_{\text{complex}} = \frac{1}{2} VI^* = P_{\text{real}} + jP_{\text{reactive}}$

Two special cases for average power P

- For a purely resistive load R :

$$P = \frac{1}{2} V_m I_m = \frac{1}{2} I_m^2 R = I_{\text{eff}}^2 R$$


- For a purely reactive load:

$$P = \frac{1}{2} V_m I_m \cos 90^\circ = 0$$

A resistive load (R) absorbs power at all times, while a reactive load (L or C) absorbs zero average power.

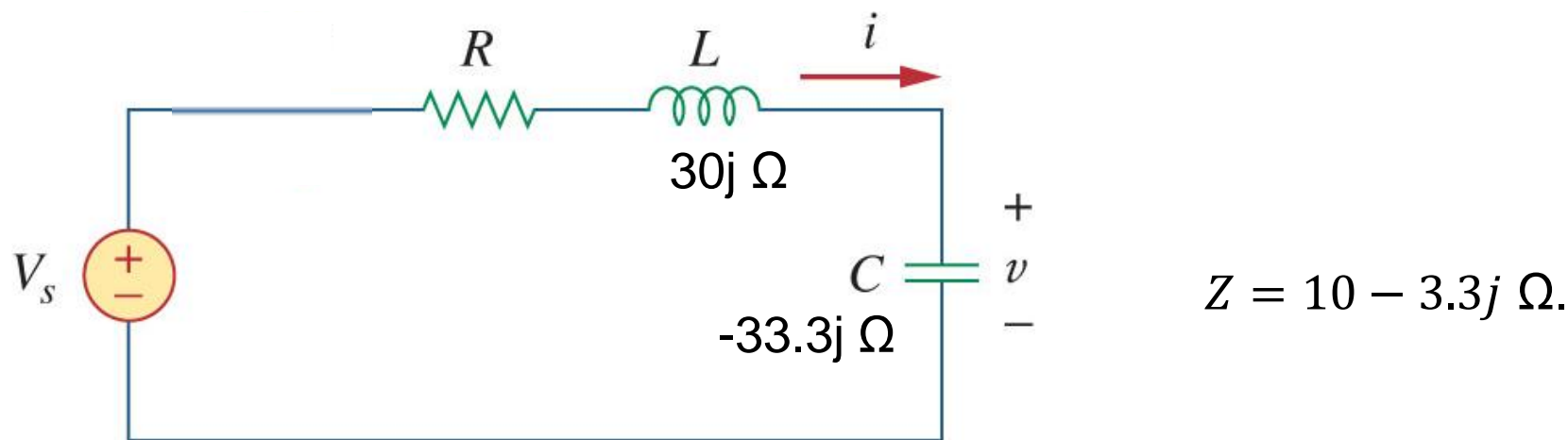Exercise

- Determine the average power dissipated in the circuit below, in which $R=10\ \Omega$, $L=3\ \mu\text{H}$, $C=3\ \text{nF}$, and $V_s = 50\cos(1.0 \times 10^7 t + 70^\circ)\ \text{V}$.



$$P = \frac{1}{2} \frac{V_{s,m}^2}{|Z|^2} \text{Re}\{Z\} = \frac{1}{2} \frac{50^2}{(100 + 3.3^2)} 10 = 112.5\ \text{W}$$

The power dissipated by the resistor: $P_R = \overline{i(t)^2 R} = \frac{V_{s,m}^2}{|Z|^2} \overline{\cos^2(10^7 t + 70^\circ)} R = P$

Note: $\overline{\cos^2(10^7 t + 70^\circ)} = \frac{1}{2}$

Power with Multiple Frequency Components

$$v(t) = V_{m,1} \cos(\omega_1 t + \theta_{v,1}) + V_{m,2} \cos(\omega_2 t + \theta_{v,2});$$

$$i(t) = I_{m,1} \cos(\omega_1 t + \theta_{i,1}) + I_{m,2} \cos(\omega_2 t + \theta_{i,2});$$

$$\begin{aligned} p(t) = v(t)i(t) = & V_{m,1} I_{m,1} \cos(\omega_1 t + \theta_{v,1}) \cos(\omega_1 t + \theta_{i,1}) \\ & + V_{m,2} I_{m,2} \cos(\omega_2 t + \theta_{v,2}) \cos(\omega_2 t + \theta_{i,2}) \\ & + V_{m,1} I_{m,2} \cos(\omega_1 t + \theta_{v,1}) \cos(\omega_2 t + \theta_{i,2}) \\ & + V_{m,2} I_{m,1} \cos(\omega_2 t + \theta_{v,2}) \cos(\omega_1 t + \theta_{i,1}) \end{aligned}$$

The third and fourth terms are equal to zero after time average.


The time averages of the first and second terms are $\frac{1}{2} V_{m,1} I_{m,1} \cos(\theta_{v,1} - \theta_{i,1})$ and $\frac{1}{2} V_{m,2} I_{m,2} \cos(\theta_{v,2} - \theta_{i,2})$.

Therefore, the total average power is equal to the sum of average powers generated by each component alone.

Effective Value (RMS)

- For any periodic function $x(t)$ in general, its rms value is

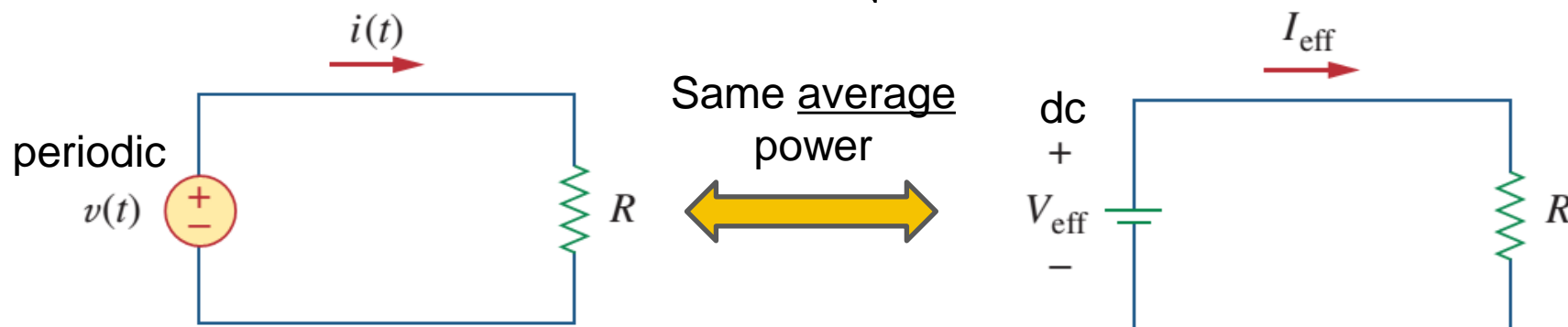
$$X_{\text{eff}} = X_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T x^2(t) dt}$$



$$I_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$

$$V_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

Example: 三角波的有效电压

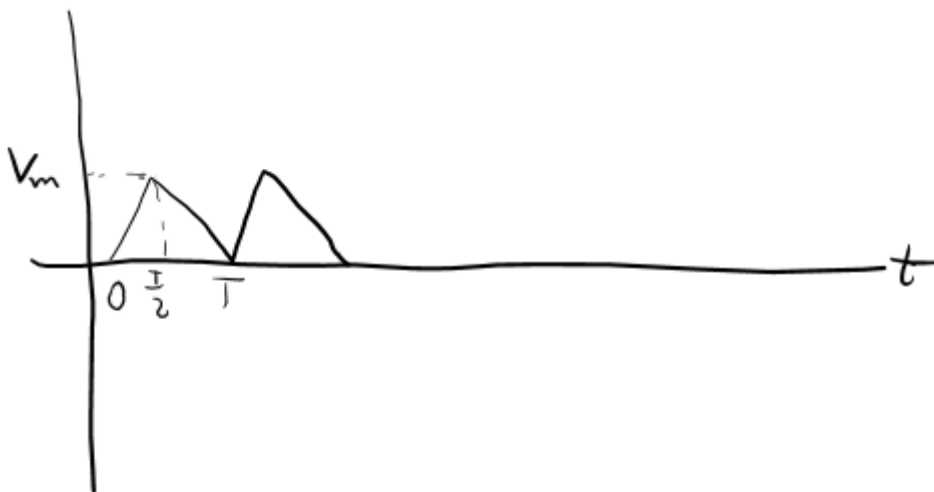


$$\frac{1}{\frac{T}{2}} \int_0^{\frac{T}{2}} \left[\frac{V_m}{(\frac{T}{2})} t \right]^2 dt = \frac{V_m^2}{(\frac{T}{2})^3} \frac{1}{3} \left(\frac{T}{2} \right)^3 = \frac{V_m^2}{3}$$


$$V_{rms} = \frac{V_m}{\sqrt{3}}$$

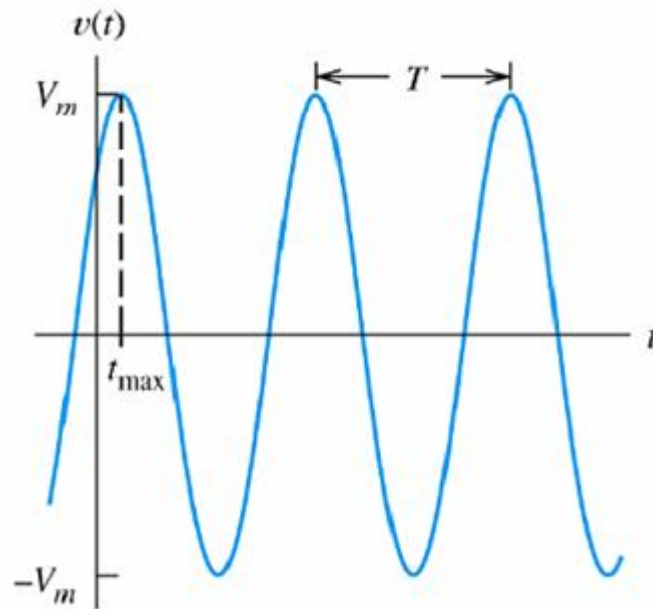Example: RMS of a Sinusoidal


- The RMS value of $v(t) = V_m \cos(\omega t + \phi)$


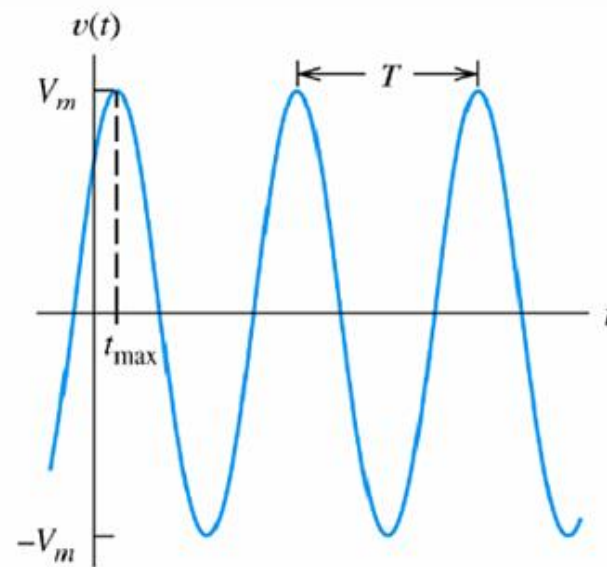
$$\begin{aligned} V_{\text{rms}} &= \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} v^2(t) dt} \\ &= \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} V_m^2 \cdot \cos^2(\omega t + \phi) dt} \\ &= \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} V_m^2 \cdot \frac{1}{2} [1 + \cos 2(\omega t + \phi)] dt} \\ &= \frac{V_m}{\sqrt{2}} \end{aligned}$$



V_{RMS} vs I_{RMS} of a Sinusoidal

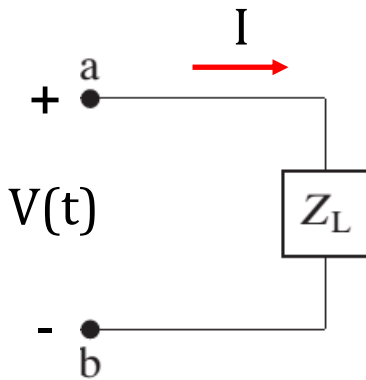

For the phasor \mathbf{V} of $V(t)$, we have $|\mathbf{V}| = \sqrt{2}V_{\text{rms}}$.

$$I = \frac{V}{Z_L} \quad \longrightarrow \quad I_{\text{rms}} = \frac{V_{\text{rms}}}{|Z_L|}$$

Average Power

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos(\theta_v - \theta_i) \\ = V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i)$$




视在功率: $S = V_{\text{rms}} I_{\text{rms}}$

- The power factor


$$\text{pf} = \frac{P}{S} = \cos(\theta_v - \theta_i)$$

- $(\theta_v - \theta_i)$ is called power factor angle.
 - >0 means a *lagging* pf (current lags voltage)
 - <0 means a *leading* pf (current leads voltage)
- pf ranges from 0 to 1.

Power Factor Correction

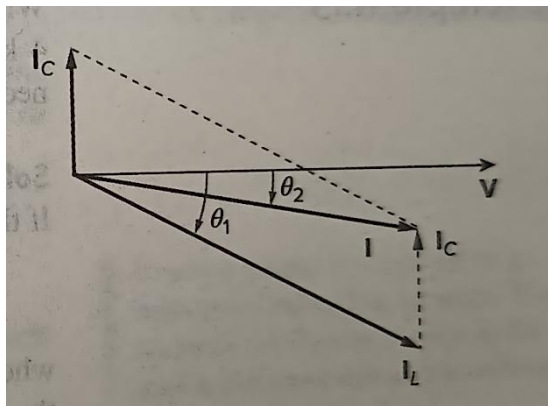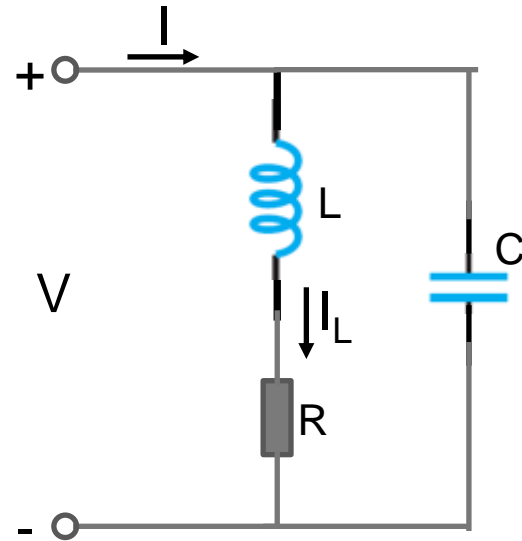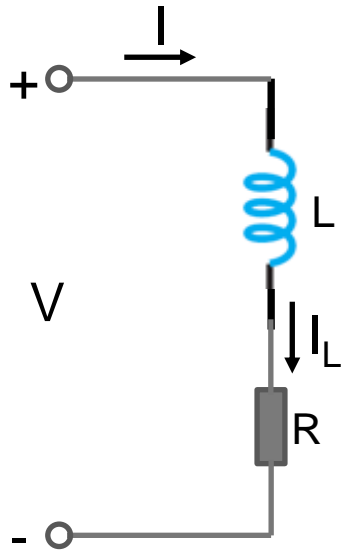

Maximum Power Transfer

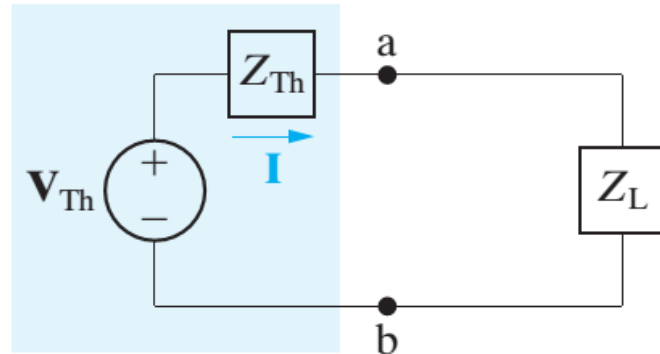

$$V_{ab} = \frac{V_{Th}}{Z_{Th} + Z_L} Z_L$$

$$V_{ab,rms} = \frac{V_{Th,rms}}{|Z_{Th} + Z_L|} |Z_L|$$

$$I_{ab,rms} = \frac{V_{Th,rms}}{|Z_{Th} + Z_L|}$$

$$\begin{aligned} \text{Load power } P &= V_{ab,rms} I_{ab,rms} \operatorname{Re}\left(\frac{Z_L}{|Z_L|}\right) = \frac{V_{Th,rms}^2}{|Z_{Th} + Z_L|^2} \operatorname{Re}(Z_L) \\ &= \frac{V_{Th,rms}^2}{[\operatorname{Re}(Z_{Th}) + \operatorname{Re}(Z_L)]^2 + [\operatorname{Im}(Z_{Th}) + \operatorname{Im}(Z_L)]^2} \operatorname{Re}(Z_L) \end{aligned}$$

It reaches maximum when $\operatorname{Im}(Z_{Th}) = -\operatorname{Im}(Z_L)$ and $\operatorname{Re}(Z_{Th}) = \operatorname{Re}(Z_L)$, i.e. $Z_L = Z_{Th}^*$. Note we have $\operatorname{Re}(Z_{Th}) > 0$ and $\operatorname{Re}(Z_L) > 0$.