



Chapter 10

- Filters







Outline


- Filter types and parameters
- Passive filters: RC, RL, RLC
- Active filters
- 50 Hz notch filter

Filter types


- Circuit designed to retain certain frequency range but discard or attenuate others
 - *Low-pass*: pass low frequencies and reject high frequencies
 - *High-pass*: pass high frequencies and reject low frequencies
 - *Band-pass*: pass some particular range of frequencies, reject other frequencies outside that band
 - *Band-reject (notch)*: reject a range of frequencies and pass all other frequencies

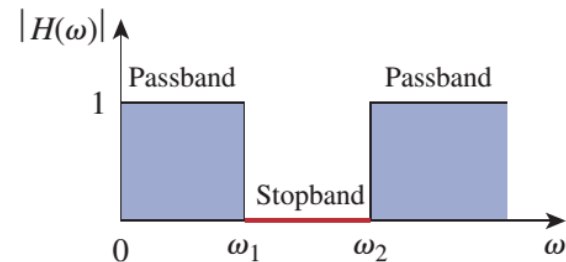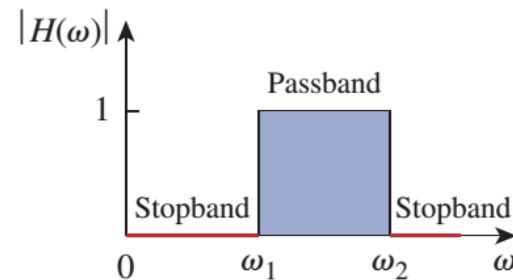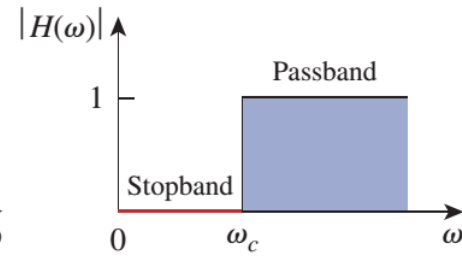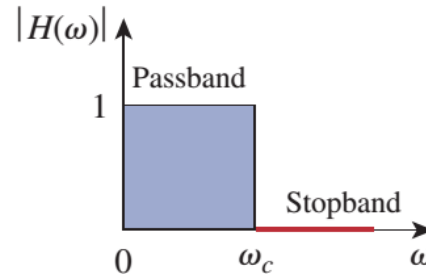


Filters – Realistic Curves

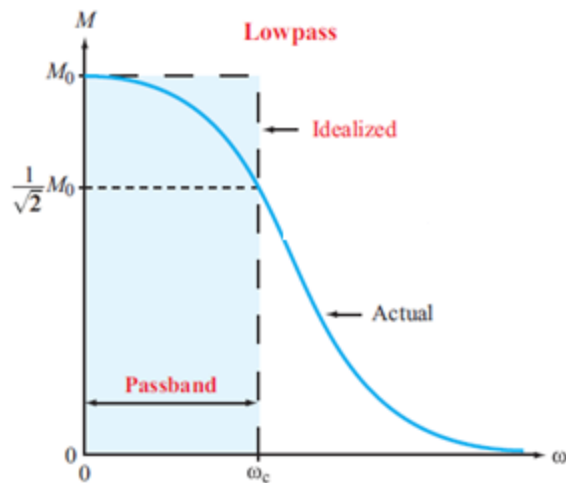


(a) Lowpass filter

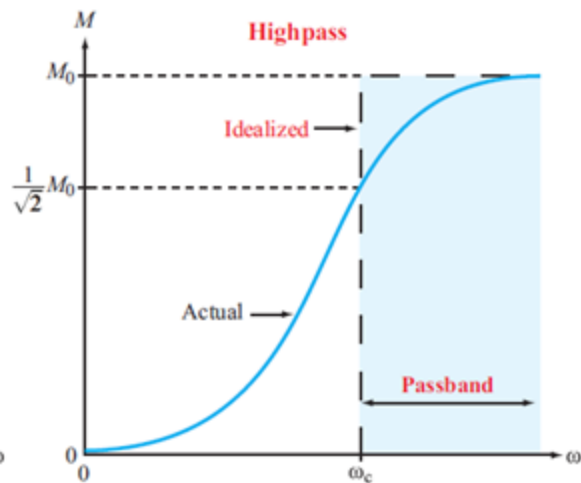

(b) Highpass filter

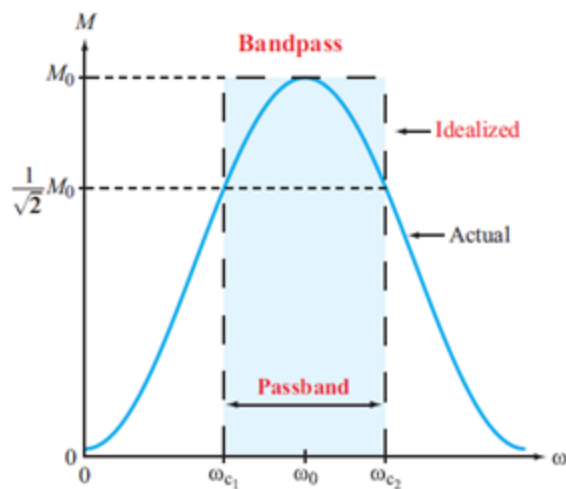

(c) Bandpass filter

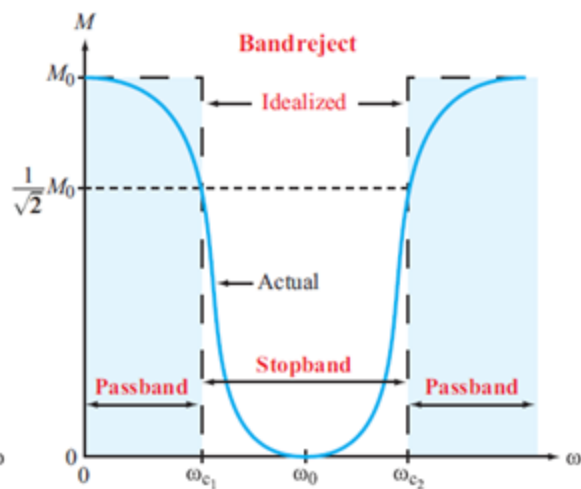

(d) Bandreject filter



Filter parameters

- Characteristic frequencies (cutoff frequencies)
- Bandwidth
- Quality factor (Q factor)/ Damping factor ($1/Q$)
- Sensitivity to component value changes
- Group delay

Group delay

$$\text{Delay } \tau(\omega) = -\frac{d\varphi(\omega)}{d\omega}$$

Prove that if both the amplitude and group delay of the transfer function are constant in the frequency range of interest, then the output signal is a delayed version of the input signal.

Proof:

$$S_{\text{in}}(t) = \int_{\omega_1}^{\omega_2} \bar{f}(\omega) e^{j\omega t} d\omega$$

$$S_{\text{out}}(t) = \int_{\omega_1}^{\omega_2} \bar{f}(\omega) |H(\omega)| e^{j\varphi(\omega)} e^{j\omega t} d\omega$$

For constant $|H(\omega)|$ and $\tau(\omega)$ in $[\omega_1, \omega_2]$, i.e.




$$|H(\omega)| = H_0$$

$$\varphi(\omega) = -\tau_0 \omega + \varphi_0$$

$$S_{\text{out}}(t) = H_0 \int_{\omega_1}^{\omega_2} \bar{f}(\omega) e^{j(-\tau_0 \omega + \varphi_0)} e^{j\omega t} d\omega = H_0 e^{j\varphi_0} S_{\text{in}}(t - \tau_0)$$


Passive Filters

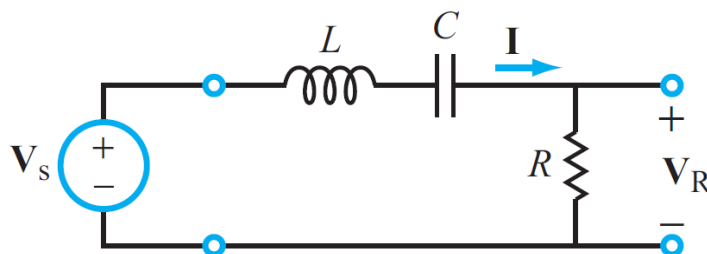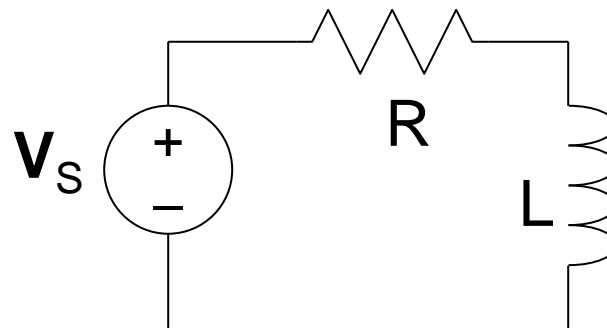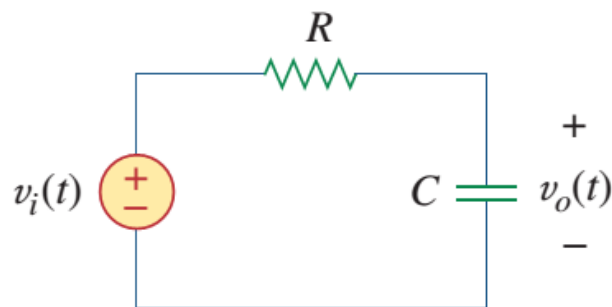- A filter is passive if it consists only of passive elements
 - R, L and C



First-Order RC Low-pass Filter

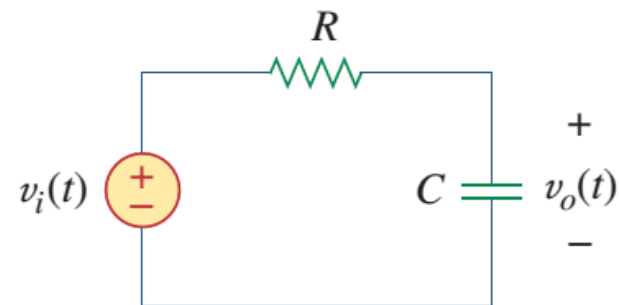- A typical low-pass filter is formed when the output of a RC circuit is taken off the capacitor.




$$\mathbf{H}(\omega) = \frac{1}{\frac{1}{j\omega C} + R} \frac{1}{j\omega C} = \frac{1}{1 + j\omega/\omega_c}$$

- The cutoff frequency is:

$$\omega_c = \frac{1}{CR}, |H(\omega_c)| = 0.707$$

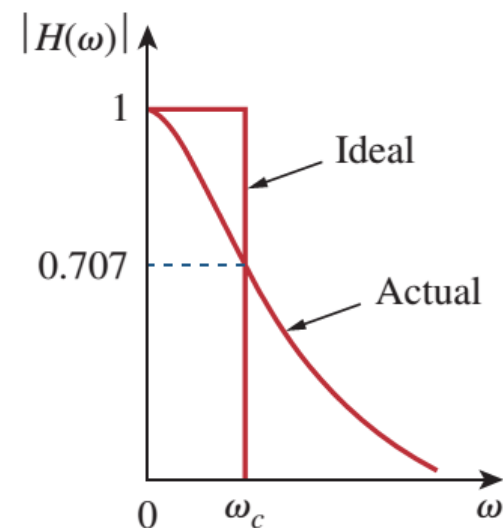- Filter is designed to pass from DC up to ω_c .





First-Order RC High-pass Filter

$$H(\omega) = \frac{R}{\frac{1}{j\omega C} + R} = \frac{j\omega/\omega_c}{1 + j\omega/\omega_c}$$


- The cutoff frequency.

$$\omega_c = \frac{1}{CR}, |H(\omega_c)| = 0.707$$

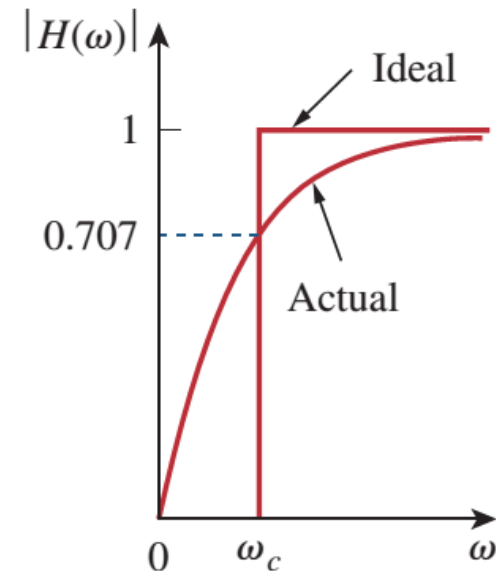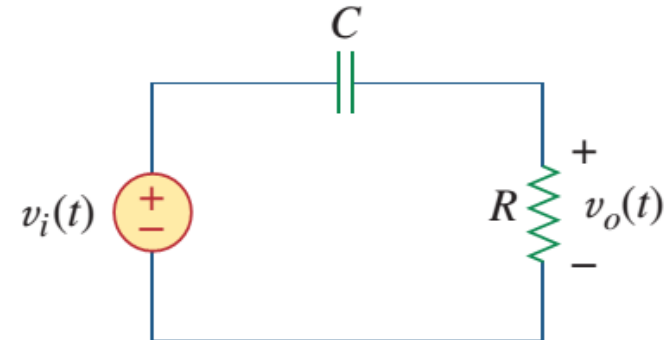- The difference being that the frequencies passed go from ω_c to infinity.




How about RL Circuits?

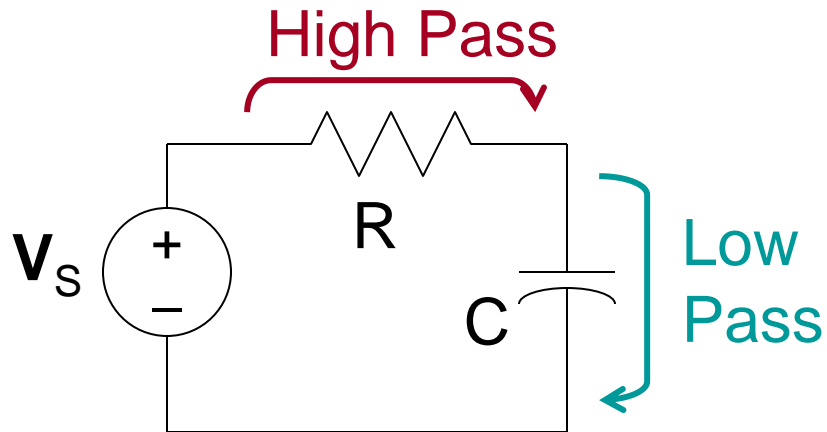

$$H_R(\omega) = \frac{j\omega/\omega_c}{1 + j\omega/\omega_c}$$

$$H_C(\omega) = \frac{1}{1 + j\omega/\omega_c}$$

$$\omega_c = \frac{1}{RC}$$

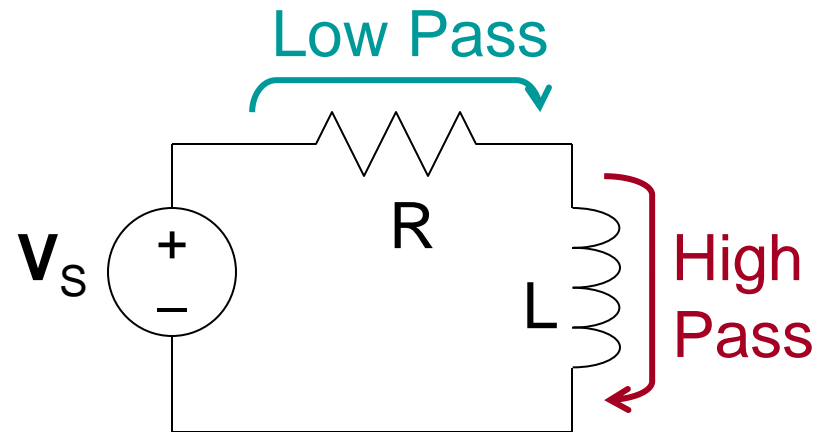


$$H_R(\omega) = \frac{R}{R + j\omega L} = \frac{1}{1 + j\omega/\omega_c}$$

$$H_L(\omega) = \frac{j\omega L}{R + j\omega L} = \frac{j\omega/\omega_c}{1 + j\omega/\omega_c}$$

$$\omega_c = \frac{R}{L}$$



Bandpass RLC Filter

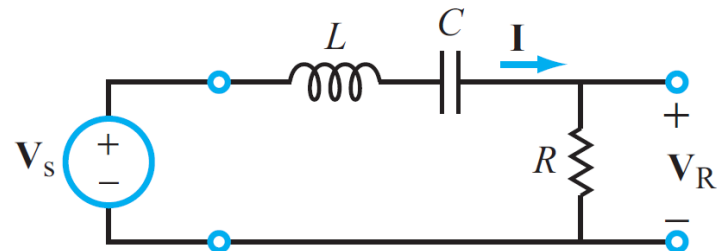

$$H_R(\omega) = \frac{R}{R + 1/j\omega C + j\omega L}$$

$$= \frac{\frac{1}{Q} \frac{j\omega}{\omega_c}}{1 + \frac{1}{Q} \frac{j\omega}{\omega_c} + (j\omega)^2 / \omega_c^2}$$

$$|H_R(\omega_c)| = 1$$

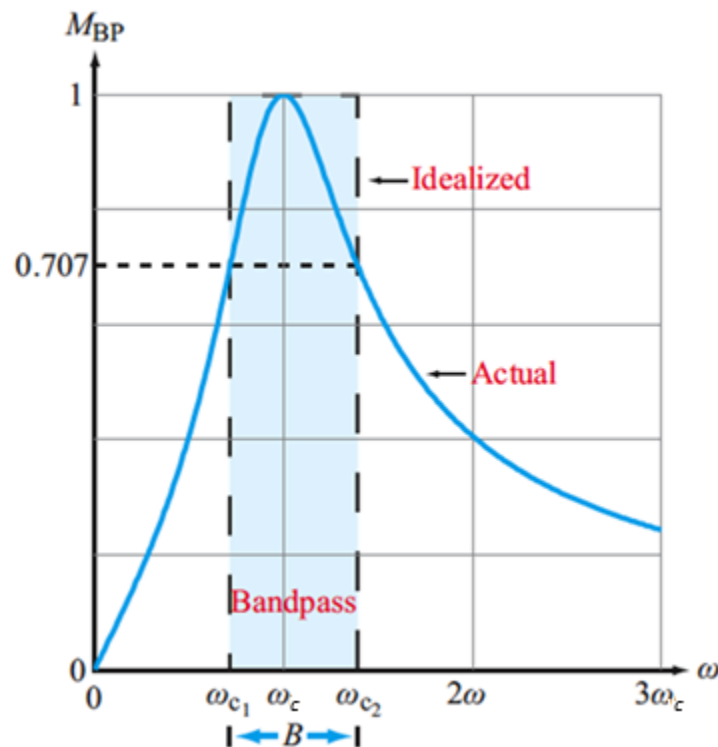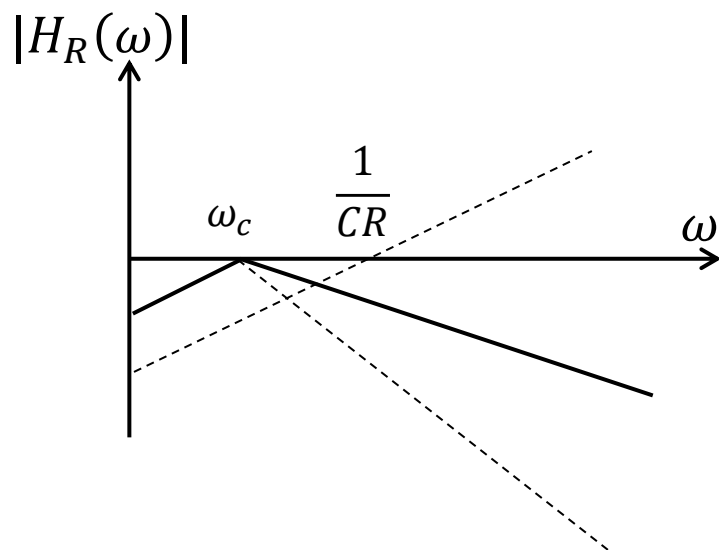

Bandwidth of the Pass Band

$$H_R(\omega) = \frac{\frac{1}{Q} \frac{j\omega}{\omega_c}}{1 + \frac{1}{Q} \frac{j\omega}{\omega_c} + (j\omega)^2 / \omega_c^2}$$


$$|H_R(\omega)|^2 = \frac{\left(\frac{1}{Q} \frac{\omega}{\omega_c}\right)^2}{\left[1 - \frac{\omega^2}{\omega_c^2}\right]^2 + \left(\frac{1}{Q} \frac{\omega}{\omega_c}\right)^2} = \frac{1}{2}$$

$$1 - \frac{\omega^2}{\omega_c^2} = \pm \frac{1}{Q} \frac{\omega}{\omega_c}$$

$\omega_{1,2} = \left[\mp \frac{1}{2Q} + \sqrt{1 + \frac{1}{4Q^2}} \right] \omega_c$, same as the cutoff frequencies for the resonance peak.

$$B = \frac{\omega_c}{Q} = \alpha \omega_c$$



Band-reject (Band-stop) Filter

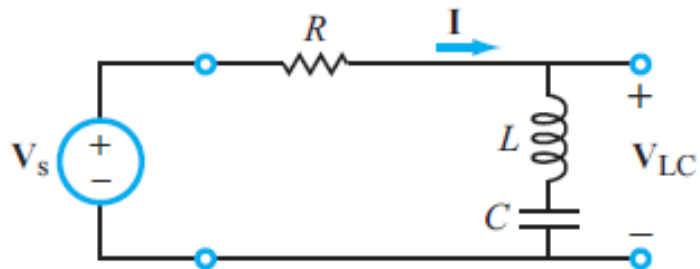

$$H_{LC}(\omega) = \frac{1 + (j\omega)2LC}{1 + j\omega CR + (j\omega)2LC}$$

$$= \frac{1 + (j\omega)^2/\omega_c^2}{1 + \frac{1}{Q} \frac{j\omega}{\omega_c} + (j\omega)^2/\omega_c^2}$$

$$|H_R(\omega_c)| = 0$$

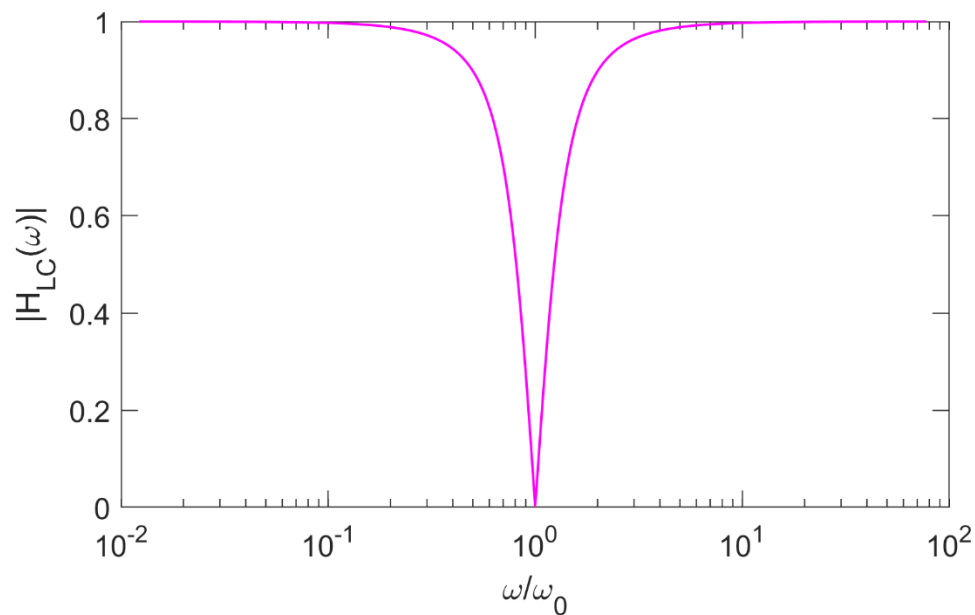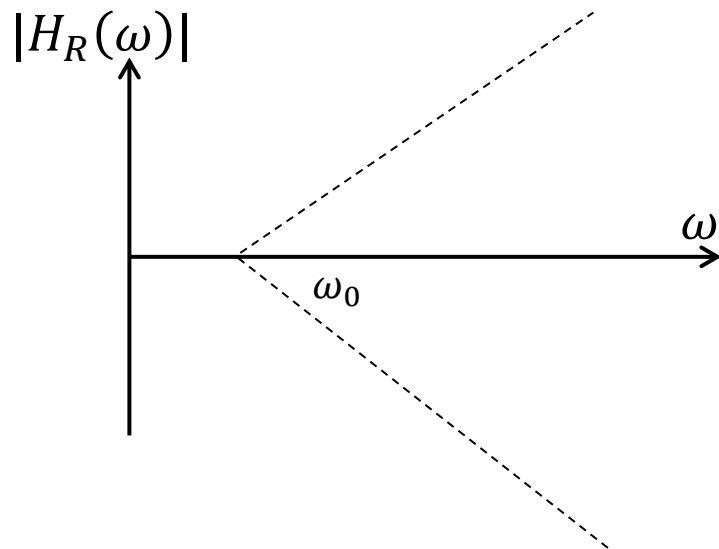

Bandwidth of the Stop Band

$$H_{LC}(\omega) = \frac{1 + (j\omega)^2/\omega_c^2}{1 + \frac{1}{Q} \frac{j\omega}{\omega_c} + (j\omega)^2/\omega_c^2}$$


$$|H_{LC}(\omega)|^2 = \frac{[1 - \frac{\omega^2}{\omega_c^2}]^2}{[1 - \frac{\omega^2}{\omega_c^2}]^2 + \left(\frac{1}{Q} \frac{\omega}{\omega_c}\right)^2} = \frac{1}{2}$$

$$1 - \frac{\omega^2}{\omega_c^2} = \pm \frac{1}{Q} \frac{\omega}{\omega_c}$$


$\omega_{1,2} = \left[\mp \frac{1}{2Q} + \sqrt{1 + \frac{1}{4Q^2}} \right] \omega_c$, same as the cutoff frequencies for the resonance peak.

$$B = \frac{\omega_c}{Q} = \alpha \omega_c$$

Second-Order RLC Filter Circuits

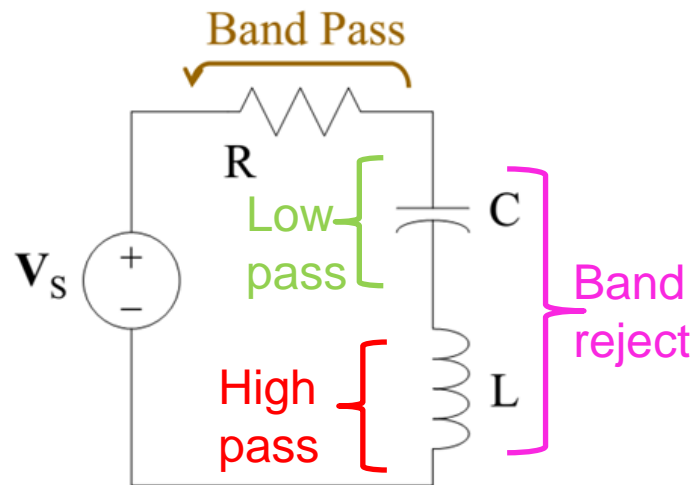

$Q=1.36$

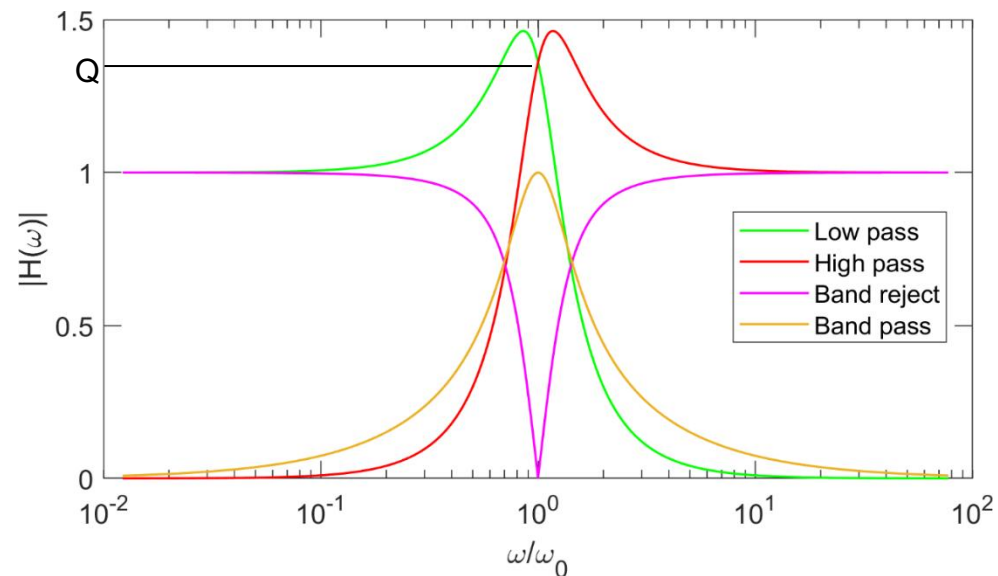


$$Z = R + 1/j\omega C + j\omega L$$

$$H_{BP} = R/Z$$

$$H_{LP} = \frac{1}{j\omega C Z}$$

$$H_{HP} = \frac{j\omega L}{Z}$$

$$H_{BR} = H_{LP} + H_{HP}$$

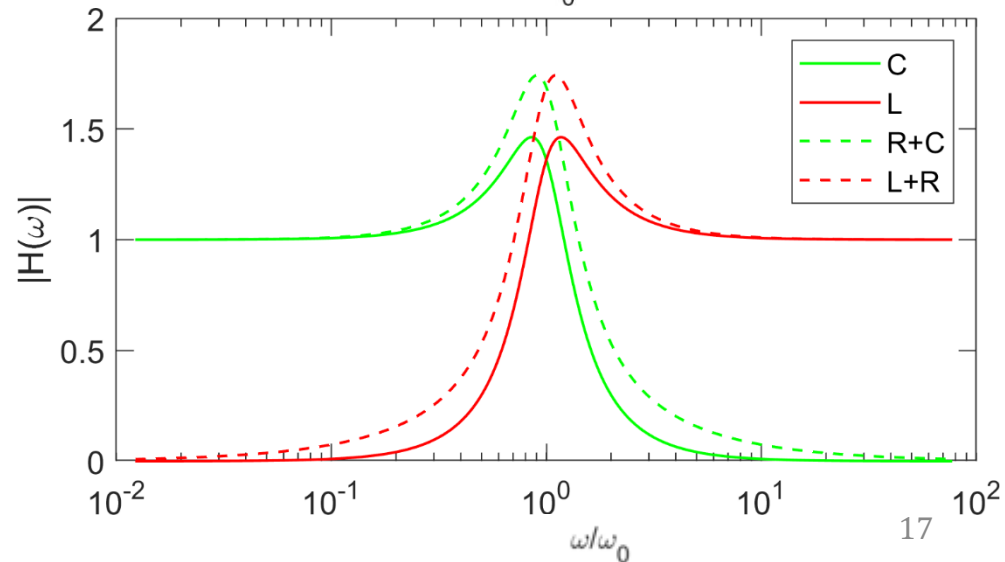



Summary (passive filters)

First order (Series RC/RL):

$$\text{Low pass: } H(\omega) = \frac{1}{j\omega/\omega_c + 1}$$

$$\text{High pass: } H(\omega) = \frac{j\omega/\omega_c}{j\omega/\omega_c + 1}$$

Second order (series RLC):

$$\text{Low pass: } H(\omega) = \frac{1}{1 + \frac{1}{Q}\frac{j\omega}{\omega_c} + (j\omega)^2/\omega_c^2}$$

$$\text{High pass: } H(\omega) = \frac{\left(\frac{j\omega}{\omega_c}\right)^2}{1 + \frac{1}{Q}\frac{j\omega}{\omega_c} + (j\omega)^2/\omega_c^2}$$

$$\text{Band pass: } H(\omega) = \frac{\frac{1}{Q}\frac{j\omega}{\omega_c}}{1 + \frac{1}{Q}\frac{j\omega}{\omega_c} + (j\omega)^2/\omega_c^2}$$

$$\text{Band reject: } H(\omega) = \frac{1 + (j\omega)^2/\omega_c^2}{1 + \frac{1}{Q}\frac{j\omega}{\omega_c} + (j\omega)^2/\omega_c^2}$$

- $\omega_c = \sqrt{LC}$
- $Q = \frac{\omega_c L}{R} = \frac{1}{\omega_c RC}$
- Bandwidth = $\frac{\omega_c}{Q}$ for BP and BR.
- Ripple in the pass band when $Q > 0.707$ for LP.



Summary

	Filter type	特征频率 (ω_c)	$ H_R(\omega_c) $
V_R in RC	High-pass	$\frac{1}{RC}$	0.707
V_C in RC	Low-pass	$\frac{1}{RC}$	0.707
V_R in RL	Low-pass	$\frac{R}{L}$	0.707
V_L in RL	High-pass	$\frac{R}{L}$	0.707
V_R in RLC	Band pass	$\frac{1}{\sqrt{LC}}$	1
V_C in RLC	Low-pass	$\frac{1}{\sqrt{LC}}$	Q
V_L in RLC	High-pass	$\frac{1}{\sqrt{LC}}$	Q
V_{LC} in RLC	Band reject	$\frac{1}{\sqrt{LC}}$	0





Outline

- Filter types
- Passive filters: RC, RL, RLC
- Active filters
 - First order active LP/HP filters
 - Cascaded filters
 - Single stage 2nd order filters
- 50 Hz notch filter

Active Filters

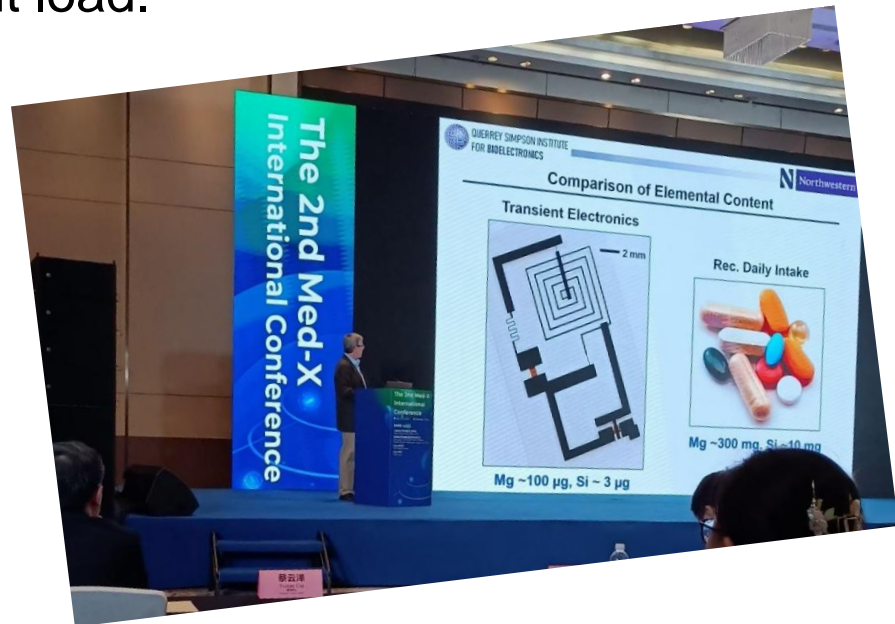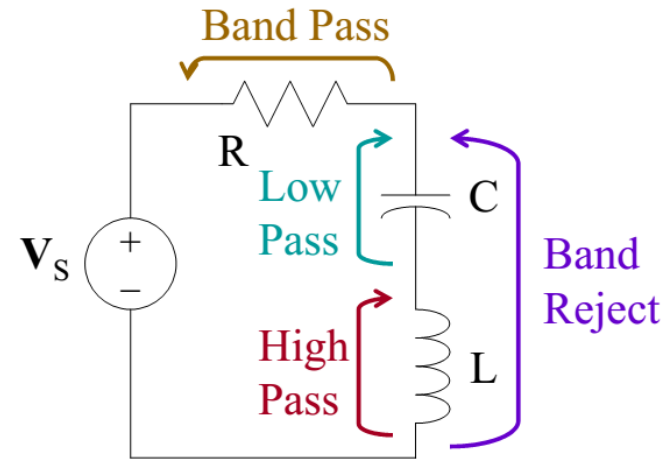- Passive filters have a few drawbacks.
 - Generally, they cannot create gain greater than 1.
 - They require inductors, which tend to be bulky and more expensive than other components.
 - Input load changes with output load.







Active Filters

- It is possible, using op-amps, together with resistors and capacitors, to create all the common filters.
 - Their ability to isolate input and output also makes them very desirable. (V_i load does not change with V_o load)
 - Limited to frequency less than 1MHz.

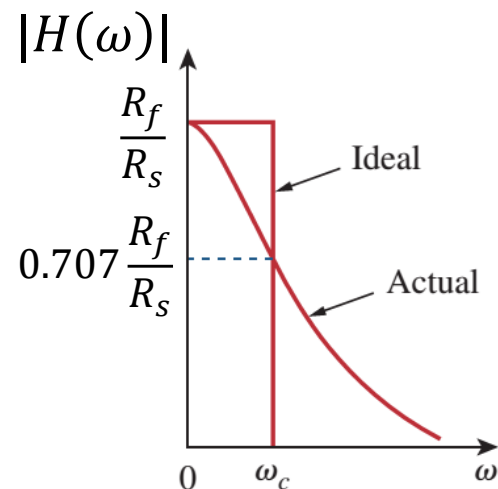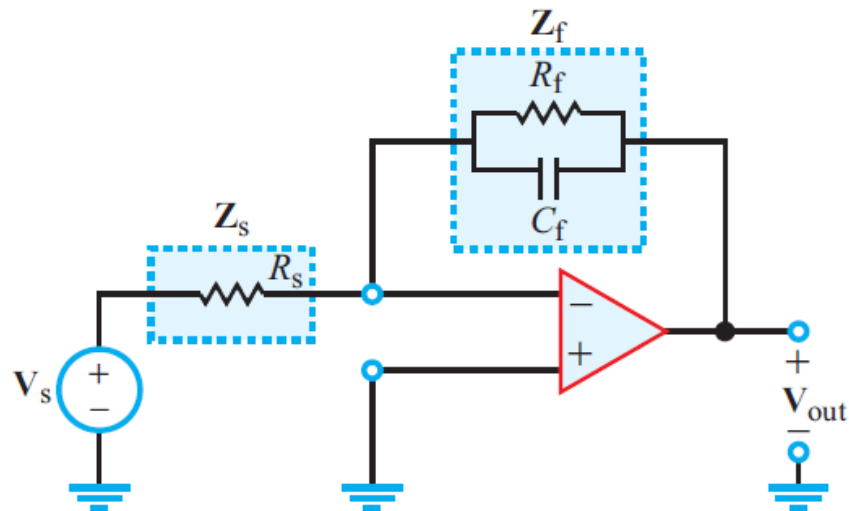
Active 1st-order Low-pass Filter (FB type)



$$H(\omega) = -\frac{Z_f}{Z_s} = -\frac{R_f}{R_s} \frac{1}{1 + j\omega R_f C_f} \quad \omega_c = \frac{1}{R_f C_f}$$

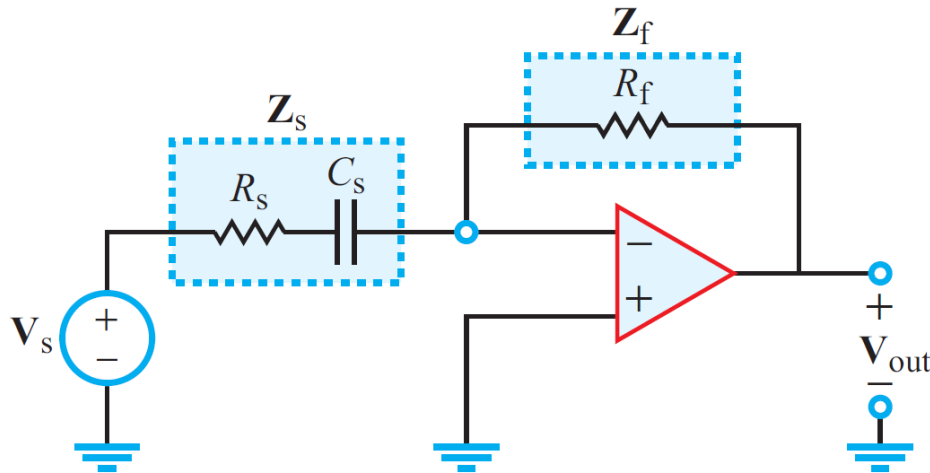Question: What if Z_f and Z_s are switched? Do we get a high-pass filter?


Active 1st-order High-pass Filters (FB type)



$$H(\omega) = -\frac{Z_f}{Z_s} = -\frac{R_f}{R_s + \frac{1}{j\omega C_s}} = -\frac{j\omega R_f C_s}{j\omega R_s C_s + 1} =$$


$$-\frac{R_f}{R_s} \frac{j\omega/\omega_c}{j\omega/\omega_c + 1},$$

where $\omega_c = \frac{1}{R_s C_s}$.

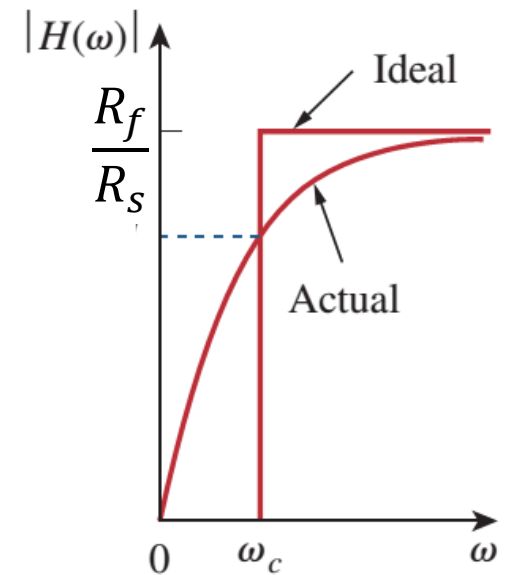

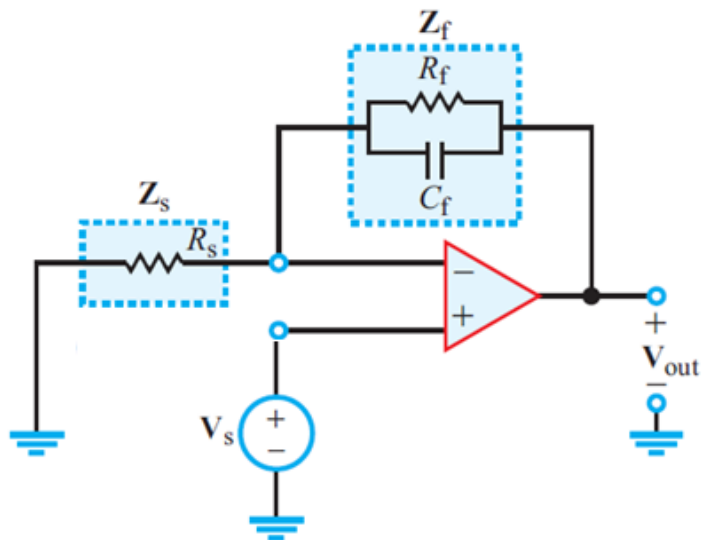Question: What if Z_f and Z_s are switched? Do we get a low-pass filter?

Active 1st-order Low-pass Filters (VCVS type)




$$V_i = \frac{R_s V_o}{R_s + \frac{R_f}{1 + j\omega C_f R_f}}$$

$$H(\omega) = 1 + \frac{R_f/R_s}{1 + j\omega C_f R_f}$$

$$\omega \rightarrow 0 : H(\omega) \rightarrow 1 + R_f/R_s$$

$$\omega \rightarrow \infty : H(\omega) \rightarrow 1$$

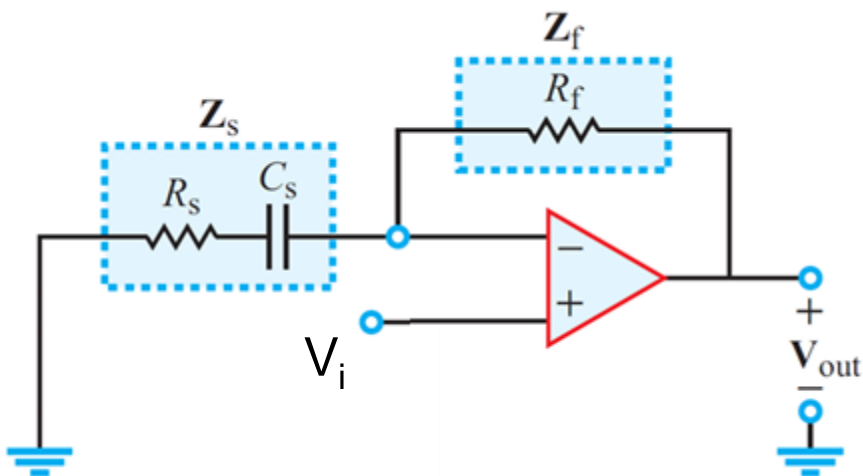Active 1st-order Low-pass Filters (VCVS type)



$$H(\omega) = 1 + \frac{Z_f}{Z_s} = 1 + \frac{R_f}{R_s + \frac{1}{j\omega C_s}} =$$




$$1 + \frac{j\omega R_f C_s}{j\omega R_s C_s + 1} = 1 + \frac{R_f}{R_s} \frac{j\omega/\omega_c}{j\omega/\omega_c + 1},$$

$$\text{where } \omega_c = \frac{1}{R_s C_s}.$$


$$\omega \rightarrow 0 : H(\omega) \rightarrow 1$$

$$\omega \rightarrow \infty : H(\omega) \rightarrow 1 + R_f/R_s$$

Band-pass filter

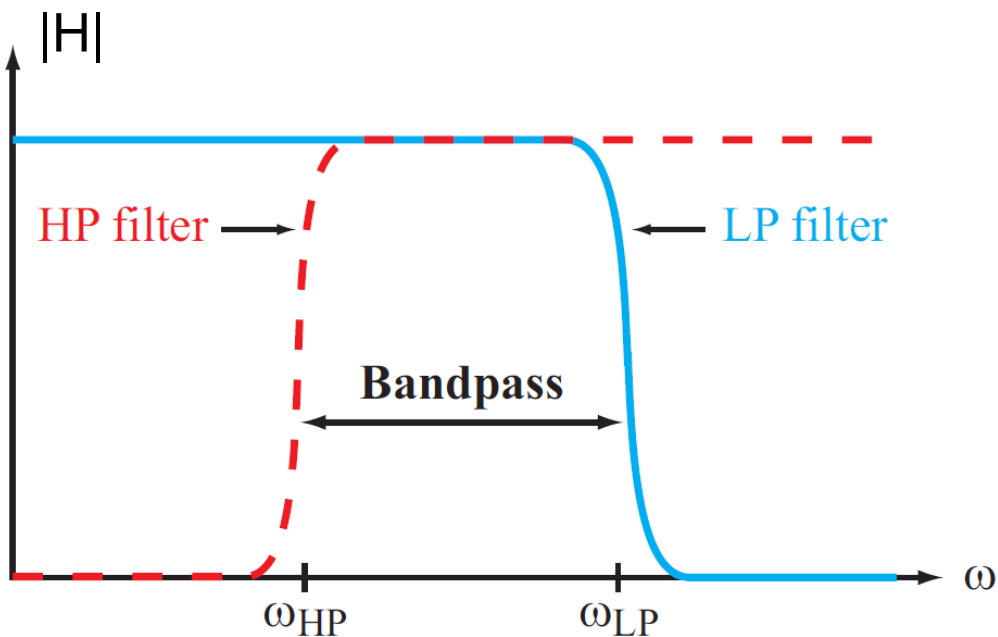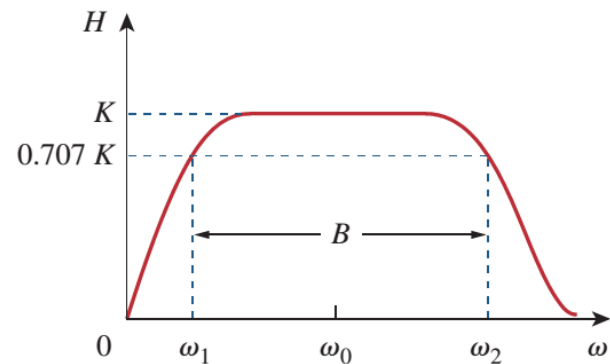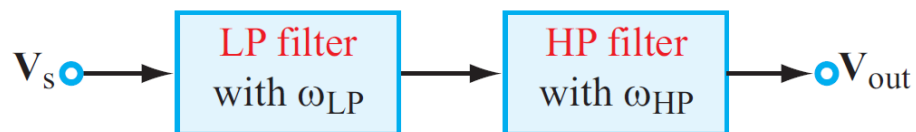


Active Band-pass Filter

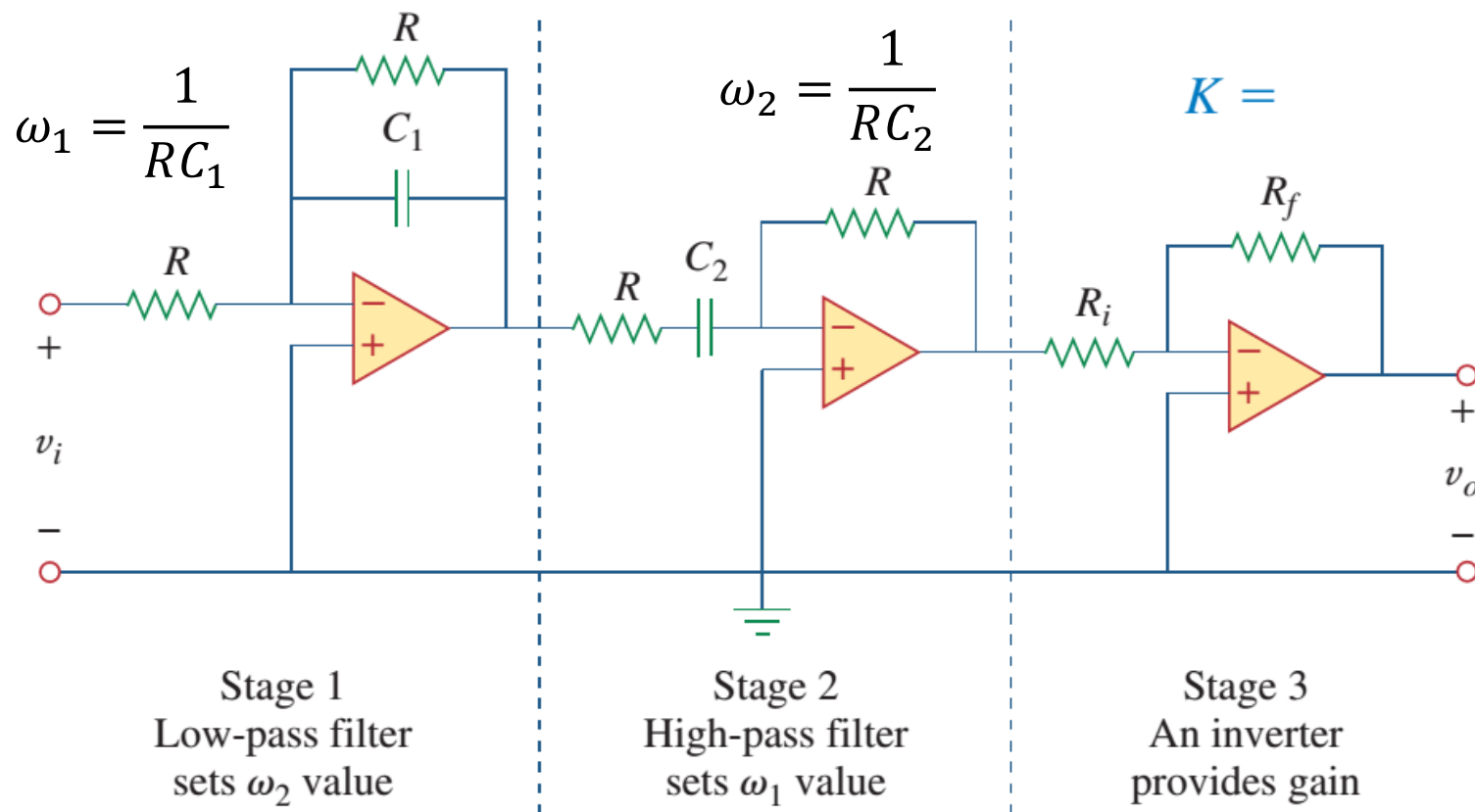

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \left(-\frac{1}{1 + j\omega C_1 R} \right) \left(-\frac{j\omega C_2 R}{1 + j\omega C_2 R} \right) \left(-\frac{R_f}{R_i} \right) \quad \omega_1 > \omega_2$$

Active Band-pass Filter
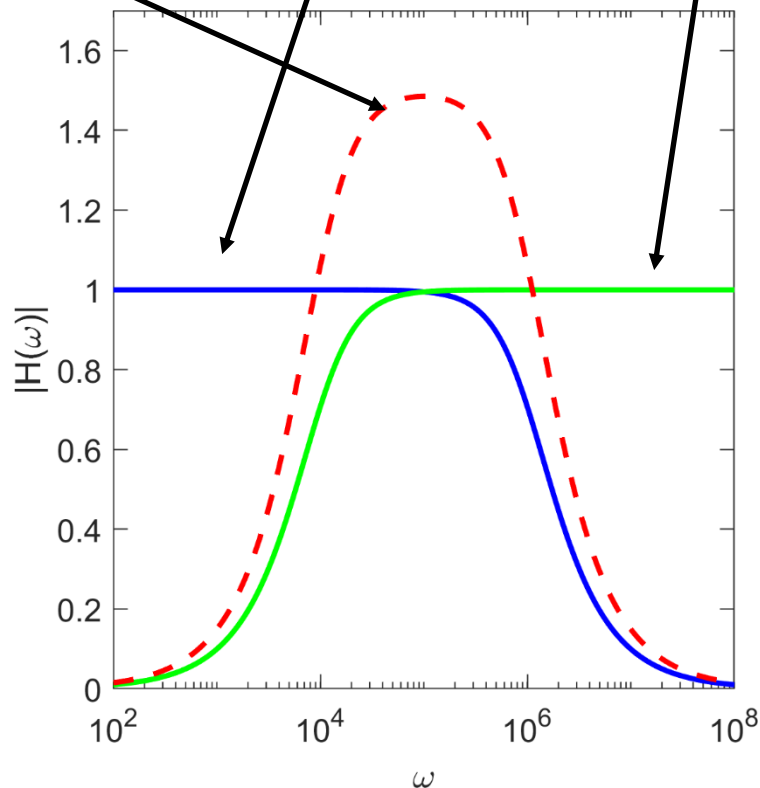
$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \left(-\frac{1}{1 + j\omega C_1 R} \right) \left(-\frac{j\omega C_2 R}{1 + j\omega C_2 R} \right) \left(-\frac{R_f}{R_i} \right)$$



$$R_i = 2 \text{ k}\Omega$$

$$R_f = 3 \text{ k}\Omega$$


$$R = 1 \text{ k}\Omega$$

$$C_1 = 1 \text{ nF}$$


$$C_2 = 100 \text{ nF}$$

Question: Do we get a band reject filter if $C_1 \gg C_2$?


Active Band-reject Filter

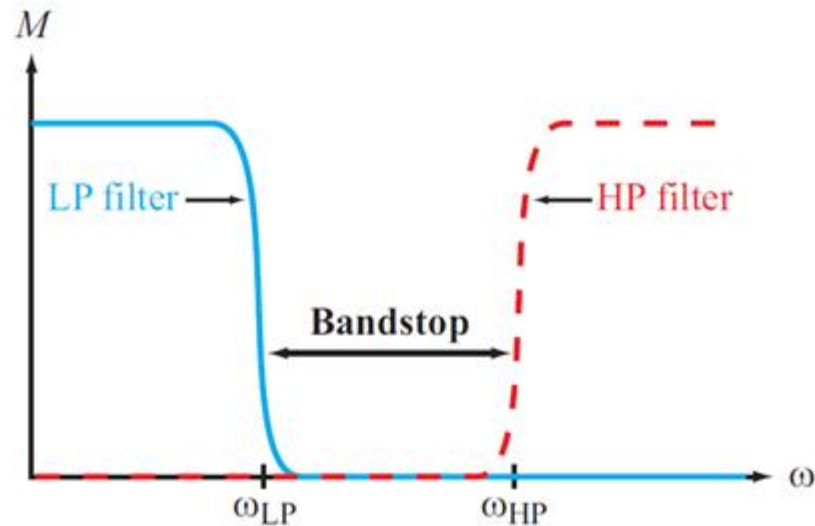

(b) Bandreject filter

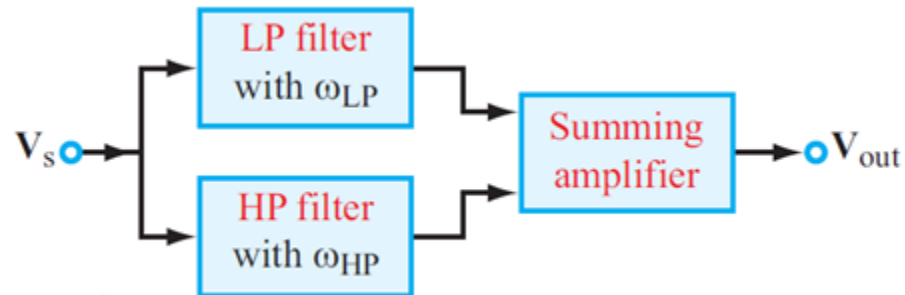

Active Band-reject Filter

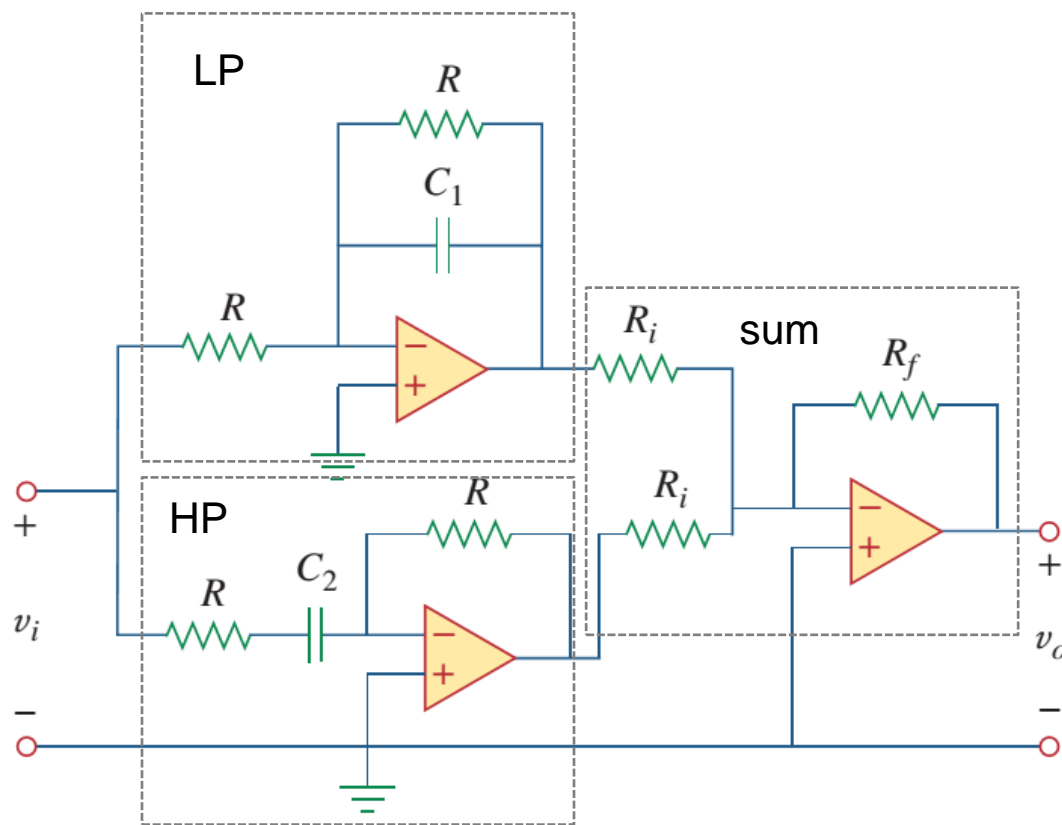

$$H(\omega) = -\frac{R_f}{R_i} \left[-\frac{1}{1 + j\omega RC_1} - \frac{j\omega RC_2}{1 + j\omega RC_2} \right]$$


$$= \frac{R_f}{R_i} \left[\frac{1}{1 + j\omega/\omega_{c1}} + \frac{j\omega/\omega_{c2}}{1 + j\omega/\omega_{c2}} \right]$$

$$\omega_{c1} = \frac{1}{C_1 R}$$

$$\omega_{c2} = \frac{1}{C_2 R}$$

$$\omega_{c1} < \omega_{c2}$$

Active Band-reject Filter

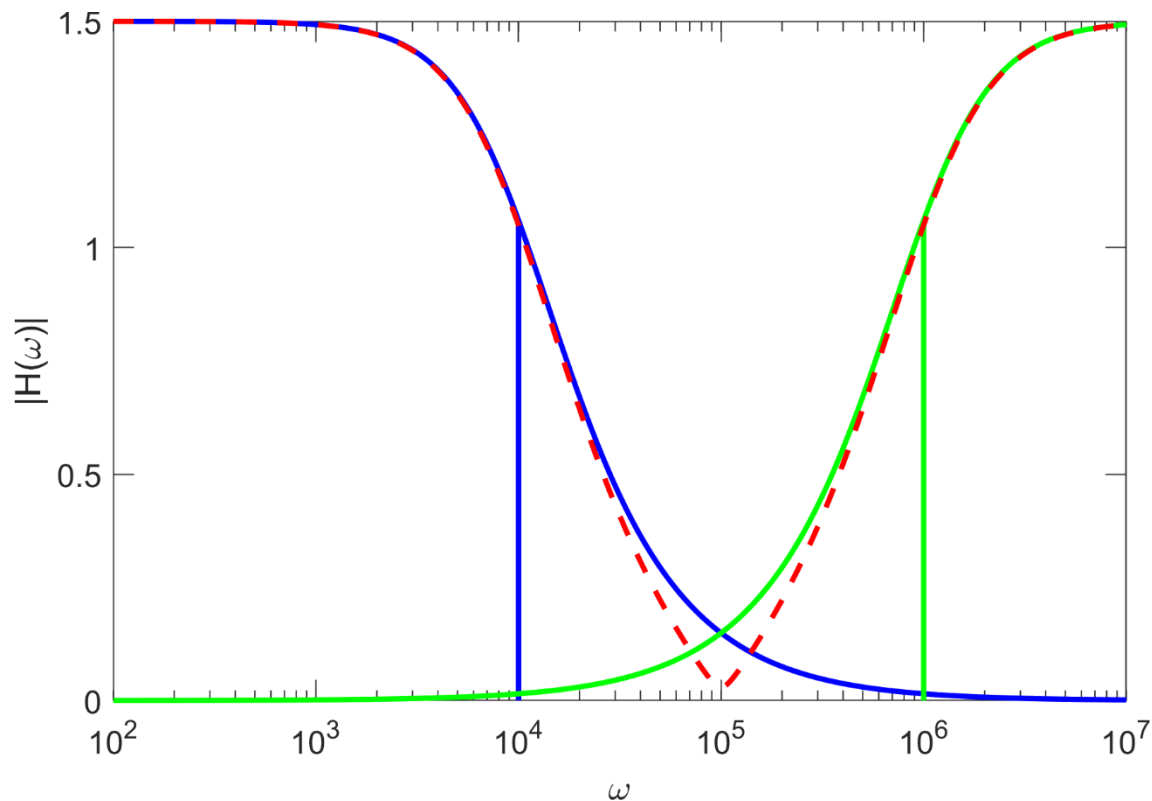

$$R_i = 2 \text{ k}\Omega$$


$$R_f = 3 \text{ k}\Omega$$

$$R = 1 \text{ k}\Omega$$

$$C_1 = 100 \text{ nF}$$

$$C_2 = 1 \text{ nF}$$

电压控制电压源型滤波器

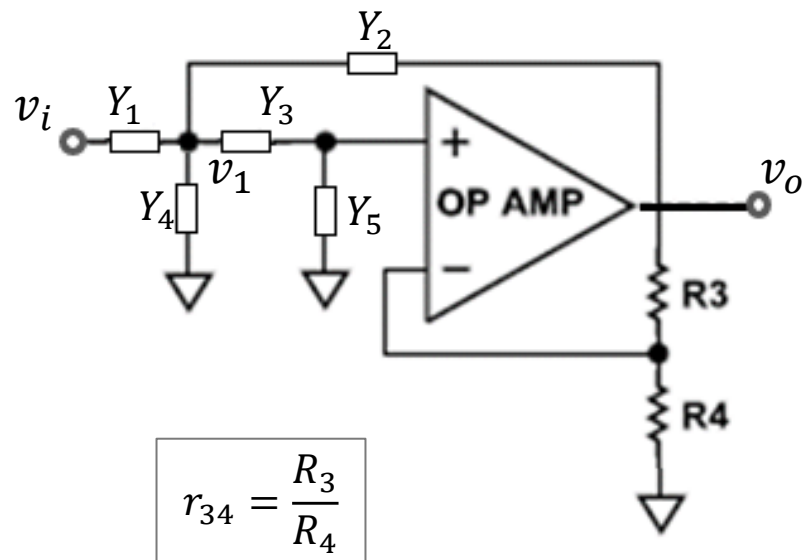

When $Y_4 = 0$, the structure is called Sallen-Key filter (proposed in 1955) .

$$\frac{1}{r_{34} + 1} v_0 = \frac{Y_3 v_1}{Y_3 + Y_5}$$



$$Y_1 v_i + Y_2 v_o + Y_3 \frac{v_0}{r_{34} + 1} - v_1 (Y_1 + Y_2 + Y_3 + Y_4) = 0$$

$$Y_1 v_i + Y_2 v_o + Y_3 \frac{v_0}{r_{34} + 1} - \frac{(Y_3 + Y_5)(Y_1 + Y_2 + Y_3 + Y_4)}{Y_3(r_{34} + 1)} v_0 = 0$$

$$\frac{v_0}{v_i} = \frac{Y_1 Y_3 (r_{34} + 1)}{Y_3 (Y_1 + Y_4 - r_{34} Y_2) + Y_5 (Y_1 + Y_2 + Y_3 + Y_4)}$$

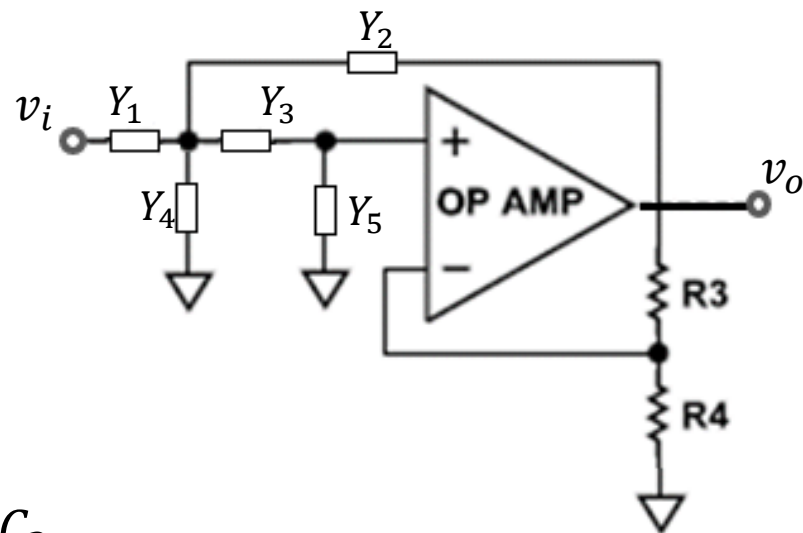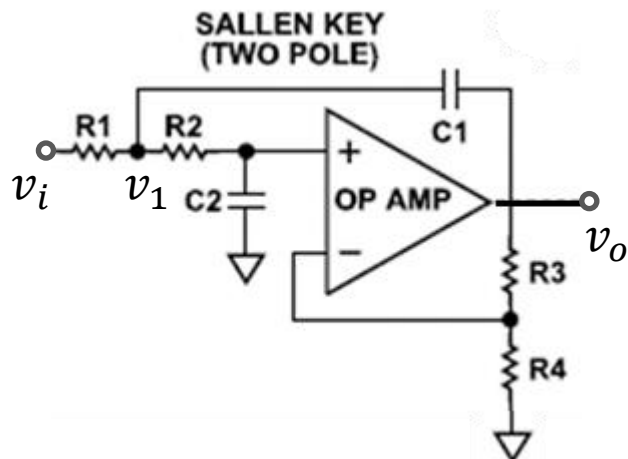Exercise

Find the frequency response of the following circuit.





$$Y_1 = \frac{1}{R_1}, Y_2 = j\omega C_1, Y_3 = \frac{1}{R_2}, Y_4 = 0, Y_5 = j\omega C_2$$

$$\begin{aligned} \frac{v_o}{v_i} &= \frac{Y_1 Y_3 (r_{34} + 1)}{Y_3 (Y_1 + Y_4 - r_{34} Y_2) + Y_5 (Y_1 + Y_2 + Y_3 + Y_4)} \\ &= \frac{r_{34} + 1}{1 + \alpha \left(\frac{j\omega}{\omega_0} \right) + \left(\frac{j\omega}{\omega_0} \right)^2} \end{aligned}$$

$$\begin{aligned} r_{34} &= \frac{R_3}{R_4}, \quad \omega_0 = \frac{1}{\sqrt{C_1 C_2 R_1 R_2}} \\ \alpha \omega_0 &= \left[\frac{1}{C_1} \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - \frac{r_{34}}{R_2 C_2} \right] \end{aligned}$$

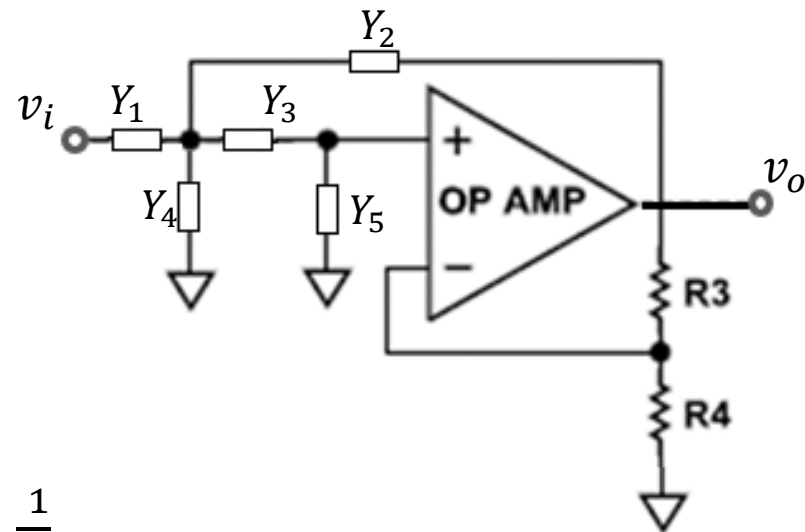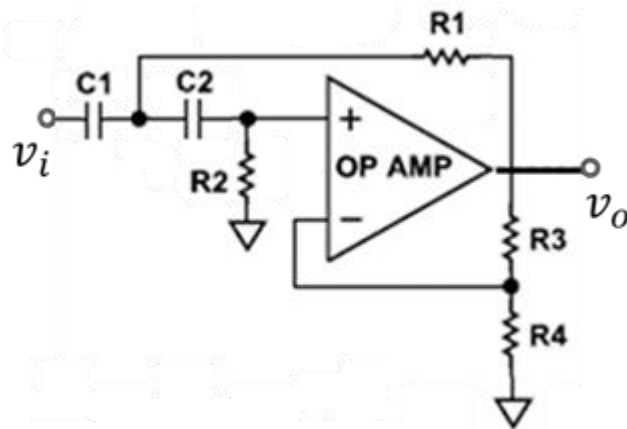Exercise II

Find the frequency response of the following circuit.





$$Y_1 = j\omega C_1, Y_2 = \frac{1}{R_1}, Y_3 = j\omega C_2, Y_4 = 0, Y_5 = \frac{1}{R_2}$$

$$\begin{aligned} \frac{v_o}{v_i} &= \frac{Y_1 Y_3 (r_{34} + 1)}{Y_3 (Y_1 + Y_4 - r_{34} Y_2) + Y_5 (Y_1 + Y_2 + Y_3 + Y_4)} \\ &= \frac{(r_{34} + 1) (j\omega / \omega_0)^2}{(j\omega / \omega_0)^2 + \alpha j\omega / \omega_0 + 1} \end{aligned}$$

$$\begin{aligned} r_{34} &= \frac{R_3}{R_4}, \omega_0 = \frac{1}{\sqrt{C_1 C_2 R_1 R_2}} \\ \alpha \omega_0 &= \left[\frac{1}{R_2} \left(\frac{1}{C_1} + \frac{1}{C_2} \right) - \frac{r_{34}}{R_1 C_1} \right] \end{aligned}$$

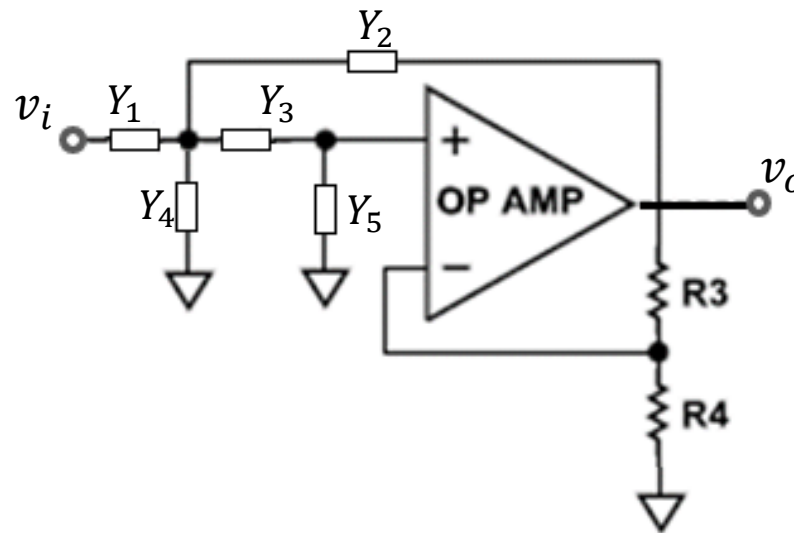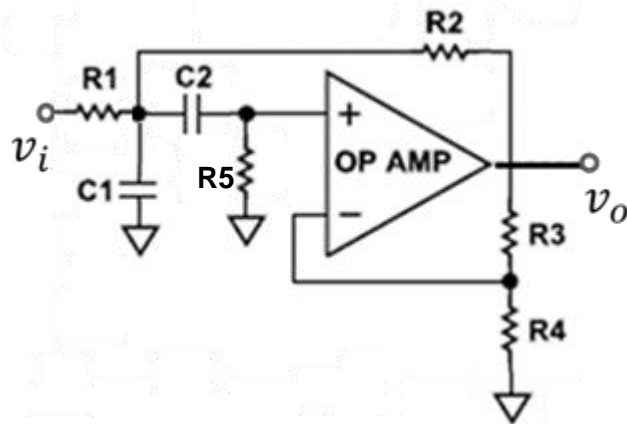Exercise III

Find the frequency response of the following circuit.







Outline

- Filter types
- Passive filters: RC, RL, RLC
- Active filters
- 50 Hz notch filter

50 Hz 陷波器

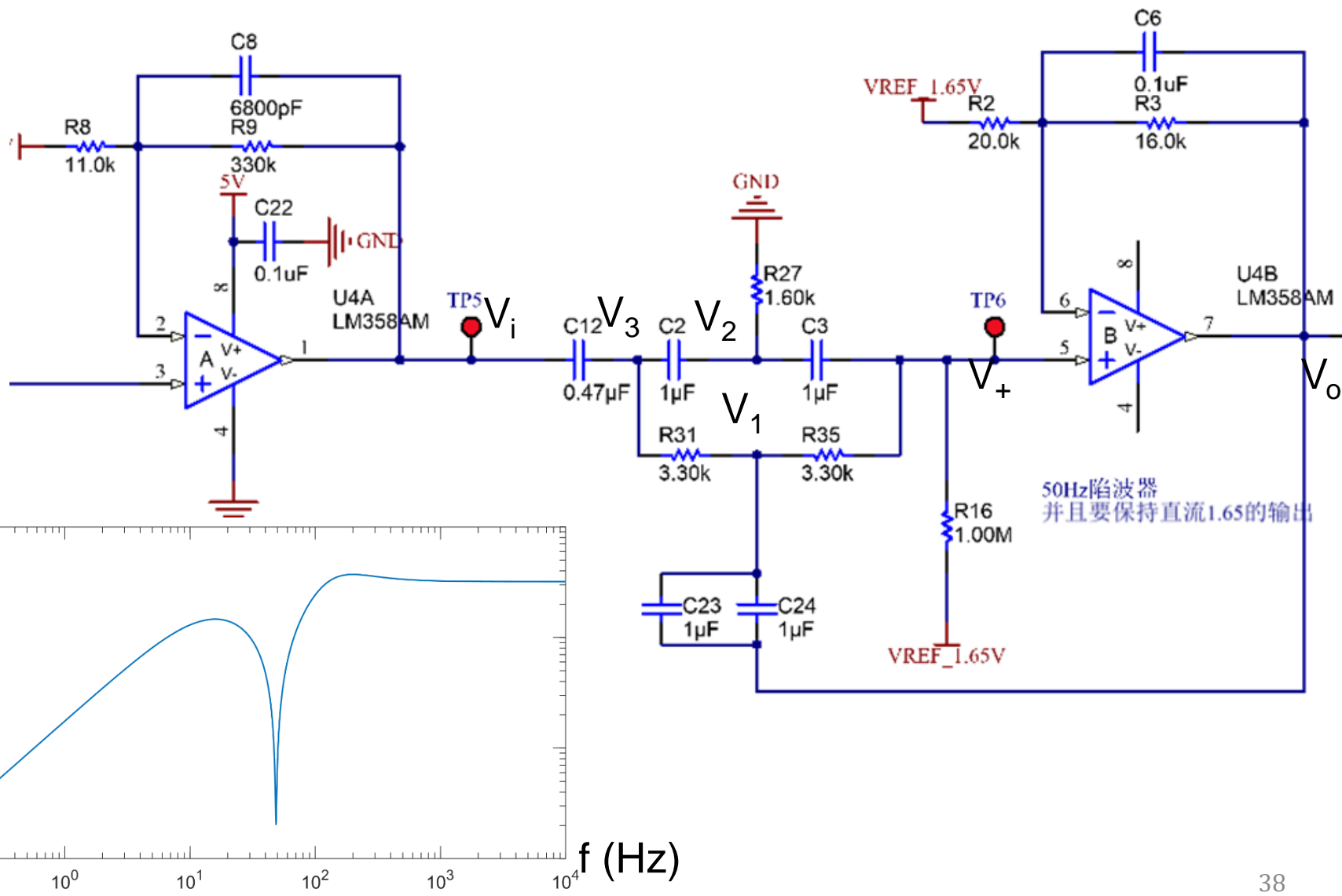

Exercise: find the frequency at the dip.

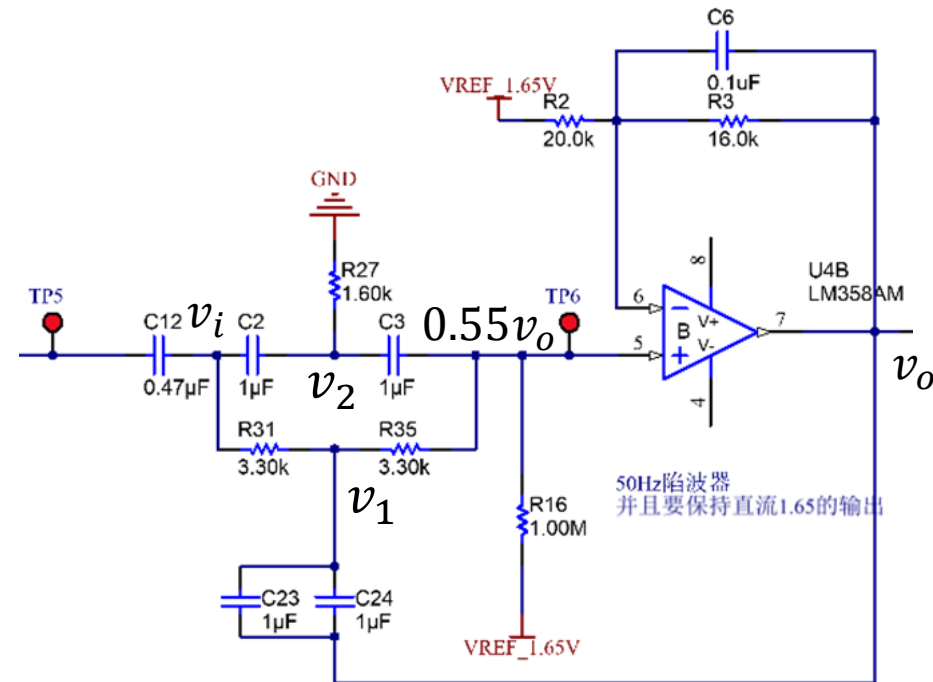

$$v_1 = \frac{j\omega 2C_{23}v_o + \frac{v_i + 0.55v_o}{R_{31}}}{j\omega 2C_{23} + 2/R_{31}}$$

$$v_2 = \frac{(v_i + 0.55v_o)j\omega C_3}{j\omega 2C_3 + 1/R_{27}}$$

$$(v_1 - 0.55v_o) \frac{1}{R_{31}} = (0.55v_o - v_2)j\omega C_3$$

$$\begin{aligned} H(\omega) &= - \frac{\frac{1}{j\omega 2R_{31}C_{23} + 2} + \frac{(j\omega C_3)^2 R_{31}R_{27}}{j\omega 2R_{27}C_3 + 1}}{\frac{j\omega 2R_{31}C_{23} + 0.55}{j\omega 2R_{31}C_{23} + 2} - 0.55 - 0.55j\omega C_3R_{31}} \\ &= - \frac{1 + \frac{(j\omega C_3)^2 R_{31}R_{27}(j2\omega R_{31}C_{23} + 2)}{j2\omega R_{27}C_3 + 1}}{j\omega 2R_{31}C_{23} + 0.55 - 1.1(1 + j\omega C_3R_{31})(1 + j\omega C_{23}R_{31})} \end{aligned}$$



$$H(\omega) = - \frac{1 + \frac{(j\omega C_3)^2 R_{31} R_{27} (j2\omega R_{31} C_{23} + 2)}{j2\omega R_{27} C_3 + 1}}{j\omega 2R_{31} C_{23} + 0.55 - 1.1(1 + j\omega C_3 R_{31})(1 + j\omega C_{23} R_{31})}$$

When $\frac{j\omega R_{31} C_{23} + 1}{j2\omega R_{27} C_3 + 1} = 1$ and $\omega = \frac{1}{C_3 \sqrt{2R_{31} R_{27}}}$, $H(\omega) = 0$.


$\frac{j\omega R_{31} C_{23} + 1}{j2\omega R_{27} C_3 + 1} = 1 \rightarrow R_{31} C_{23} = 2R_{27} C_3$, which is roughly satisfied in the circuit.

$$\omega_c = \frac{1}{C_3 \sqrt{2R_{31} R_{27}}} = 307.7 \text{ rad/s}$$

$$f_c = \frac{\omega}{2\pi} = 49 \text{ Hz}$$

$$\begin{aligned} H(\omega) &= \frac{1}{0.55} \frac{1 + 2(j\omega C_3)^2 R_{31} R_{27}}{1 + j\omega R_{31} (1.1C_3 - 0.9C_{23})/0.55 + 2(j\omega)^2 C_3 C_{23} R_{31}^2} \\ &= 1.82 \frac{1 + (j\omega/\omega_c)^2}{1 + j\omega R_{31} (1.1C_3 - 0.9C_{23})/0.55 + 2(j\omega/\omega_c)^2} \end{aligned}$$


Summary (Active filters)

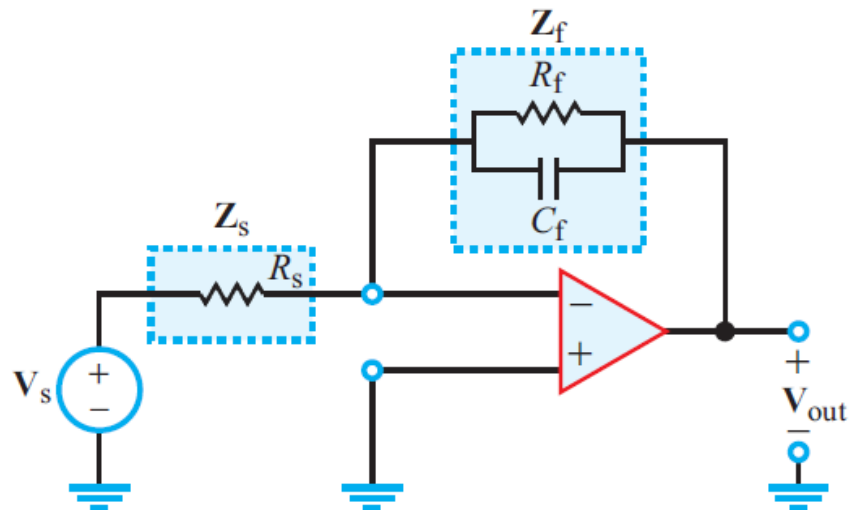

Low pass

$$H(\omega) = -\frac{Z_f}{Z_s} = -\frac{R_f}{R_s} \frac{1}{1 + j\omega R_f C_f}$$


$$\omega_c = \frac{1}{R_f C_f}$$

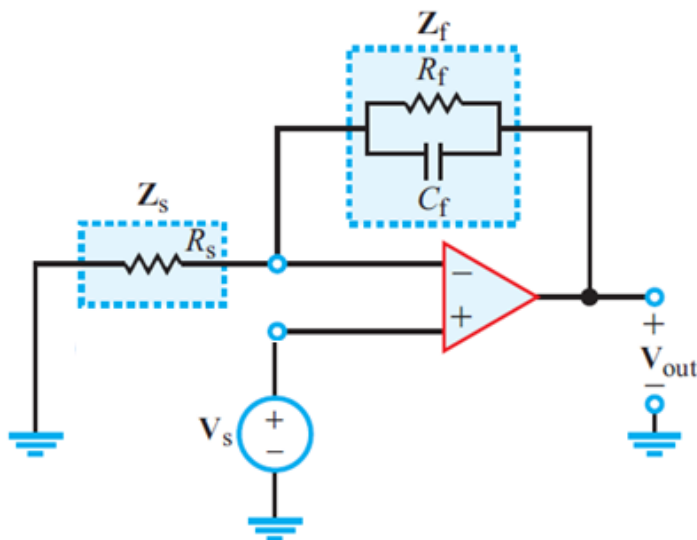


$$H(\omega) = 1 + \frac{R_f/R_s}{1 + j\omega/\omega_c}$$

Summary (Active filters)

High pass

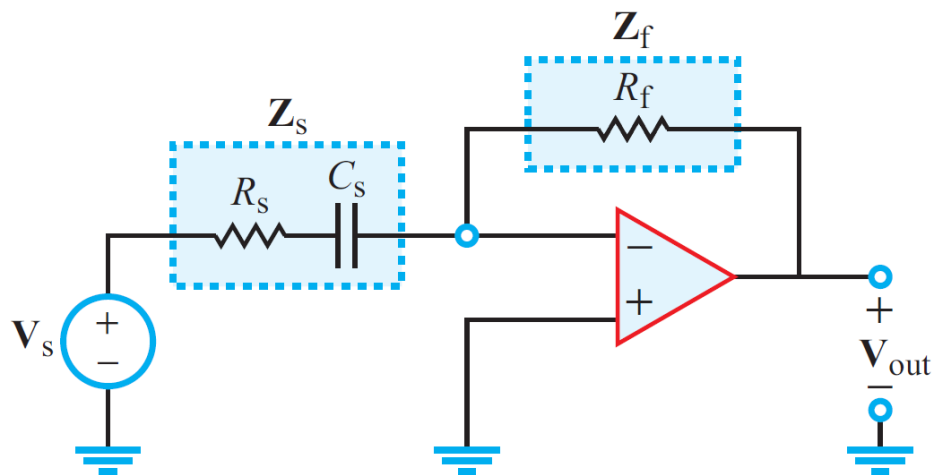

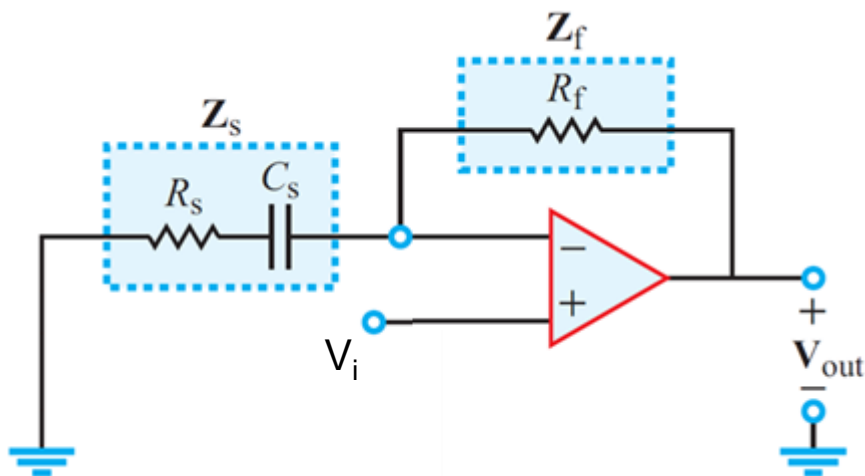
$$H(\omega) = -\frac{R_f}{R_s} \frac{j\omega/\omega_c}{j\omega/\omega_c + 1},$$



$$H(\omega) = 1 + \frac{R_f}{R_s} \frac{j\omega/\omega_c}{j\omega/\omega_c + 1}$$

$$\omega_c = \frac{1}{R_s C_s}$$

Summary (Active filters)

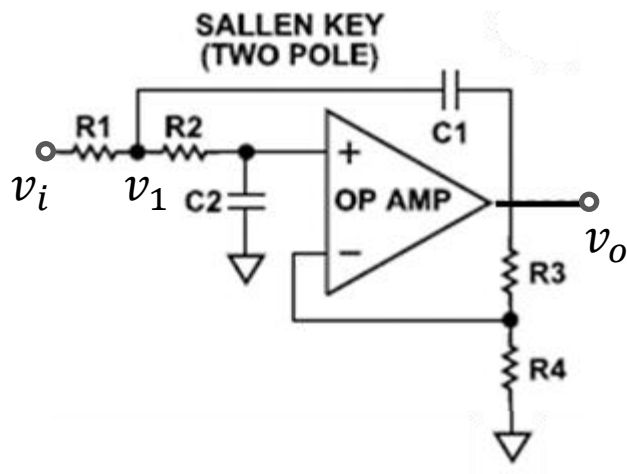


$$H(\omega) = \frac{r_{34} + 1}{1 + 1/Q \left(\frac{j\omega}{\omega_0} \right) + \left(\frac{j\omega}{\omega_0} \right)^2}$$

$$r_{34} = \frac{R_3}{R_4}, \quad \omega_0 = \frac{1}{\sqrt{C_1 C_2 R_1 R_2}}$$

$$Q = \frac{\sqrt{C_1 C_2 R_1 R_2}}{C_2(R_2 + R_1) - R_1 C_1 r_{34}}$$

No ripple in the pass band when $Q < 0.707$.

Summary (Active filters)

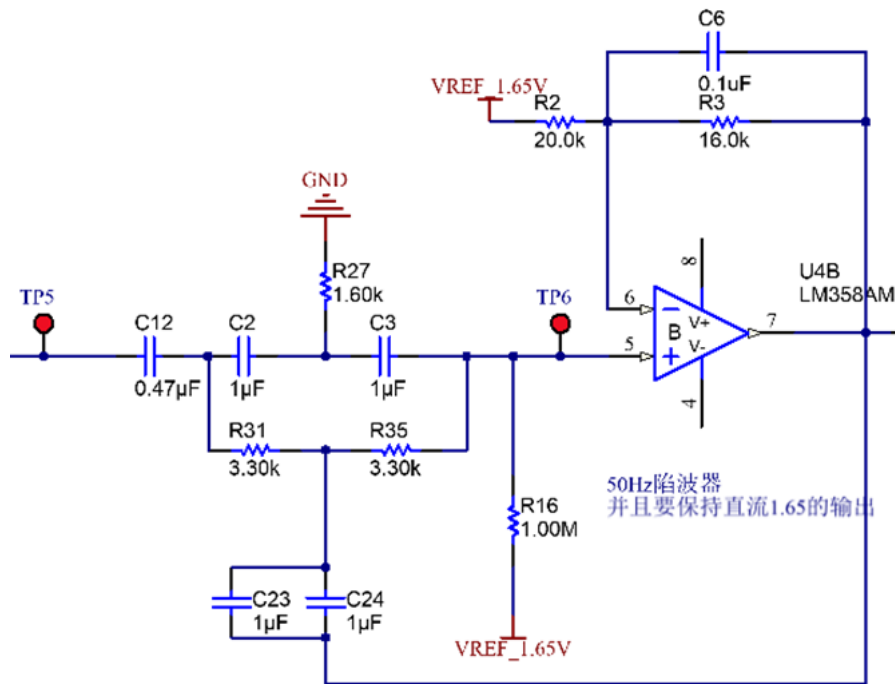

Band reject ($H(\omega) = 0$)
condition: $R_{31}C_{23} = 2R_{27}C_3$

$$\omega_c = \frac{1}{C_3 \sqrt{2R_{31}R_{27}}} = 307.7 \text{ rad/s}$$

$$f_c = \frac{\omega}{2\pi} = 49 \text{ Hz}$$