



# 第六章 一阶电路




# 大纲


- 电容与电感
- 一阶电路方程和求解
- 一阶电路实例分析
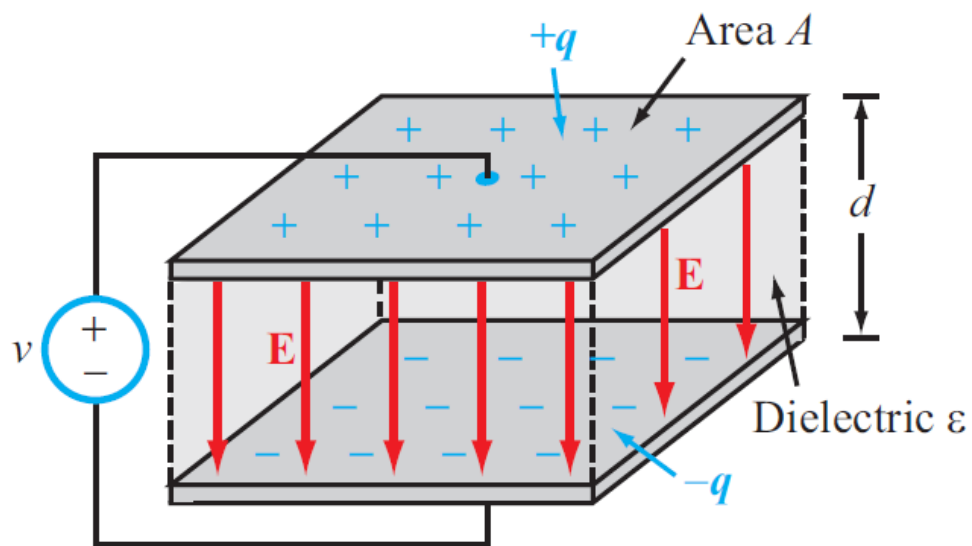
# Capacitors

An element that stores energy in electric field



Parallel plate capacitor

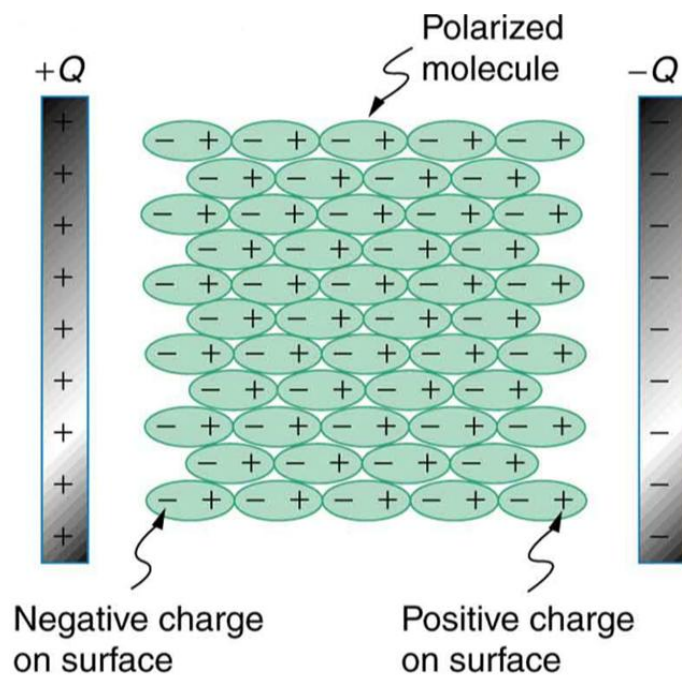



## 平板电容器公式

$$\text{电场 } E = \frac{\text{电荷面密度}}{\varepsilon_0} = \frac{\text{自由电荷面密度}}{\varepsilon}$$

$\varepsilon_0$ : 真空介电常数 ( $8.85 \times 10^{-12} \text{ F/m}$ ) ;  $\varepsilon$ : 介质的介电常数

$$\text{自由电荷 } Q = \text{自由电荷面密度} \times \text{面积} = \varepsilon A E$$

$$\text{电压} = \text{电场对路径的积分}: V = E d$$


$$\text{电容 } C = \frac{Q}{V} = \frac{\varepsilon A E}{E d} = \frac{\varepsilon A}{d}$$

$$\text{自由电荷 } Q = C V = \varepsilon A E$$

$$\text{Energy} = \int_0^Q V dq = \int_0^Q \frac{q}{C} dq = \frac{Q^2}{2C} = \frac{C V^2}{2}$$
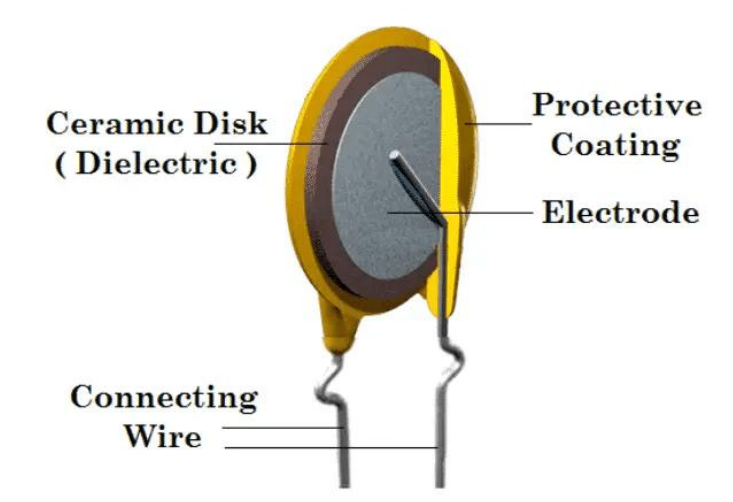
## Practice

- What is the capacitance of a capacitor with diameter of 4 mm, electrode distance of 1 mm;  $\varepsilon = 100 \varepsilon_0$ ?





$$\frac{100 \times 8.85 \text{ F/m} \times 10^{-12} \pi (0.002 \text{ m})^2}{0.001 \text{ m}} = 11.1 \text{ pF}$$


What is the energy stored in the capacitor when the voltage is 5 V?

$$\frac{11.1 \cdot 10^{-12} \text{ F} \cdot 25 \text{ V}^2}{2} = 0.139 \text{ nJ}$$

# Capacitor Response

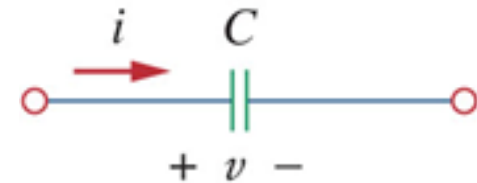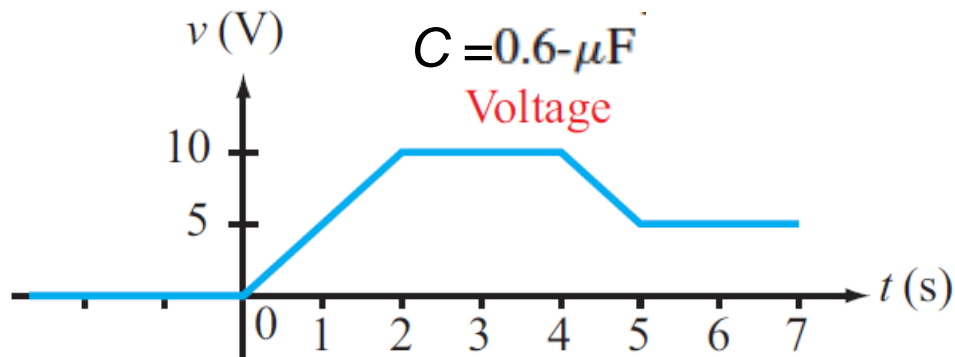


$$I = \frac{dQ}{dt} = C \frac{dV}{dt}$$


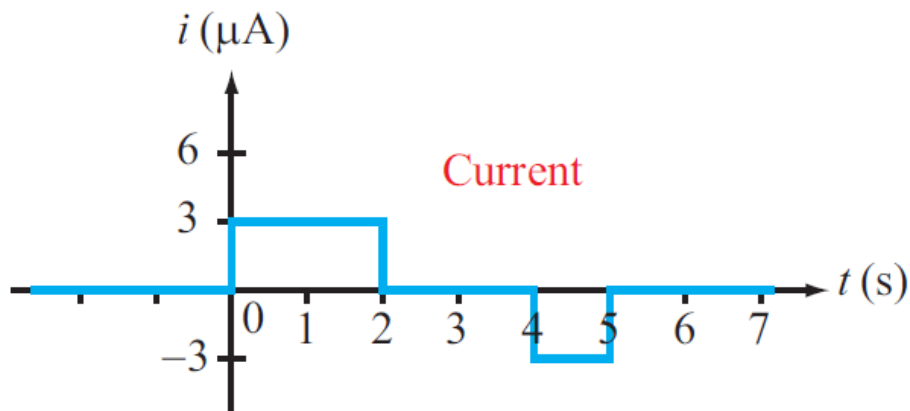


# Capacitor Response

$$C = 0.6\text{-}\mu\text{F}$$

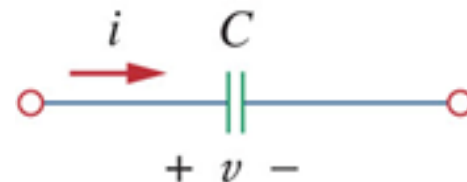



$$I = \frac{dQ}{dt} = C \frac{dV}{dt}$$

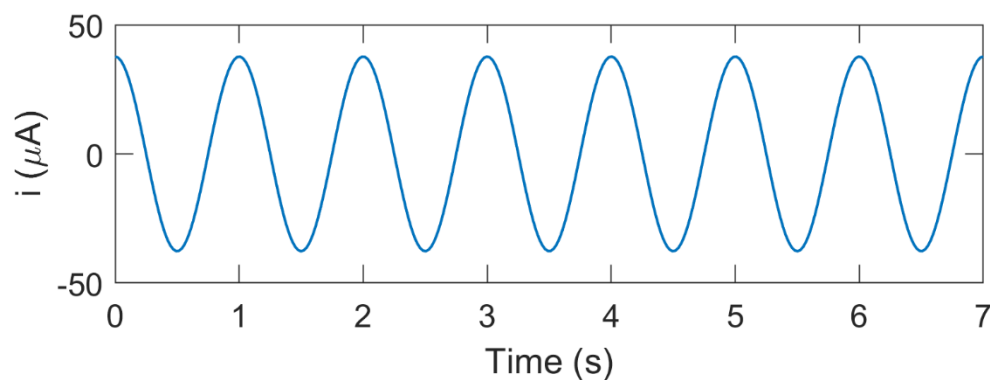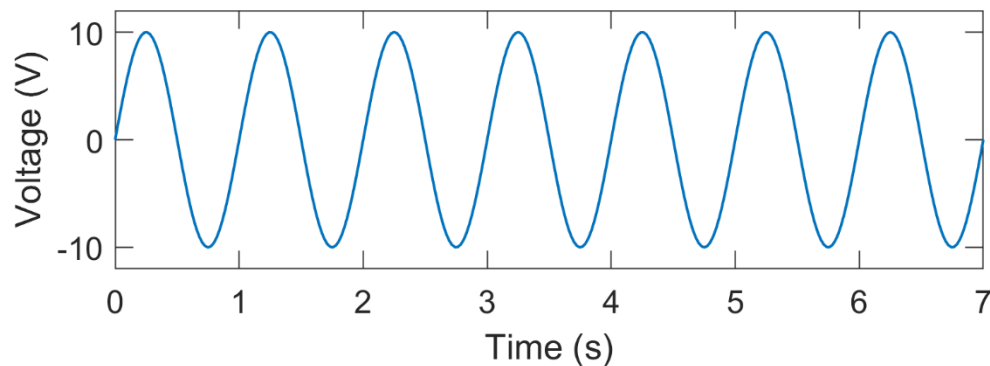

$$\text{Amplitude} = 2\pi C 10 = 37.7\text{ }\mu\text{A}$$

# Capacitors in Series

## Combining In-Series Capacitors

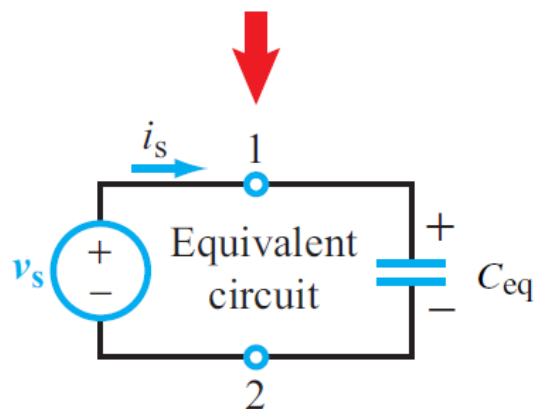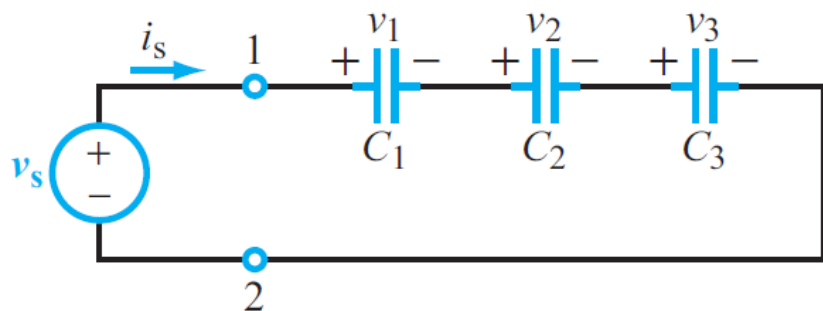

$$I = C_1 \frac{dV_1}{dt} = C_2 \frac{dV_2}{dt} = C_3 \frac{dV_3}{dt}$$

$$I = C_{eq} \frac{dV}{dt} = C_{eq} \frac{d(V_1 + V_2 + V_3)}{dt}$$


$$= C_{eq} \left( \frac{I}{C_1} + \frac{I}{C_2} + \frac{I}{C_3} \right)$$

$$C_{eq} = \left( \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)^{-1}$$

与并联电阻的等效电阻公式类似。



## 稳态时各电容的分压

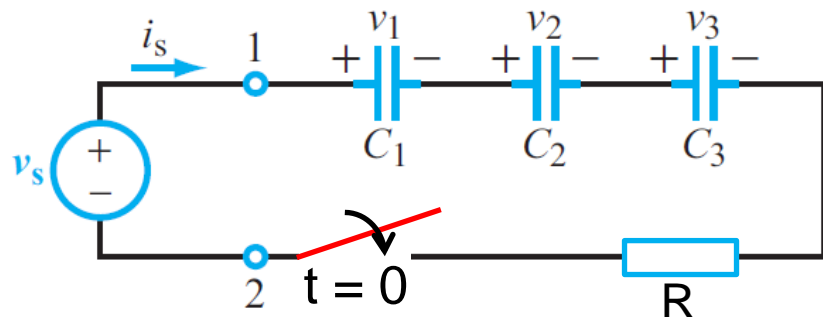

假设连接电源之前各电容所存储的电荷为0, 求当开关闭合且达到稳态时各电容的电压。

$$C_1 v_1 - C_2 v_2 = 0 \quad (2)$$

$$C_2 v_2 - C_3 v_3 = 0 \quad (3)$$

$$\text{KVL: } v_s = v_1 + v_2 + v_3 \quad (1)$$

方程(1)-(3)联立可得,

$$\text{KCL: } C_1 \frac{dv_1}{dt} = C_2 \frac{dv_2}{dt} = C_3 \frac{dv_3}{dt}$$

$$\frac{d(C_1 v_1 - C_2 v_2)}{dt} = 0$$

$$\frac{d(C_2 v_2 - C_3 v_3)}{dt} = 0$$

$$v_1 = \frac{v_s C_2 C_3}{C_1 C_2 + C_1 C_3 + C_2 C_3} = v_s \frac{\frac{1}{C_1}}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}}$$


$$v_2 = \frac{v_s C_1 C_3}{C_1 C_2 + C_1 C_3 + C_2 C_3}$$

$$v_3 = \frac{v_s C_1 C_2}{C_1 C_2 + C_1 C_3 + C_2 C_3}$$

因此,  $C_1 v_1 - C_2 v_2$  和  $C_2 v_2 - C_3 v_3$  不随时间变化。

串联电容的分压公式和并联电阻的分流公式类似。


# Capacitors in Parallel

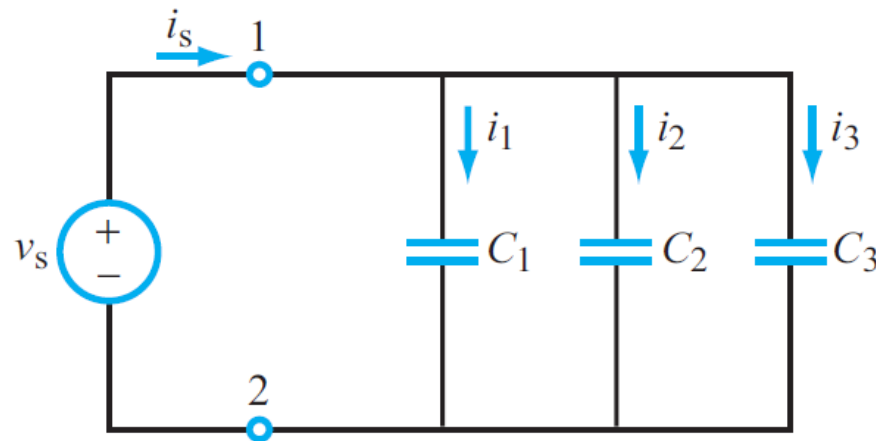


$$\begin{aligned} I &= \left[ C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + C_3 \frac{dv}{dt} \right] \\ &= (C_1 + C_2 + C_3) \frac{dv}{dt} \\ &= C_{\text{eff}} \frac{dv}{dt} \end{aligned}$$

$$C_{\text{eq}} = C_1 + C_2 + C_3$$

与串联电阻的等效电阻公式相同

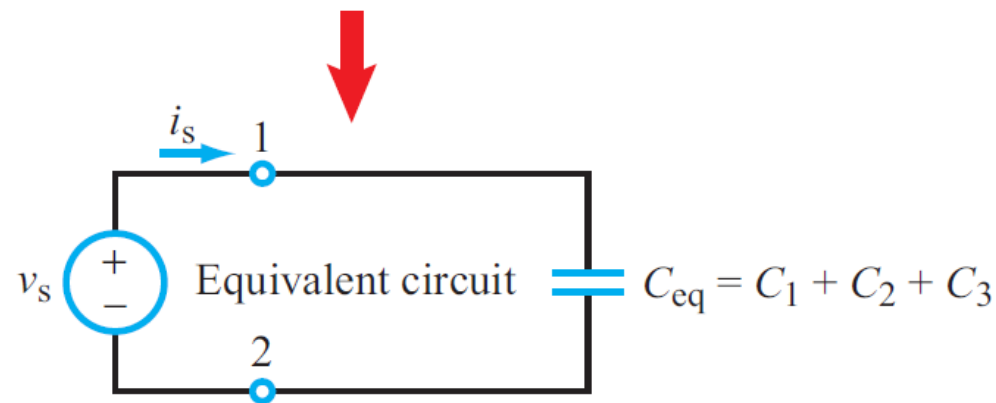

# Capacitors in Parallel

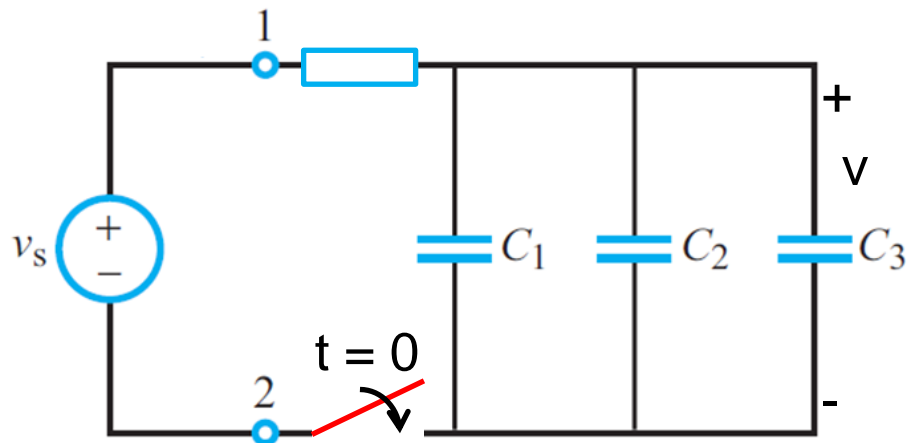

求当开关闭合且达到稳态时各电容的所存储的电荷。

因为电容并联，它们两端的电压相等且均为 $v_s$ 。

$$Q_1 = v_s C_1$$

$$Q_2 = v_s C_2$$

$$Q_3 = v_s C_3$$




## 电路的动态响应

- 当电路的结构或内部元件特性发生改变时，电路的瞬态响应可分解为自然响应和稳态值之和（线性系统的可叠加性）
- 自然响应描述电路中不存在电源时的动态变化过程，电压电流值在 $t \rightarrow \infty$ 时趋向0。
- 稳态值对应应在电源作用下电路的最终状态。
- 稳态时流过电容器的电流为0（开路）。



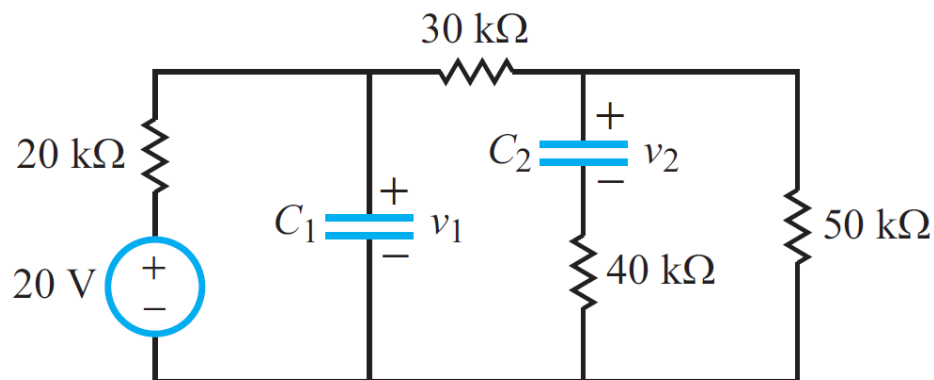
## Exercise

Find the voltages across  $C_1$  and  $C_2$  at steady state.




Equivalent circuit at steady state

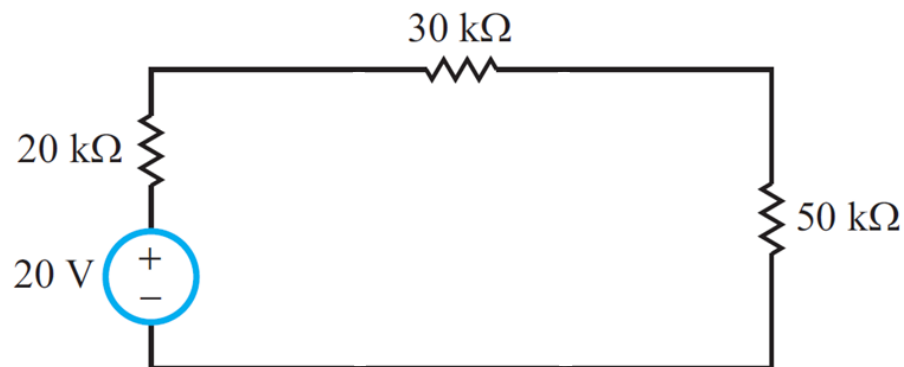

$$V_1 = 16 \text{ V}; V_2 = 10 \text{ V};$$
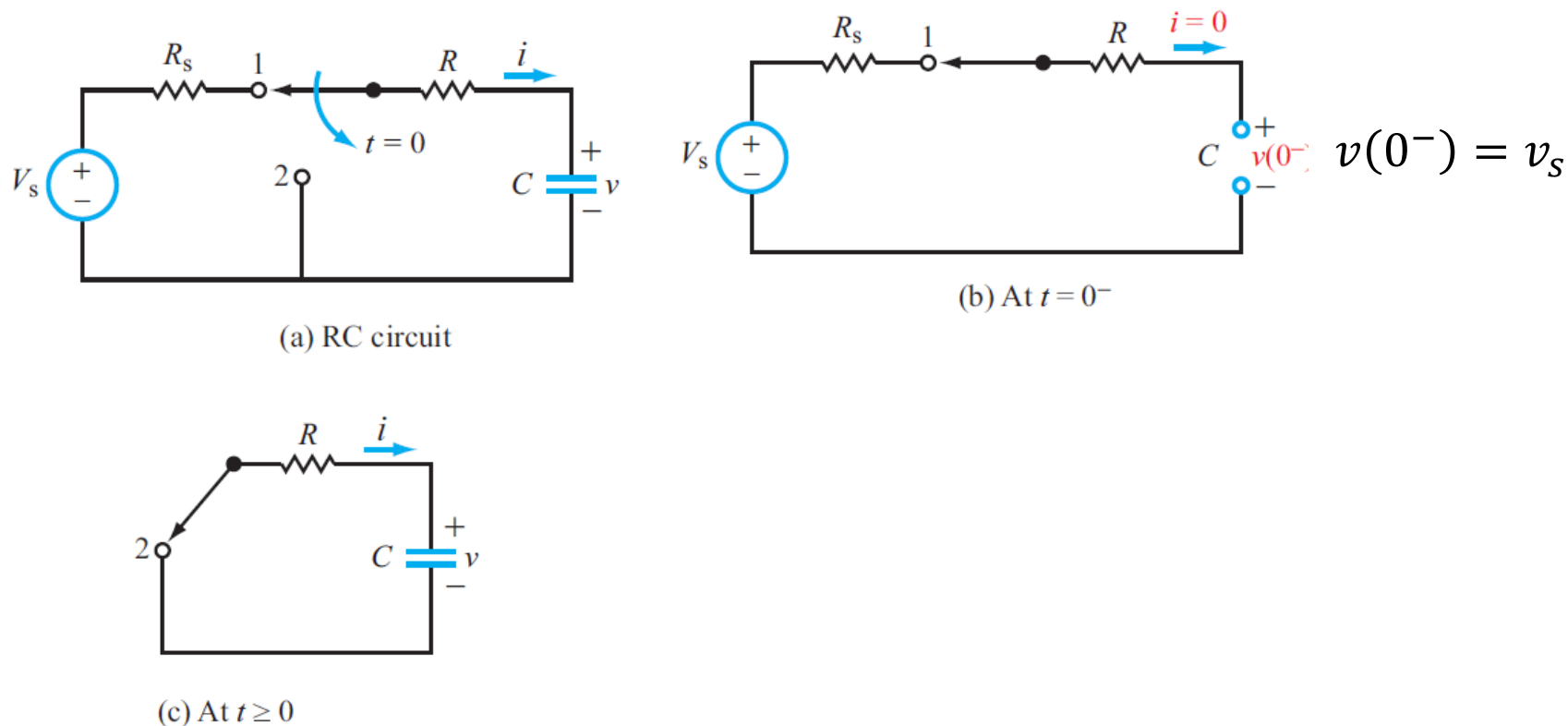
# 自然响应


**Natural response:** The behavior (in terms of voltage and current) of the circuit itself, with no external sources of excitation.






# RC电路的自然响应

电压响应

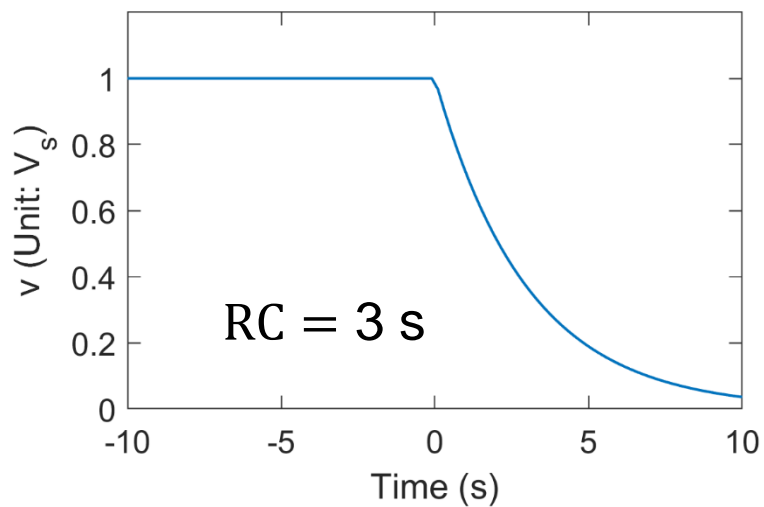

连续

电流响应

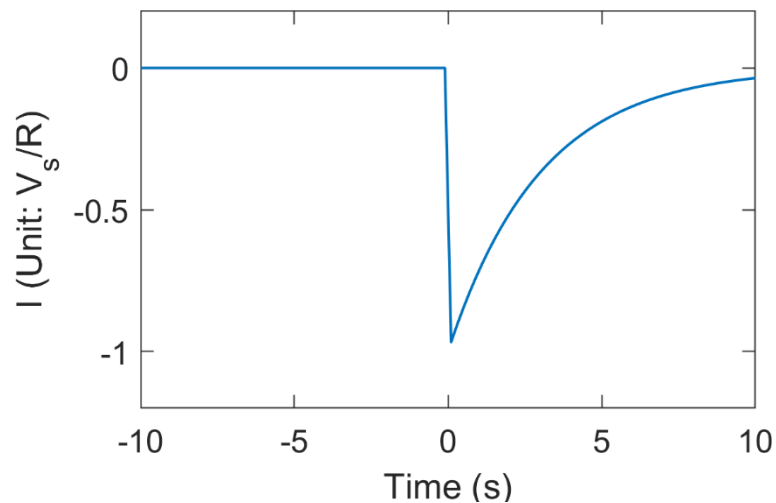

不连续



# 电容电压电流的瞬时变化特性

- 电容的电压具有时间连续性


$$v(0^+) = v(0^-) + \frac{1}{C} \int_{0^-}^{0^+} i(t) dt; \quad v(0^-) = v(0^+) = v_s$$

- 电容的电流可以发生突变



# 自然响应的求解

$$v(0^+) = v_s$$

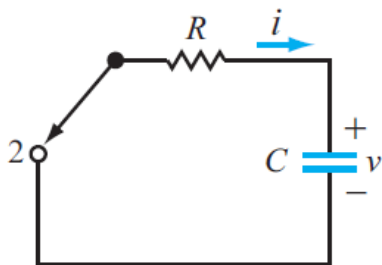

(c) At  $t \geq 0$

## 节点电压法

$$\text{KCL: } C \frac{dv}{dt} + \frac{v}{R} = 0$$

$$\frac{dv}{v} = -\frac{1}{RC} dt$$

$$d\ln(v) = -\frac{1}{RC} dt$$

$$\ln v - \ln v(0) = \ln \frac{v}{V_s} = -\frac{1}{RC} t$$

$$\frac{v}{V_s} = e^{-\frac{1}{RC} t}$$

$$v = V_s e^{-\frac{1}{RC} t}$$

$$[RC] = \Omega \cdot F = s$$



# General First Order Constant Coefficient Differential Equation

$$a \frac{dx}{dt} + bx + c = 0 \quad (1)$$

$$x(t = 0) = x_0$$

$$a \frac{d(x + \frac{c}{b})}{dt} + b(x + \frac{c}{b}) = 0$$

Let  $x' = x + \frac{c}{b}$ , then  $\frac{a}{b} \frac{dx'}{dt} + x' = 0$ , which has the same form as the natural response. Therefore,

$$x' = x'(0)e^{-\frac{b}{a}t}$$

$$x = \left[ x(0) + \frac{c}{b} \right] e^{-\frac{b}{a}t} - \frac{c}{b}$$

$$= \underbrace{[x(0) - x(\infty)]e^{-\frac{b}{a}t}}_{\text{自然响应}} + \underbrace{x(\infty)}_{\text{稳态}}$$


Note:

1.  $x(\infty) = -\frac{c}{b}$  is the solution of Eq.

(1) when  $\frac{dx}{dt} = 0$ .

2. 自然响应的等效初始值为真实初始值与稳态值之差。

# Step Response of an RC circuit

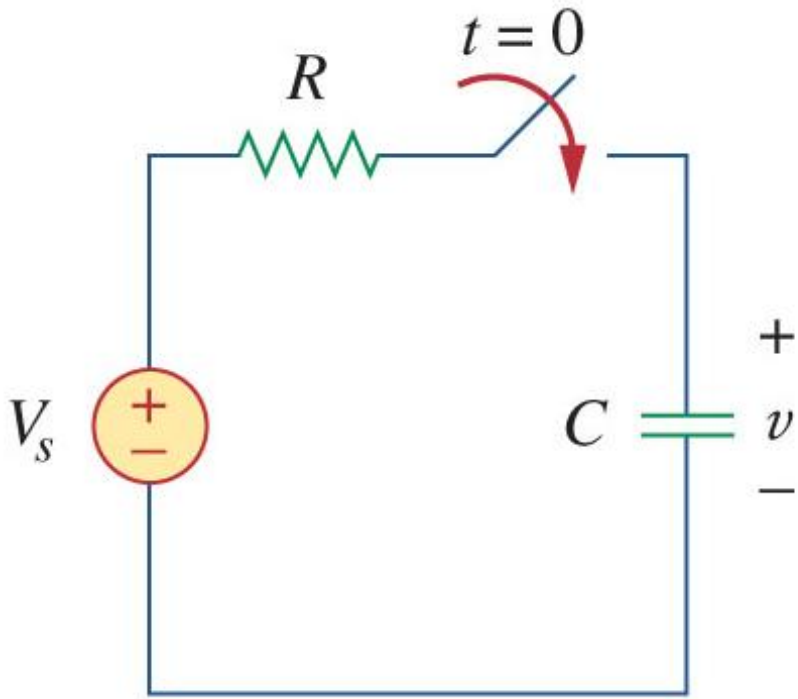

## Method 1

$$t = 0^+: v = 0.$$

$$t > 0: \frac{v - V_s}{R} + C \frac{dv}{dt} = 0$$

Then solve the equation following the general procedure.

## Method 2


$$t = 0^+: v = 0.$$

$$t = \infty: v = V_s$$


$$V(t) = -V_s e^{-\frac{t}{RC}} + V_s$$



# RC电路的阶跃响应

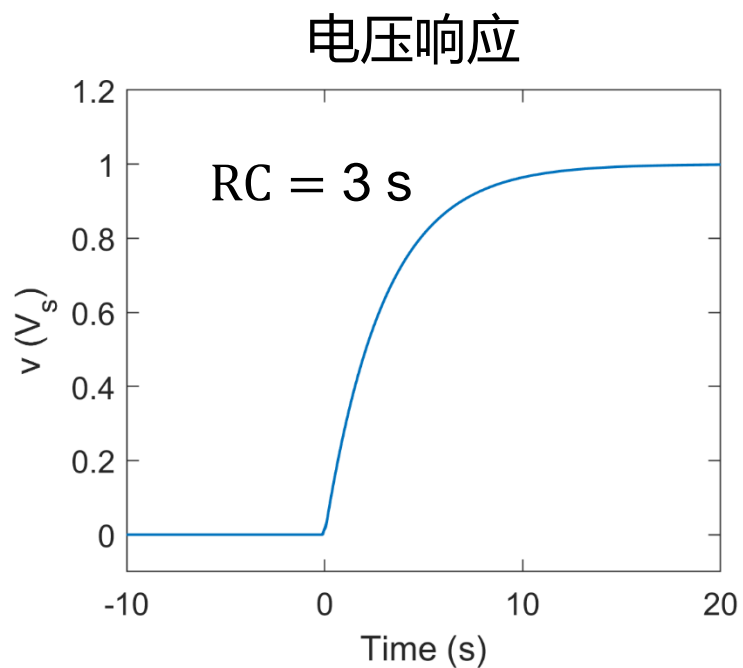


连续

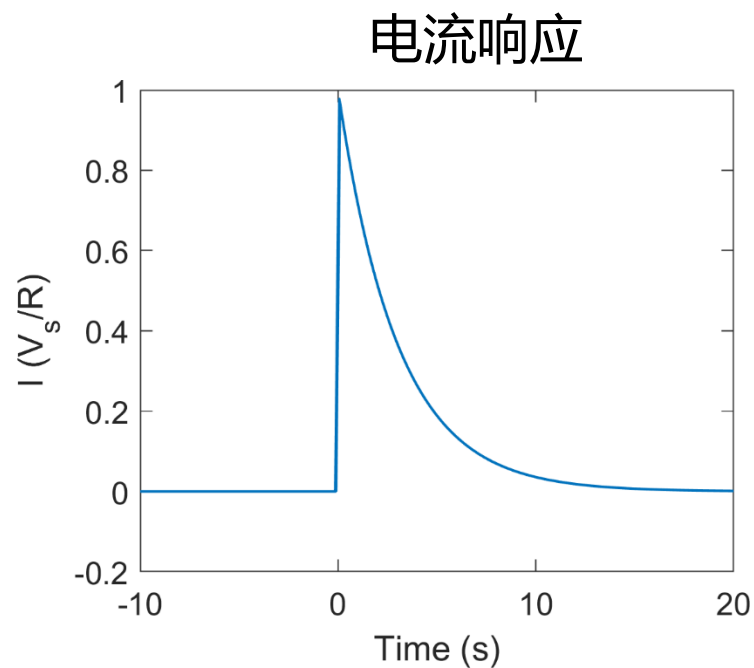

不连续

## RC电路应用实例

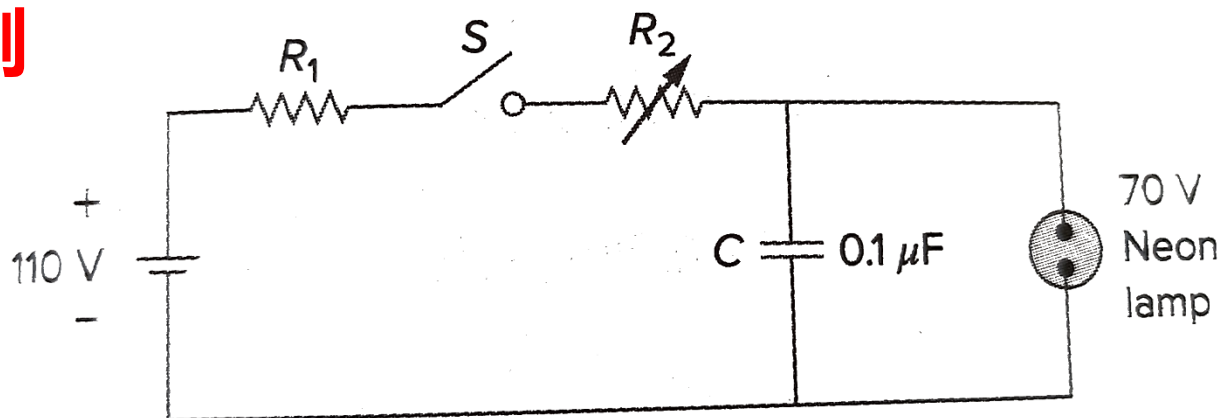

当电容两端电压达到70 V时，霓虹灯开启。开启后的低电阻使电容两端电压迅速降为零，霓虹灯关闭，电容重新开始充电。求霓虹灯的闪烁频率。当闪烁频率为1 Hz时，电阻值应为多少？


After lamp is turned off at  $t=0$ ,  $v = -110e^{-\frac{t}{(R_1+R_2)C}} + 110$ .

When lamp is on at  $t = t_{\text{on}}$ ,  $-110e^{-\frac{t_{\text{on}}}{(R_1+R_2)C}} + 110 = 70$ .  
 $t_{\text{on}} = (R_1+R_2)C \ln \frac{11}{4}$ ,  $f = \frac{1}{t_{\text{on}}} = 0.99 \frac{1}{(R_1+R_2)C}$ .


当  $0.99 \frac{1}{(R_1+R_2)C} = 1$ ,  $(R_1+R_2) = 9.9 \text{ M}\Omega$ .
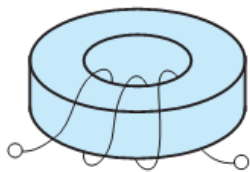
# Inductors


- A storage element that stores energy in magnetic field.
  - They have applications in lamps, transformers, radios, MRI machines, defibrillator, and electric motors.
- Any conductor has inductance, but the effect is typically enhanced by coiling the wire up around high permeability cores.



(a) Toroidal inductor

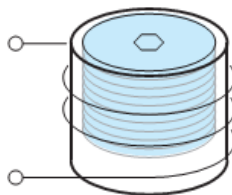

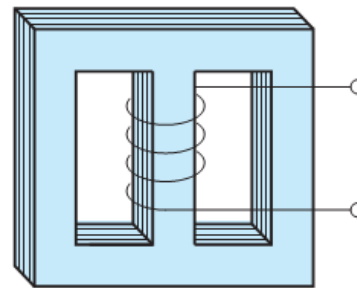(b) Coil with an iron-oxide slug that can be screwed in or out to adjust the inductance



(c) Inductor with a laminated iron core



## 螺旋线圈电感器相关公式

$$\text{磁场 } B = \mu \cdot \text{单位长度电流密度} = \mu \frac{N}{l} I;$$

$$\text{磁通量 } \Phi = BSN, \quad S \text{ 为线圈的截面积}$$

$$V = \frac{d\phi}{dt} = \frac{\mu N^2 S}{l} \frac{dI}{dt} = L \frac{dI}{dt}$$

$$\text{所以, 电感 } L = \frac{N^2 \mu S}{l}$$

$$\Delta \text{ Energy} = \int_0^t V I dt = \int_0^t L \frac{dI}{dt} I dt = \int_0^t L I dI = \frac{1}{2} L I^2 \Big|_0^t$$

$$E = \frac{1}{2} L I^2; (\text{单位换算: } \text{H A}^2 = \text{J})$$

$N$ 为线圈的圈数,  $l$ 为长度,  $\mu$  – magnetic permeability;  
磁导率 (真空  $\mu_0 = 4\pi \cdot 10^{-7} \text{ N/A}^2$  or  $4\pi \cdot 10^{-7} \text{ H/m}$ )



# 电感与电容比较

	电容	电感
储存量	$Q = CV$	$\Phi = LI$
电磁场	$E = \frac{\text{自由电荷面密度}}{\varepsilon}$	$B = \mu \cdot \text{单位长度电流密度}$ $= \mu \frac{N}{l} I = \frac{\Phi}{SN}$
$I - V$ 关系	$I = \frac{dQ}{dt} = C \frac{dV}{dt}$	$V = \frac{d\Phi}{dt} = L \frac{dI}{dt}$
电容电感公式	$C = \frac{Q}{V} = \frac{\varepsilon AE}{Ed} = \frac{\varepsilon A}{d}$	$L = \frac{N^2 \mu S}{l}$
能量	$\frac{1}{2} CV^2$	$\frac{1}{2} LI^2$





## Practice

- What is the inductance of a coil with diameter = 4 mm, length = 10 mm, 50 loops and  $\mu = 100 \mu_0$ ?

$$\frac{100 \times 4\pi \times \frac{10^{-7} \text{H}}{\text{m}} 50^2 \pi (0.002 \text{ m})^2}{0.01 \text{ m}} = 395 \mu\text{H}$$


- What is the stored energy if the current is 1 A?

$$E = \frac{1}{2} L I^2 = 197.5 \mu\text{J}$$


## Direction of the induced voltage



楞次定律：感应电压具有这样的方向，它的效应总要阻碍引起感应电压的磁通量的变化。

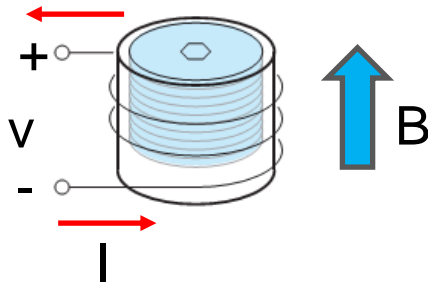


or

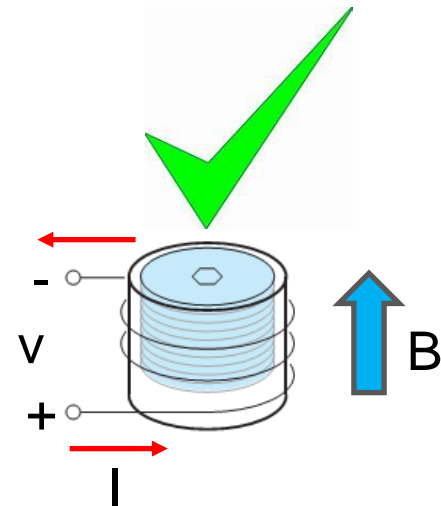



What is the direction of  $v$  when  $I$  increases with time?

该电压施加于外部电路所造成的电流方向与  $I$  的变化方向相反。

# Important Property of Inductors

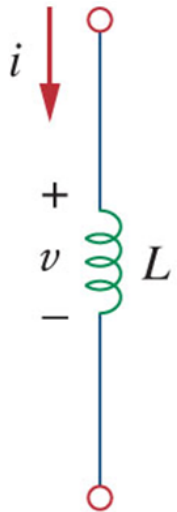

$$v = L \frac{di}{dt}$$

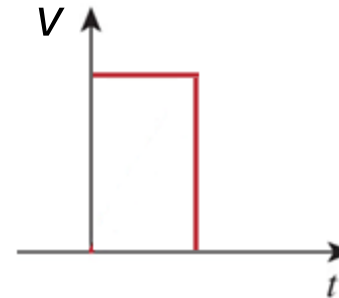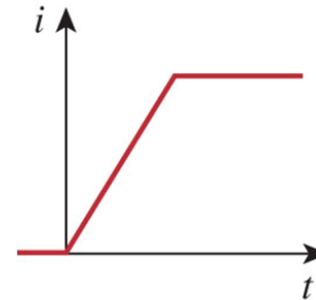



At static state,  $v = 0 \text{ V}$ ,  $R = 0 \Omega$ ;

Inductor can be treated as short circuit at steady state.





# Inductor response to a sinusoidal current

电容

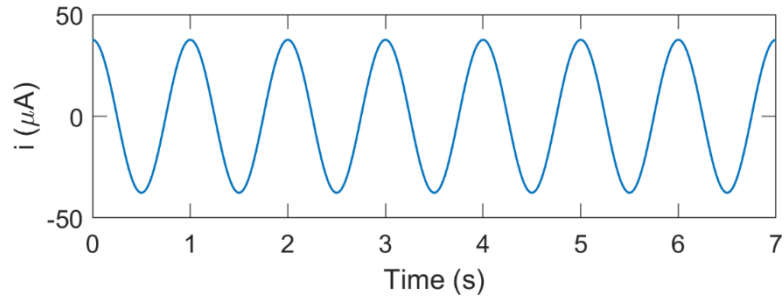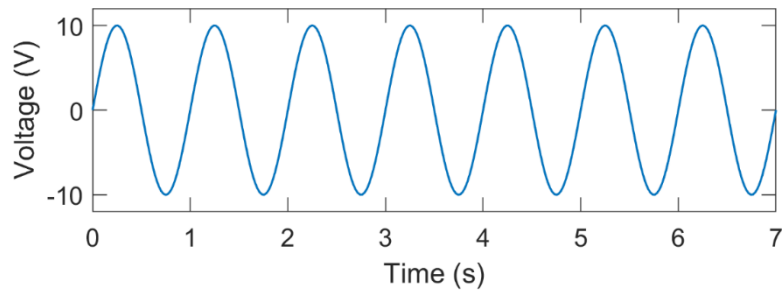



电流相位提早 $\pi/2$

电感

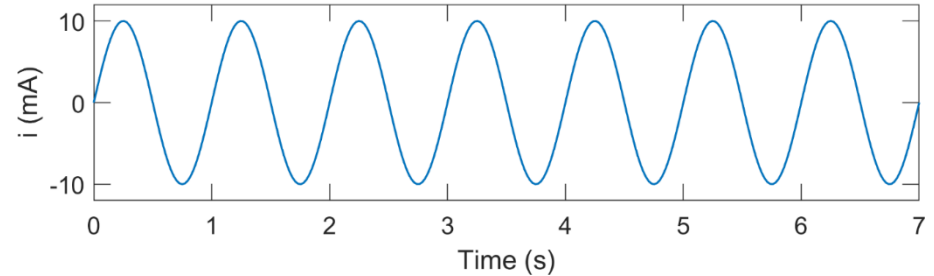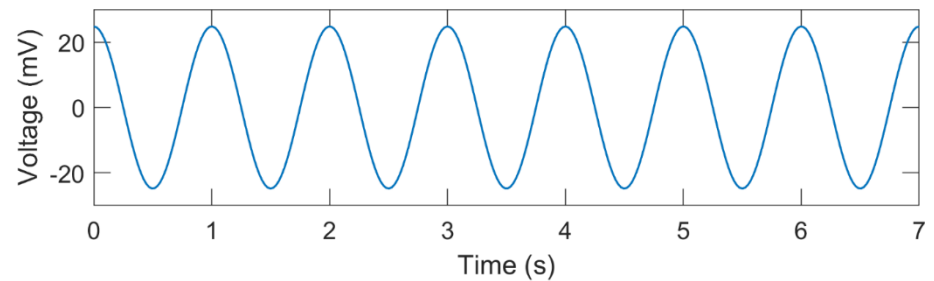

电压相位提早 $\pi/2$

# Inductors in Series

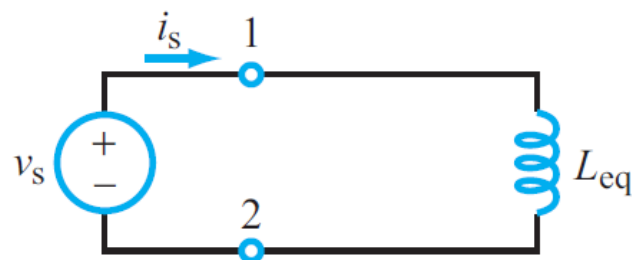
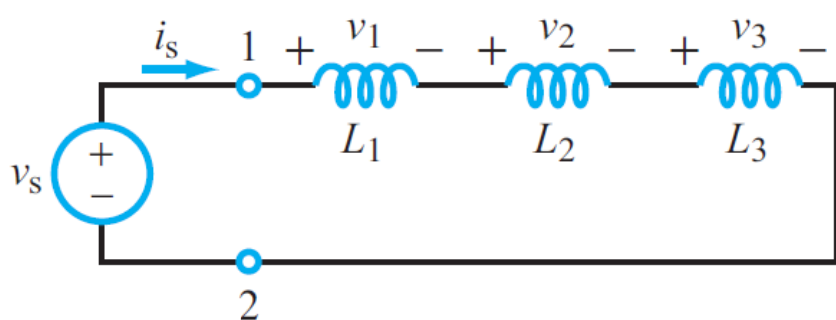


$$\begin{aligned} V_s &= v_1 + v_2 + v_3 = L_1 \frac{dI}{dt} + L_2 \frac{dI}{dt} + L_3 \frac{dI}{dt} \\ &= (L_1 + L_2 + L_3) \frac{dI}{dt} \\ &= L_{eq} \frac{dI}{dt} \end{aligned}$$

$$L_{eq} = L_1 + L_2 + L_3$$

# Inductors in Parallel

## Combining In-Parallel Inductors

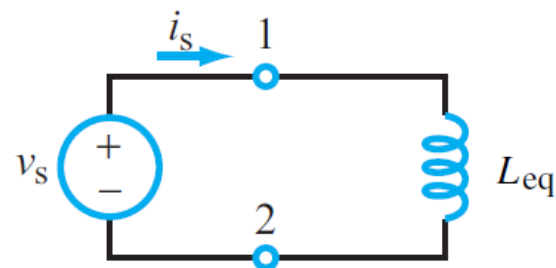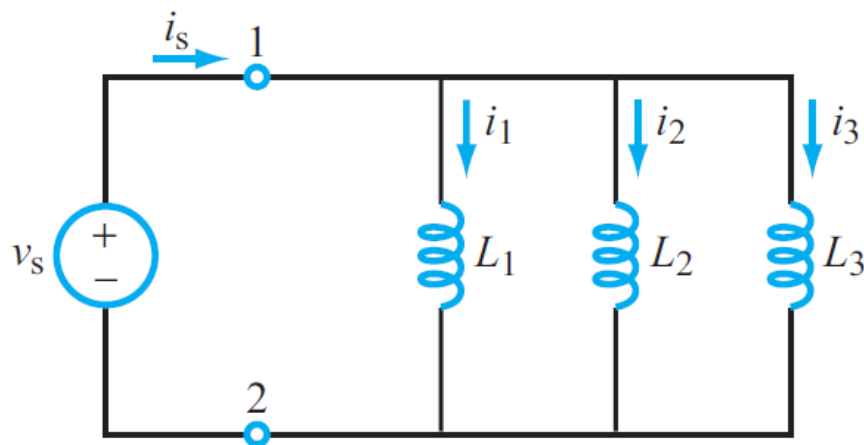

$$I = i_1 + i_2 + i_3$$

$$V_s = L_1 \frac{di_1}{dt} = L_2 \frac{di_2}{dt} = L_3 \frac{di_3}{dt}$$

$$\begin{aligned} V_s &= L_{eq} \frac{dI}{dt} = L_{eq} \left( \frac{di_1}{dt} + \frac{di_2}{dt} + \frac{di_3}{dt} \right) \\ &= L_{eq} \left( \frac{V_s}{L_1} + \frac{V_s}{L_2} + \frac{V_s}{L_3} \right) \Rightarrow L_{eq} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}} \end{aligned}$$




## RLC串并联的等效公式

	串联	并联
电阻	$R_1 + R_2$	$\frac{R_1 R_2}{R_1 + R_2}$
电容	$\frac{C_1 C_2}{C_1 + C_2}$	$C_1 + C_2$
电感	$L_1 + L_2$	$\frac{L_1 L_2}{L_1 + L_2}$


	串联分压	并联分流
电阻	$\frac{R_i}{R_1 + R_2}$	$\frac{1/R_i}{1/R_1 + 1/R_2}$
电容	$\frac{1/C_i}{1/C_1 + 1/C_2}$	$\frac{C_i}{C_1 + C_2}$
电感	$\frac{L_i}{L_1 + L_2}$	$\frac{1/L_i}{1/L_1 + 1/L_2}$

# 稳态值

求当开关位于1和2位置时电感的稳态电压和电流分别时多少？

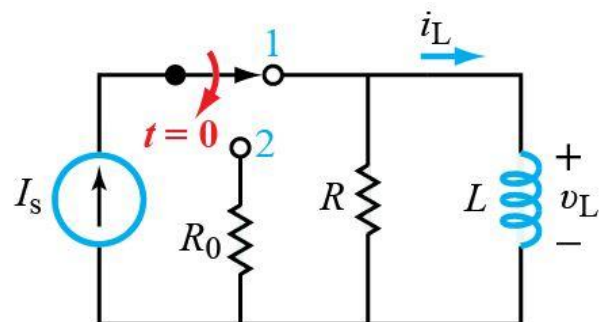


开关位置1

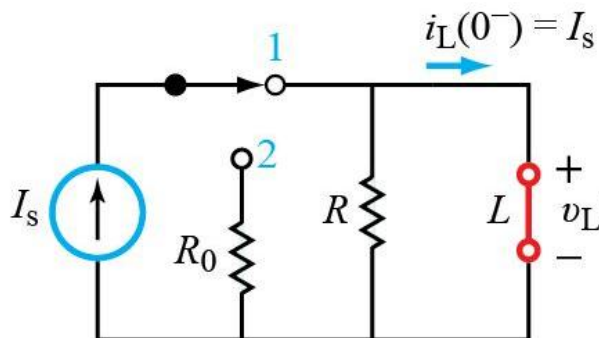

$$i_L = I_s$$

$$v_L = 0$$

开关位置2

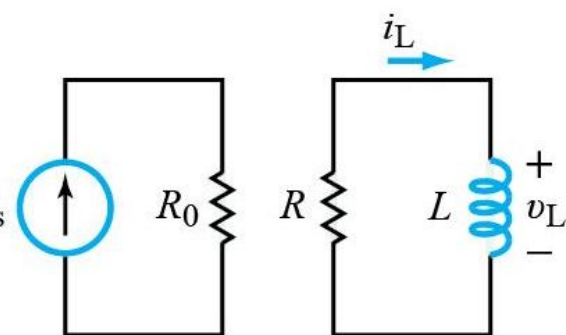


$$i_L = 0$$

$$v_L = 0$$




# Natural Response of the RL Circuit

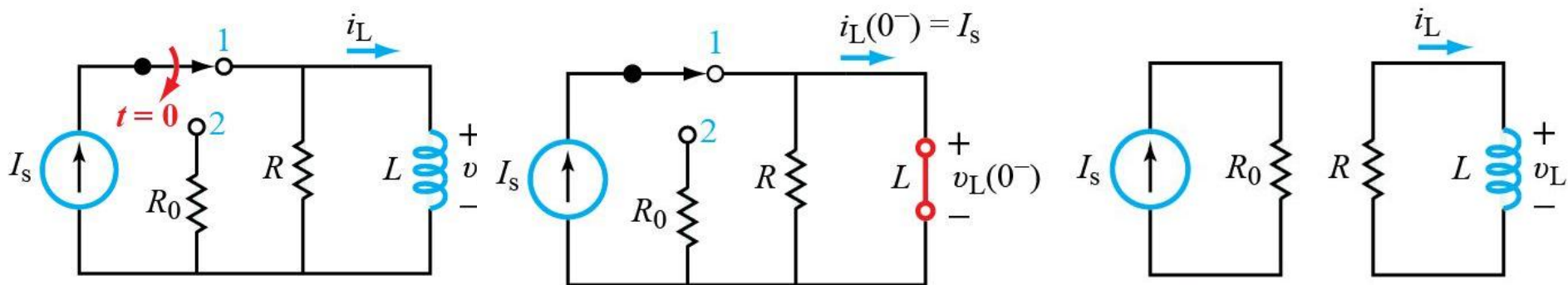

求开关从1切换至2后电感电压电流的自然响应？

$$i_L(0^+) = i_L(0^-) = I_s$$

# Natural Response of the RL Circuit

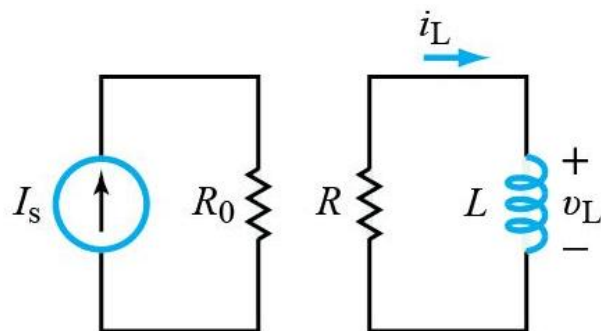

$$i_L(0^+) = I_s$$

$$Ri_L + L \frac{di_L}{dt} = 0$$

$$a=L, \quad b=R, \quad c=0$$

$$i_L(t) = I_s e^{-\frac{R}{L}t} = I_s e^{-\frac{t}{\tau}}$$

$$\tau = \frac{L}{R}$$

$$\text{if } R = 100 \Omega, L = 395 \mu\text{H}$$

$$\tau = \frac{L}{R} = 3.95 \text{ ns}$$

Initial energy stored in the inductor:  $\frac{1}{2} L I_s^2$


Total energy dissipated by the resistor:

$$\int_0^{\infty} i_L^2 R dt = I_s^2 R \int_0^{\infty} e^{-\frac{2t}{\tau}} dt = \frac{\tau}{2} I_s^2 R = \frac{1}{2} L I_s^2$$




# RL电路的自然响应

电压响应

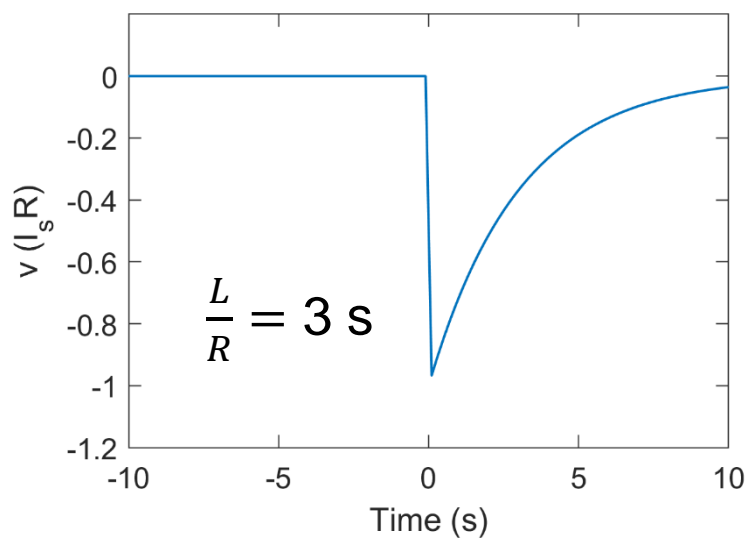


不连续

电流响应

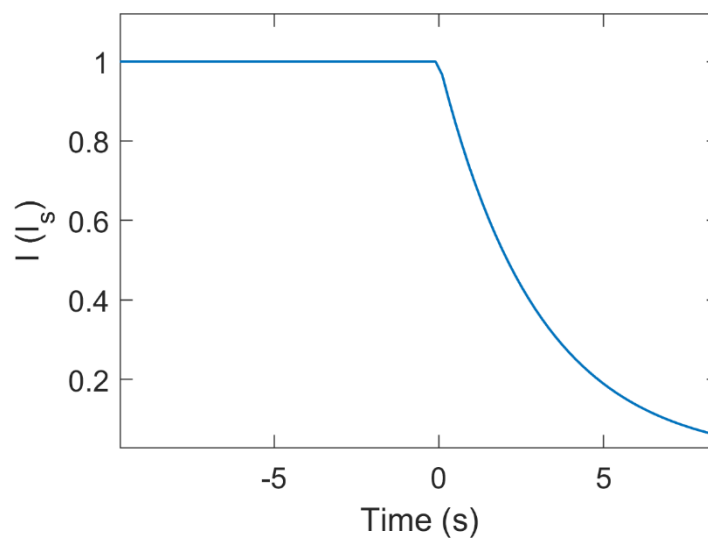

连续

# Step Response of the RL Circuit

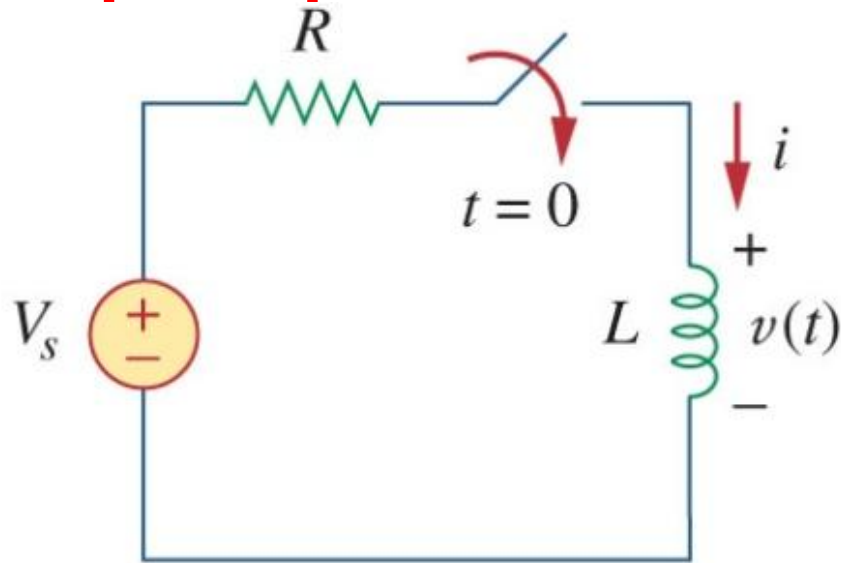

## Method 1

$$i(0^+) = i(0^-) = 0$$

$$-V_s + Ri + L \frac{di}{dt} = 0$$

$$a = L, \quad b = R, \quad c = -V_s$$

$$\tau = \frac{L}{R}$$

## Method 2

$$i(0^+) = i(0^-) = 0$$


$$i(\infty) = \frac{V_s}{R}$$

$$i = -\frac{V_s}{R} e^{-\frac{R}{L}t} + \frac{V_s}{R}$$




# RL电路的阶跃响应

电压响应

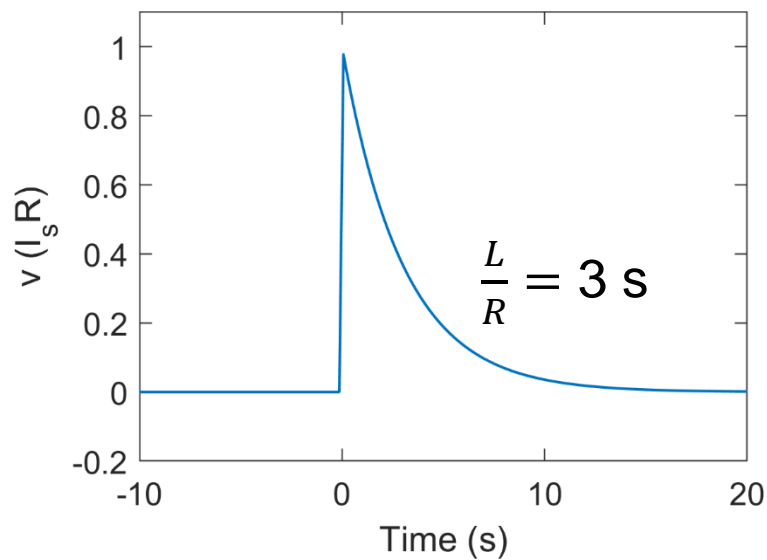

不连续


电流响应

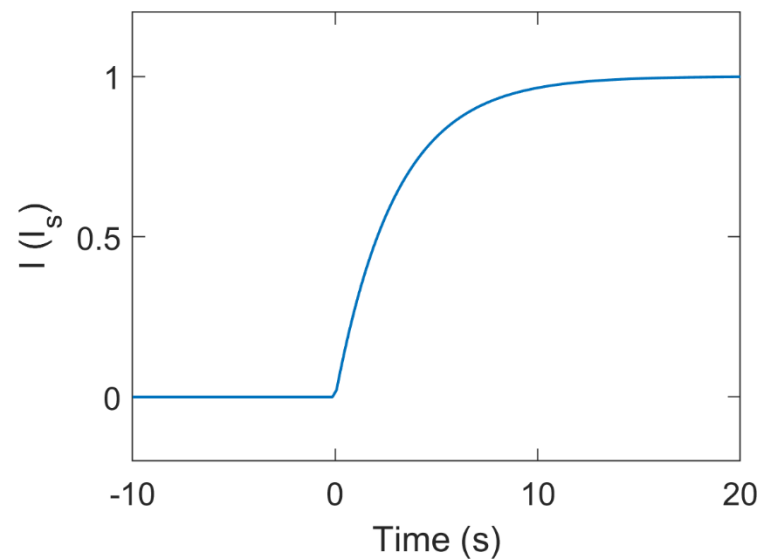

连续
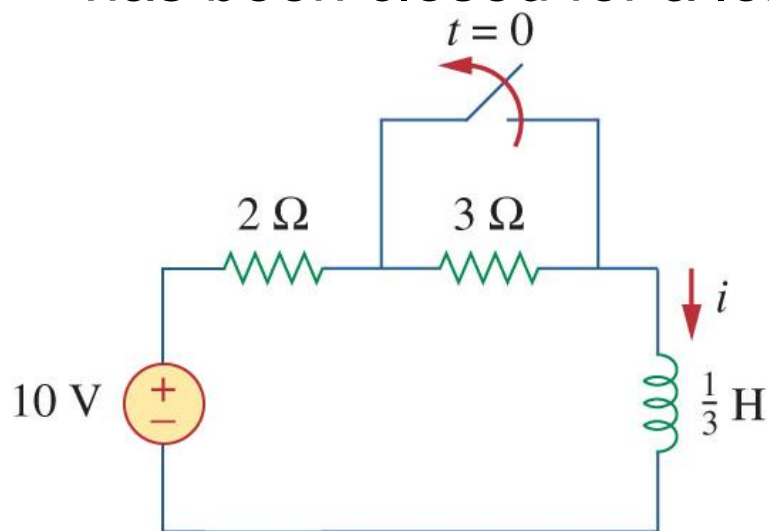
## Exercise

- Find  $i(t)$  in the circuit for  $t > 0$ . Assume that the switch has been closed for a long time.



$$i(0) = 5A$$

$$i(\infty) = 2A$$

$$\tau = \frac{L}{R} = \frac{\frac{1}{3}}{5} = 66.7ms$$

$$t > 0: i(t) = (5-2)e^{-\frac{t}{66.7ms}} + 2 \text{ unit } A$$