




Lecture 10

- Frequency Response

Relevance to BME

ECG信号工频干扰去除

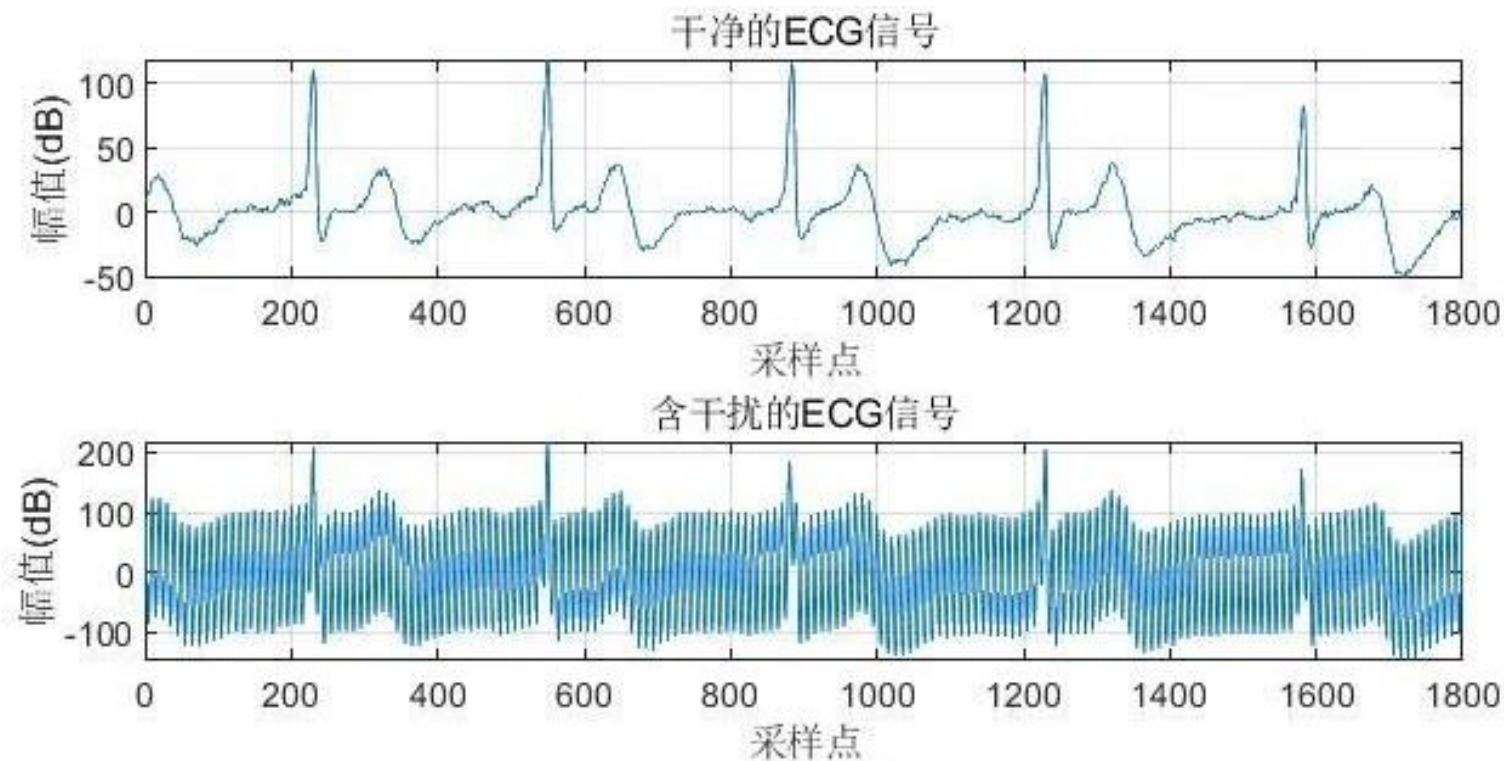




EEG frequency bands

脑电信号采集


Comparison of EEG Bands




Gamma: 30-100+ Hz

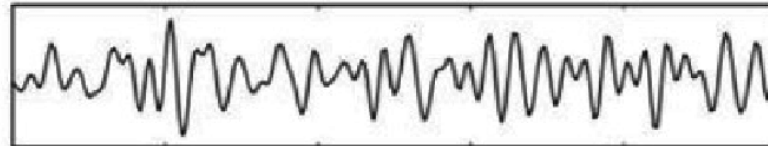


Beta: 12-30 Hz

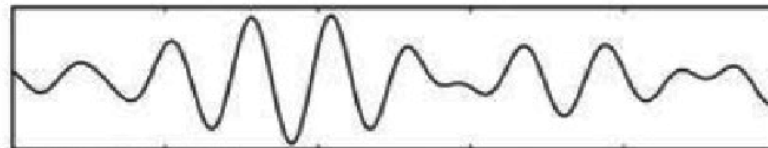

Alpha: 8-12 Hz

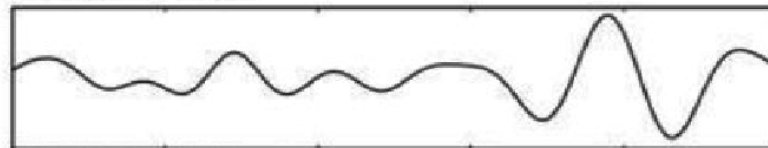

Theta: 4-7 Hz

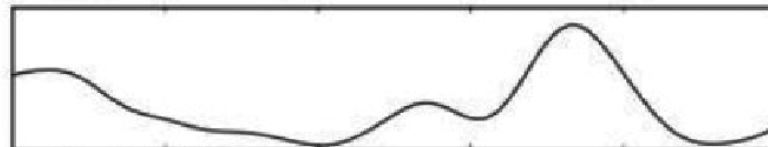


Delta: 0-4 Hz



Outline


- Frequency response
- Transfer function
- Bode plots
- Resonance
- Filters

Frequency Response

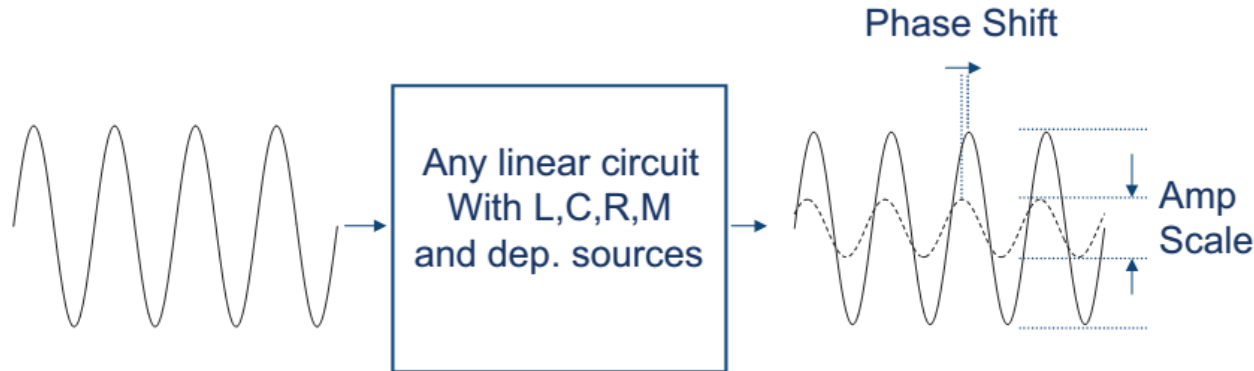


- When a linear circuit is excited by a sinusoid, its steady-state output is a sinusoid at the *same* frequency.
 - Only the magnitude and phase of the output differ from the input.
- The “Frequency Response” is a characterization of the variation in input-output relationship for sinusoidal inputs with frequency.

Frequency Dependence

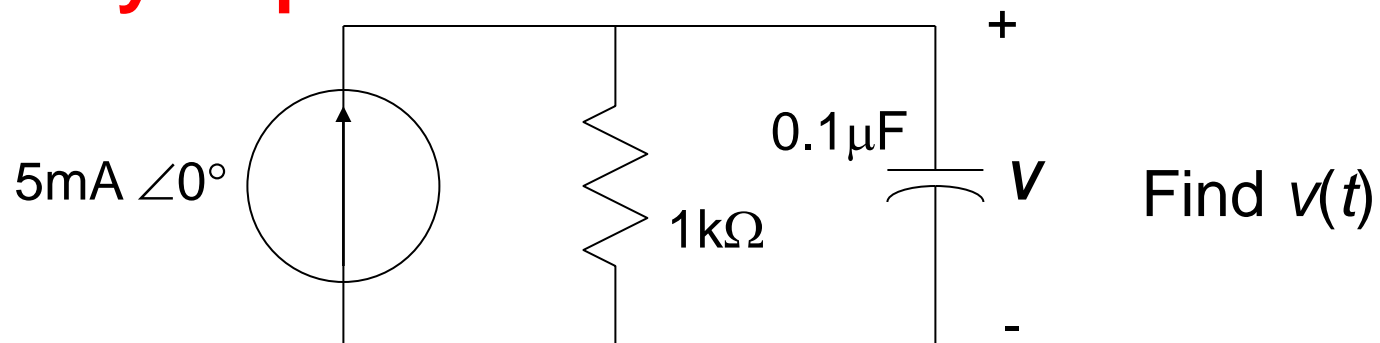


Case 1: $\omega = 2\pi \times 3000$

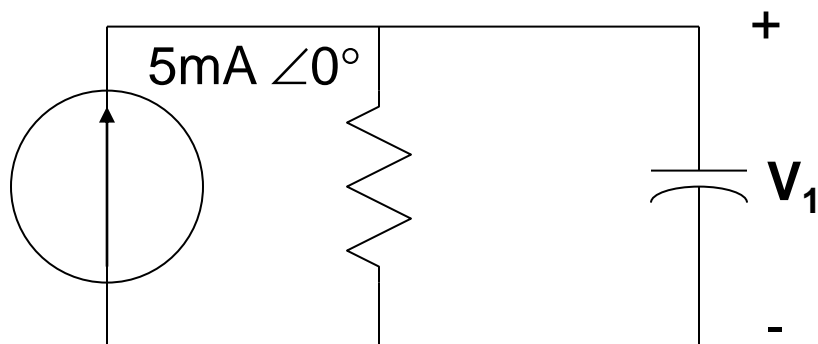

$$\mathbf{Z}_{eq} = 468.2 \angle -62.1^\circ \Omega$$

$$\mathbf{V}_1 = 2.34 \angle -62.1^\circ \text{V}$$

Case 2: $\omega = 2\pi \times 455000$

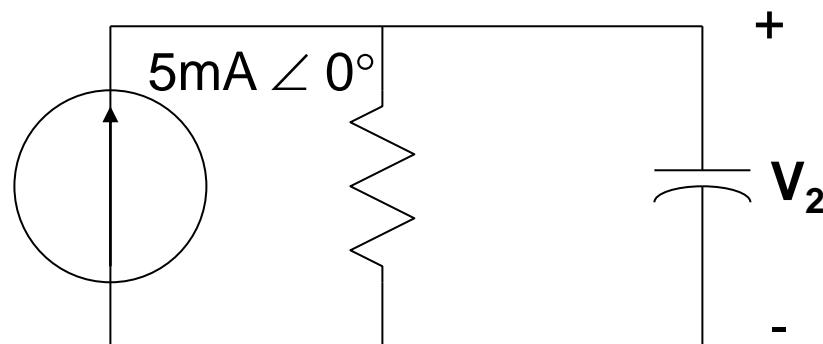

$$\mathbf{Z}_{eq} = 3.5 \angle -89.8^\circ \Omega$$

$$\mathbf{V}_2 = 17.5 \angle -89.8^\circ \text{mV}$$




Outline

- Frequency response
- Transfer function
 - Definition
 - Capacitor voltage in RC circuit
 - Inductor voltage in RL circuit
 - Human impedance model
 - Output prediction
- Bode plots
- Resonance
- Filters


Transfer Function

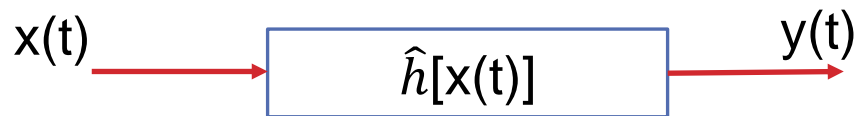- The transfer function $H(\omega)$ is the frequency-dependent ratio of a phasor output $Y(\omega)$ to a phasor input $X(\omega)$.



$$H(\omega) = \text{Voltage gain} = \frac{V_o(\omega)}{V_i(\omega)}$$
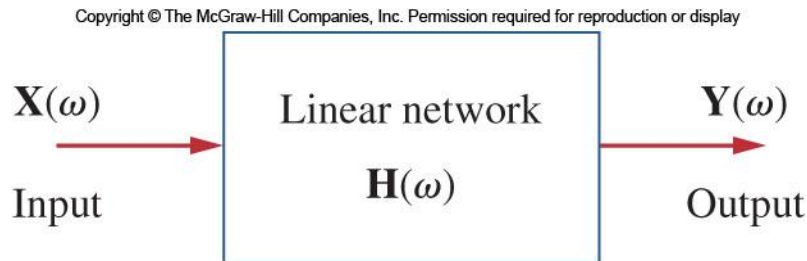
$$H(\omega) = \text{Current gain} = \frac{I_o(\omega)}{I_i(\omega)}$$



$$H(\omega) = \frac{Y(\omega)}{X(\omega)}$$

$$H(\omega) = \text{Transfer impedance} = \frac{V_o(\omega)}{I_i(\omega)}$$

$$H(\omega) = \text{Transfer admittance} = \frac{I_o(\omega)}{V_i(\omega)}$$

Transfer impedance is equal to the impedance if the input and output ports are the same.


Transfer Function

- Complex quantity; ratio of two phasors (but not a phasor)
- Both magnitude and phase are functions of frequency



$$\mathbf{H}(f) = \frac{\mathbf{V}_{out}}{\mathbf{V}_{in}} = \frac{V_{out}}{V_{in}} \angle (\theta_{out} - \theta_{in})$$
$$\mathbf{H}(\mathbf{f}) = H(f) \angle \theta(f)$$

Example


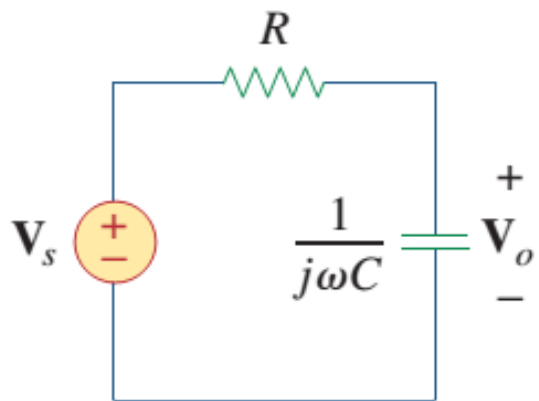


$$V_o = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} V_s = \frac{1}{j\omega CR + 1} V_s = \frac{1}{j\omega/\omega_0 + 1} V_s$$

$$\omega_0 = \frac{1}{RC}$$





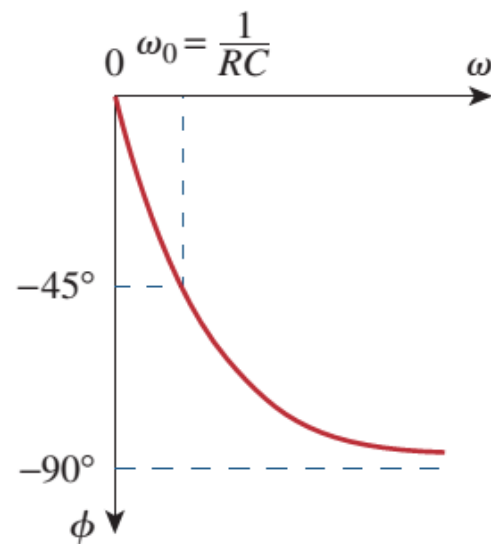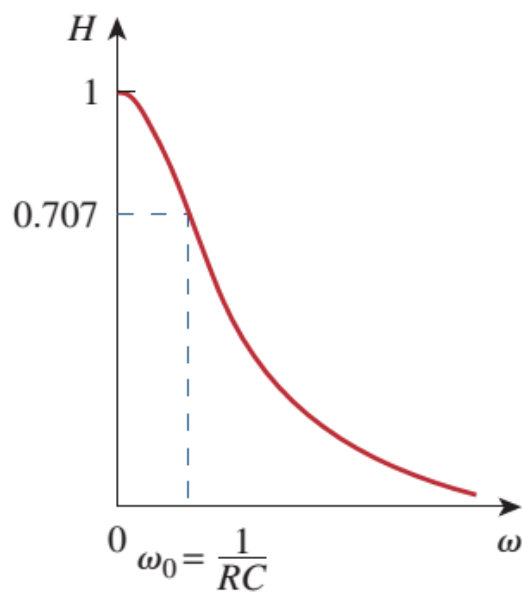
$$H = \frac{1}{\sqrt{1 + (\omega/\omega_0)^2}}, \quad \phi = -\tan^{-1} \frac{\omega}{\omega_0}$$



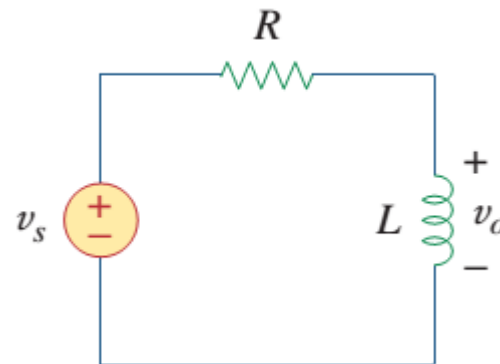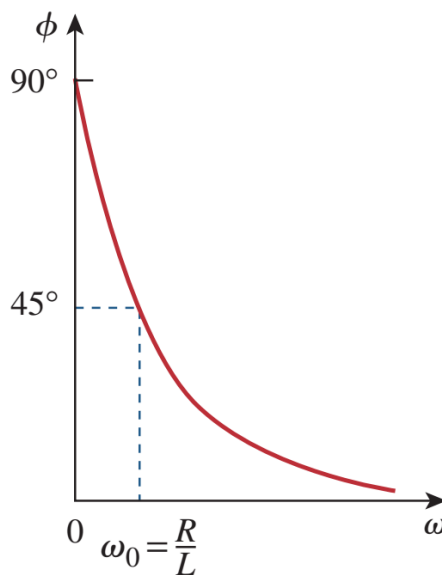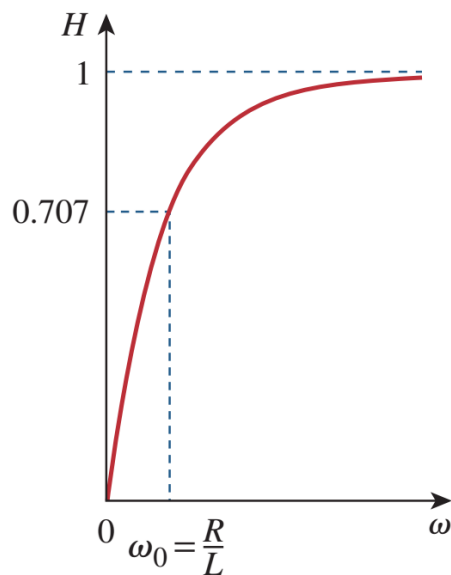
Exercise

- Obtain the transfer function V_o/V_s of the RL circuit.



Human Impedance Model


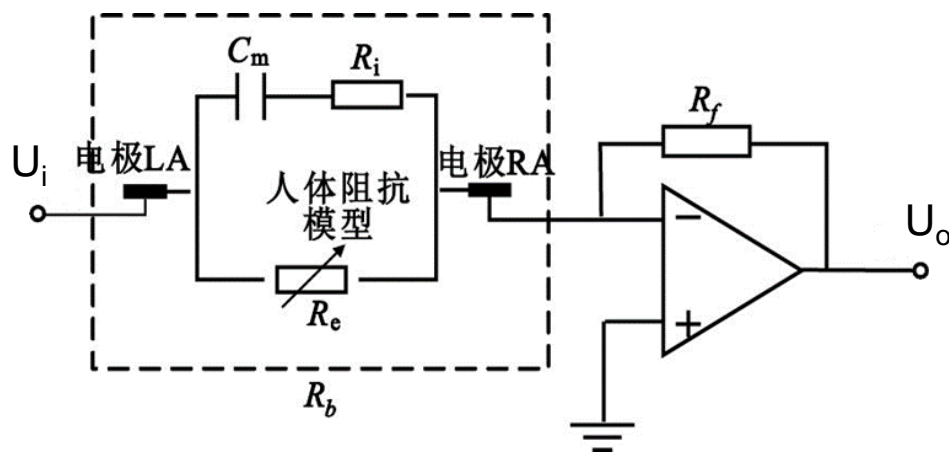
Obtain the transfer function of the following circuit which can be used to measure the impedance of the human body.



$$\begin{aligned} \frac{U_o}{U_i} &= -R_f \left(\frac{1}{R_e} + \frac{j\omega C_m}{j\omega R_i C_m + 1} \right) = -\frac{R_f}{R_e} - \frac{R_f}{R_i} \frac{j\frac{\omega}{\omega_0}}{j\frac{\omega}{\omega_0} + 1} = -\frac{R_f}{R_e} - \frac{R_f}{R_i} \left[1 - \frac{1}{j\frac{\omega}{\omega_0} + 1} \right] \\ &= -\frac{R_f}{R_e} - \frac{R_f}{R_i} + \frac{R_f}{R_i} \frac{1}{j\frac{\omega}{\omega_0} + 1} \quad \omega_0 = \frac{1}{R_i C_m} \end{aligned}$$




Human Impedance Model

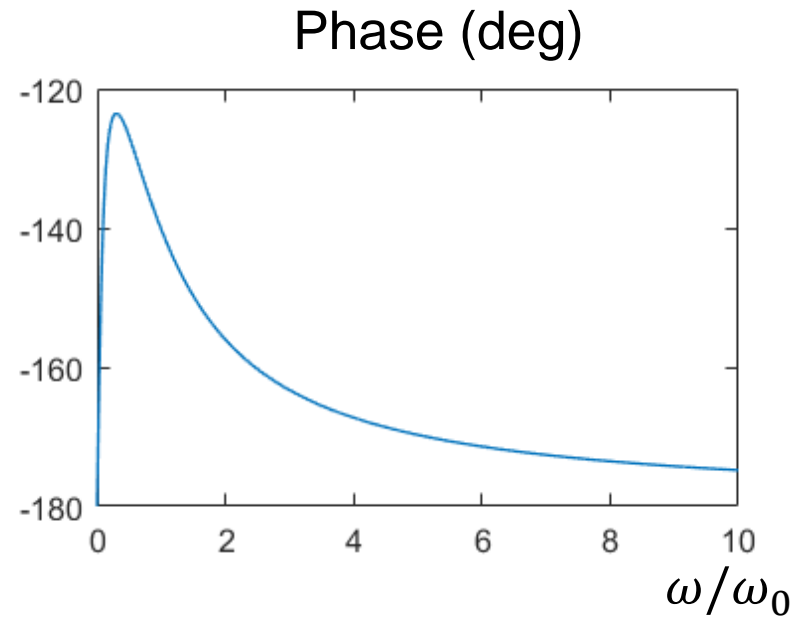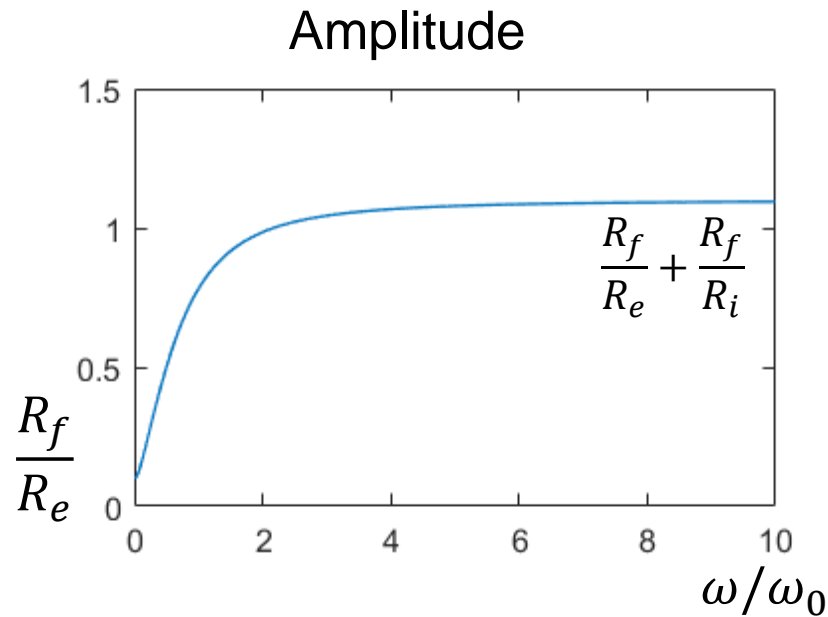

$$\sqrt{\left(\frac{R_f}{R_e} + \frac{R_f}{R_i} \frac{(\frac{\omega}{\omega_0})^2}{1 + (\frac{\omega}{\omega_0})^2}\right)^2 + \left(\frac{R_f}{R_i} \frac{\frac{\omega}{\omega_0}}{1 + (\frac{\omega}{\omega_0})^2}\right)^2}$$

$$\omega_0 = \frac{1}{R_i C_m}$$

Response to multiple frequency components


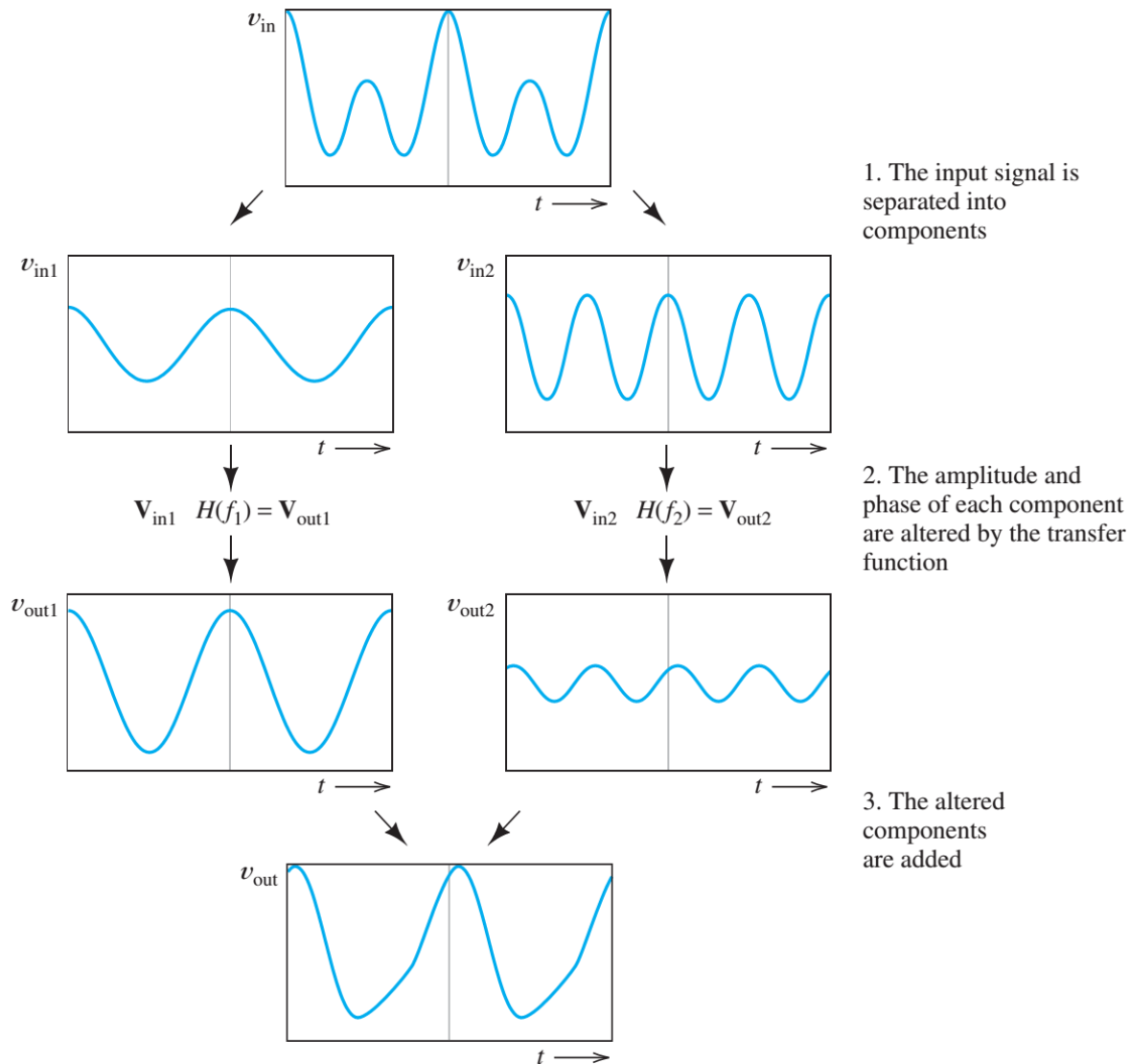


Exercise II – output prediction

- If the input signal is

$$v_{\text{in}}(t) = 3 + 2 \cos(2000\pi t) + \cos(4000\pi t - 70^\circ),$$

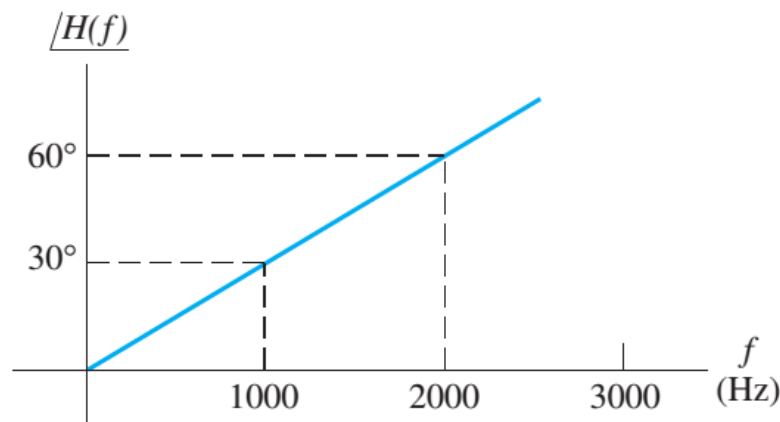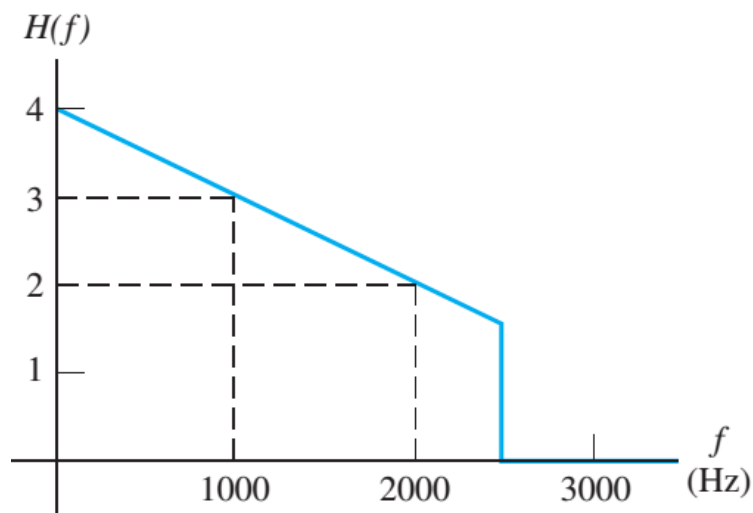find an expression as a function of time for the output.



Answer: $v_{\text{out}}(t) = 12 + 6 \cos(2000\pi t + 30^\circ) + 2 \cos(2000\pi t - 10^\circ)$



Outline

- Frequency response
- Transfer function
- Bode plots (or diagram)
 - Motivation
 - General form of transfer functions
 - Bell and Decibel
 - Bode plots for 0th, 1st, 2nd order polynomials
- Resonance
- Filters



General Form of the Transfer Function

$$H(f) = \frac{\sum_{i=0}^m a_i (j2\pi f)^i}{\sum_{i=0}^n b_i (j2\pi f)^i}$$

The circuit unknown variables (x ; voltage or current) can be expressed in matrix form as

$$Ax = c$$

Input and output are one of the components in c and x , respectively.

Therefore, $x = A^{-1}c$. The transfer function is an element of the A^{-1} matrix.

$$[A^{-1}]_{i,j} = \frac{\det(A_{j,i}^*)}{\det(A)}, \text{ } A_{ij}^* \text{ is the cofactor (代数余子式) of } A_{ij}.$$

All determinants can be expressed as polynomials of the impedances.

$$\det(A) = K \sum_{i=0}^n a_i (j\omega)^{i-m} = \frac{K}{(j\omega)^m} \sum_{i=0}^n a_i (j\omega)^i, \text{ where}$$

m and n depend on the number of independent inductors and capacitors.

$$\text{Similarly, } \det(A_{j,i}^*) = \frac{K'}{(j\omega)^{m'}} \sum_{i=0}^{n'} a_i (j\omega)^i$$

Bode Plots

- Bode plot is a tool for visualizing (understanding) the transfer function.


$$H(f) = \frac{\sum_{i=0}^m a_i (j\omega)^i}{\sum_{i=0}^n b_i (j\omega)^i} = \frac{K(j\omega)^{\pm 1} (1 + j\omega/z_1)[1 + j2\zeta_1\omega/\omega_k + (j\omega/\omega_k)^2]\cdots}{(1 + j\omega/p_1)[1 + j2\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2]\cdots}$$

$$\log |H(f)| = \log |K| \pm \log \omega + \log |1 + j \frac{\omega}{z_1}| + \log |1 + \frac{j2\zeta_1\omega}{\omega_k} + (j\omega/\omega_k)^2| + \dots$$

$$\begin{aligned} \angle(H(f)) &= \angle(K) \pm \angle(j\omega) + \angle(1 + j \frac{\omega}{z_1}) + \angle\left(1 + \frac{j2\zeta_1\omega}{\omega_k} + \left(\frac{j\omega}{\omega_k}\right)^2\right) - \\ &\angle(1 + j \frac{\omega}{p_1}) - \angle\left(1 + \frac{j2\zeta_2\omega}{\omega_n} + \left(\frac{j\omega}{\omega_n}\right)^2\right) \dots \end{aligned}$$

- Each of the above terms are not always present.
- Each term can be considered separately and then summed up.



Bode Plots

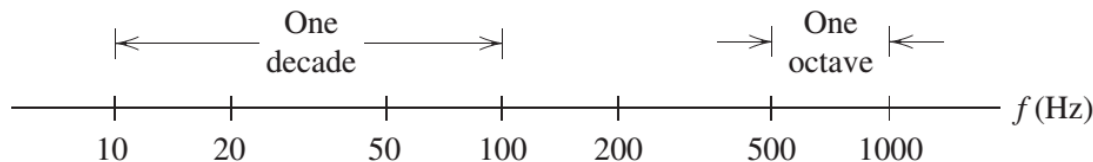

Plotting the frequency response, magnitude or phase, on plots with

- Frequency X in log scale
- Y scale in dB (for magnitude) or degree (for phase)

Example: $H(w) = \frac{1}{1+j(f/f_B)}$

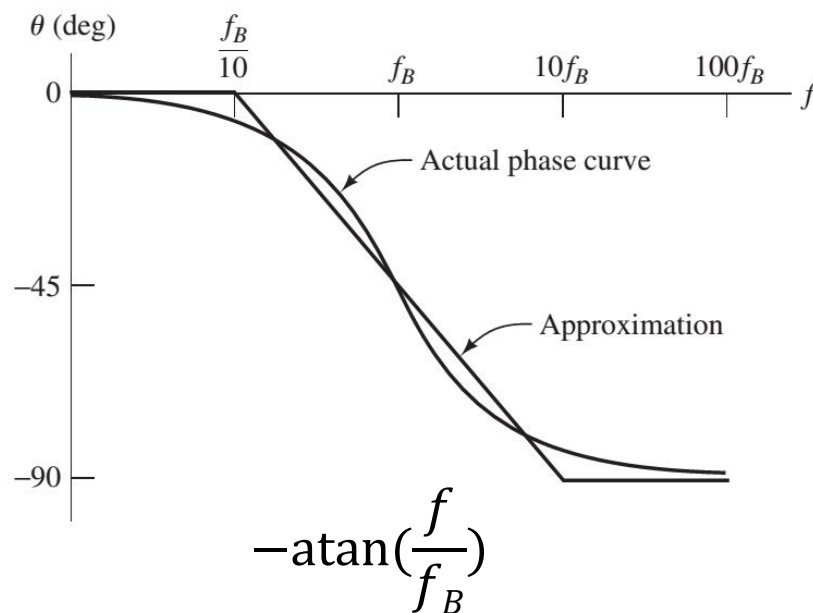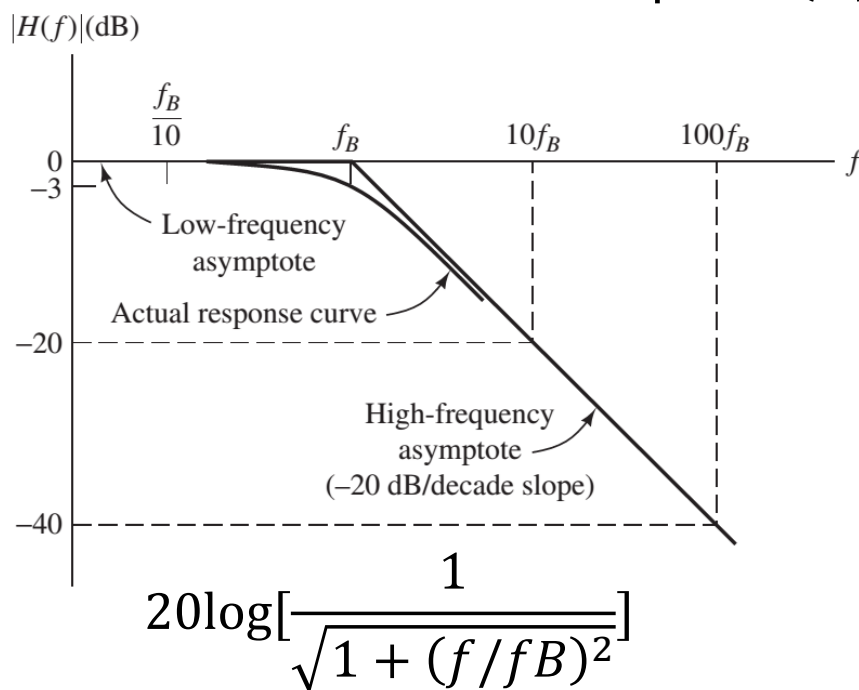

Bel and Decibel (dB)

- A **bel** (symbol **B**) is a unit of measure of ratios of *power* levels, i.e. relative power levels.
 - The name was coined in the early 20th century in honor of Alexander Graham Bell, a telecommunication pioneer.
 - Definition of bel: $\text{Ratio} = \log_{10}(P_1/P_2) \text{ B}$,
where P_1 and P_2 are *power levels*.
- One bel is too large for everyday use, so the **decibel (dB)**, equal to 0.1B, is more commonly used.

$$\text{Ratio} = \log_{10}(P_1/P_2) \text{ B} = 10 \log_{10}(P_1/P_2) \text{ dB}$$

$$\begin{aligned} 1 \text{ B} &= 10 \text{ dB} \\ 1 \text{ dB} &= 0.1 \text{ B} \end{aligned}$$



dB for Power

- To express a power in terms of decibels, one starts by choosing a reference power, $P_{\text{reference}}$, and write


$$\text{Power } P \text{ in decibels} = 10 \log_{10}(P/P_{\text{reference}})$$

- When the reference is 1 mW, the dB value is called dBm. dBm is a measure of absolute power. e.g. 0 dBm = 1 mW; 10 dBm = 10 mW
- Exercise: Express a power of 50 mW in decibels relative to 1 watt and 1mW.

$$\begin{aligned} P \text{ (dB)} &= -13 \text{ dB when } P_{\text{reference}} = 1 \text{ W.} \\ P \text{ (dBm)} &= 17 \text{ dBm} \end{aligned}$$

dB for transfer function

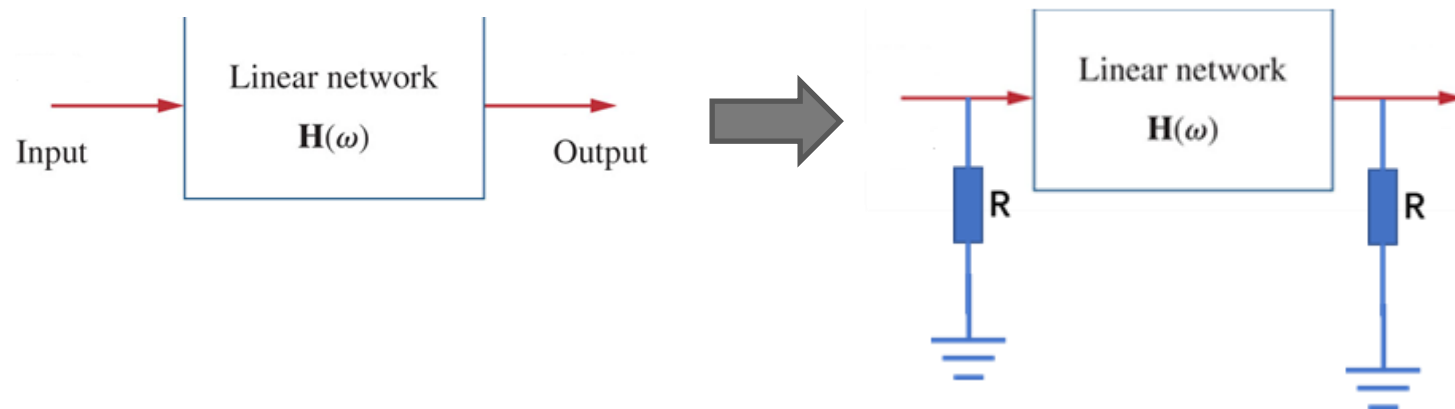To convert transfer function into power ratio, imagine connecting two loads with the same impedance to the input and output.



$$G_{dB} = 10 \log_{10} \frac{P_{\text{output}}}{P_{\text{input}}} = 10 \log_{10} |H(\omega)|^2 = 20 \log_{10} |H(\omega)|$$



dB for Voltage or Current

Question: How many decibels larger is the voltage of a 9-volt battery than that of a 1.5-volt AA battery?

$$\text{Answer: } 20\log_{10}(9/1.5) = 15.6 \text{ dB}$$

Question: What is the output/input voltage(power) ratio of an amplifier with a gain of 34 dB?

$$\text{Answer: } 10^{34/20} = 50 \text{ (voltage); } 10^{34/10} = 2512 \text{ (power)}$$


Question: How many decibels larger is the voltage(power) if the voltage (power) is doubled?

$$\begin{aligned} \text{Answer: } 20\log_{10}(2) &= 6 \text{ dB (voltage)} \\ 10\log_{10}(2) &= 3 \text{ dB (power)} \end{aligned}$$


Constant term K

$$\mathbf{H}(\omega) = \frac{K(j\omega)^{\pm 1} (1 + j\omega/z_1)[1 + j2\zeta_1\omega/\omega_k + (j\omega/\omega_k)^2]\cdots}{(1 + j\omega/p_1)[1 + j2\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2]\cdots}$$

$K > 0$

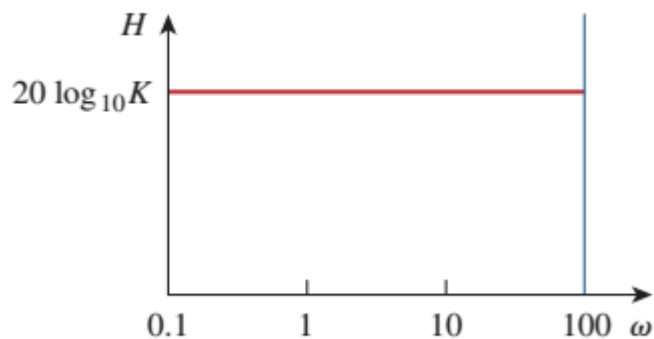


(a)

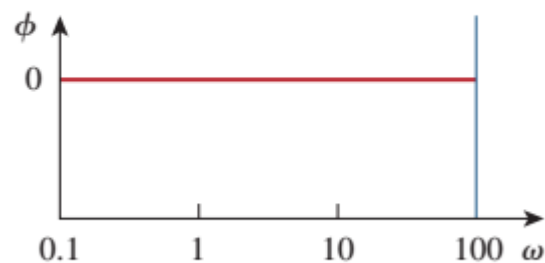


(b)

$K < 0$

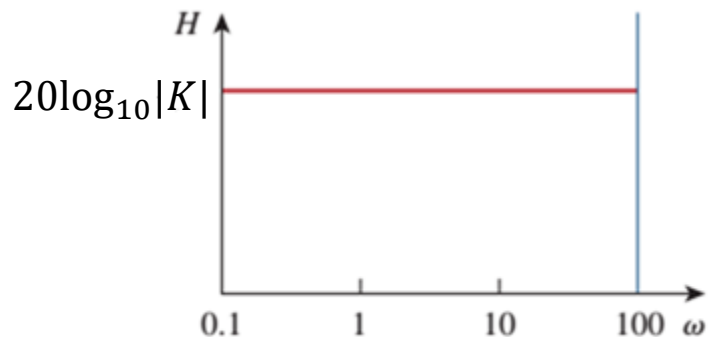

(a)

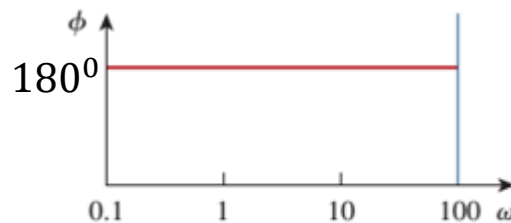


(b)




$j\omega$
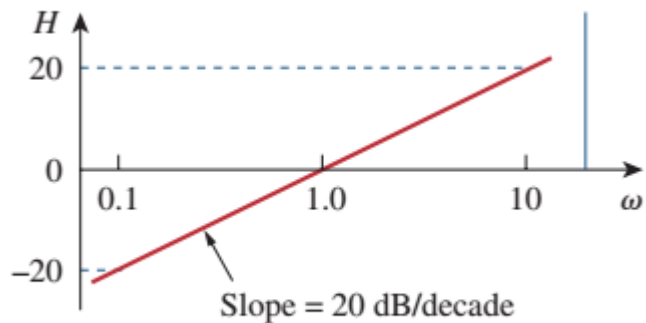
$$\mathbf{H}(\omega) = \frac{K(j\omega)^{\pm 1} (1 + j\omega/z_1)[1 + j2\zeta_1\omega/\omega_k + (j\omega/\omega_k)^2]\cdots}{(1 + j\omega/p_1)[1 + j2\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2]\cdots}$$




(a)

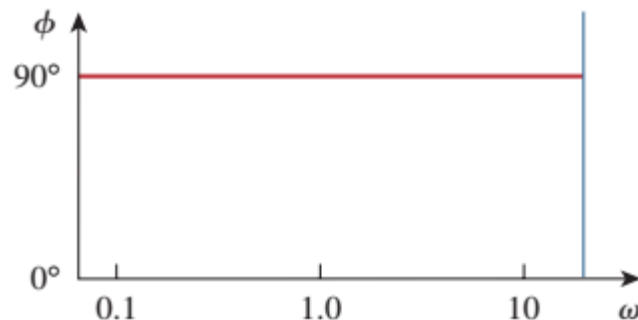


(b)

$(j\omega)^{-1}$

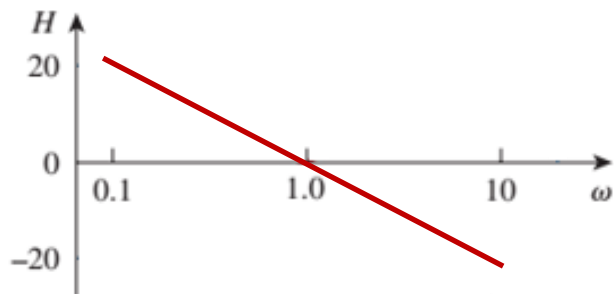


(a)

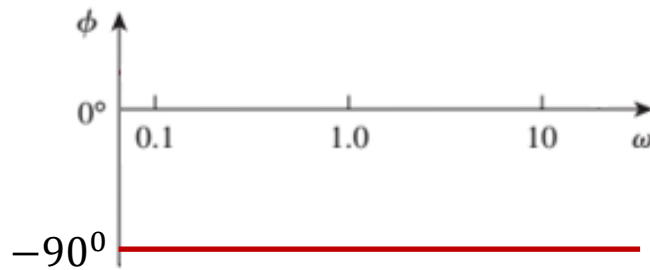

(b)



$$(j\omega)^{\pm N}$$

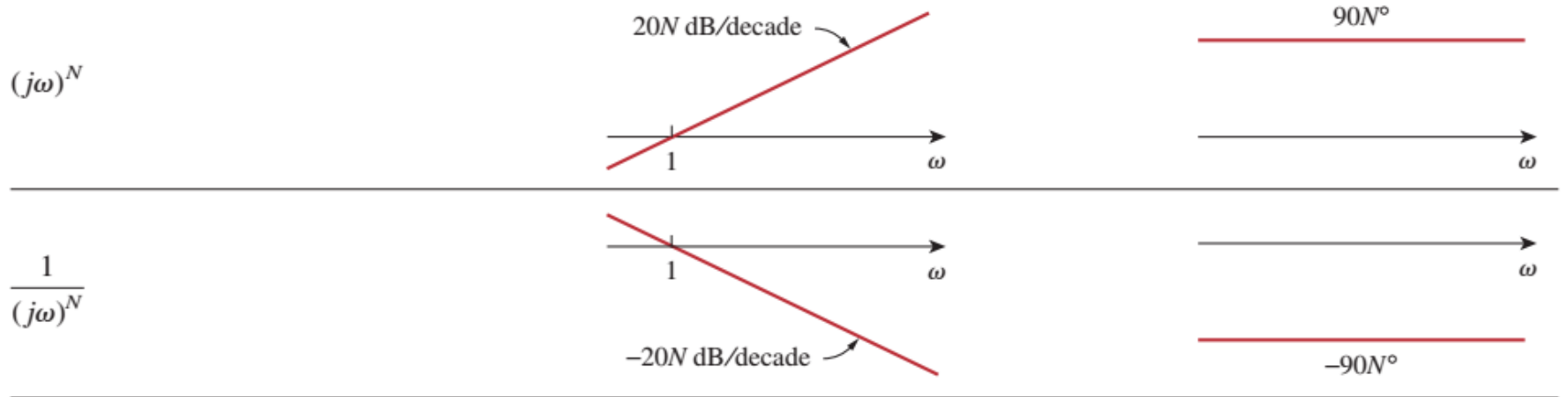





$$1 + j\omega/z_1$$

$$\mathbf{H}(\omega) = \frac{K(j\omega)^{\pm 1} (1 + j\omega/z_1)[1 + j2\zeta_1\omega/\omega_k + (j\omega/\omega_k)^2]\cdots}{(1 + j\omega/p_1)[1 + j2\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2]\cdots}$$

	H_{dB}	φ
$\omega \rightarrow 0$	0	0
$\omega \gg z_1$	$20(\log_{10} \omega - \log_{10}z_1)$	90°

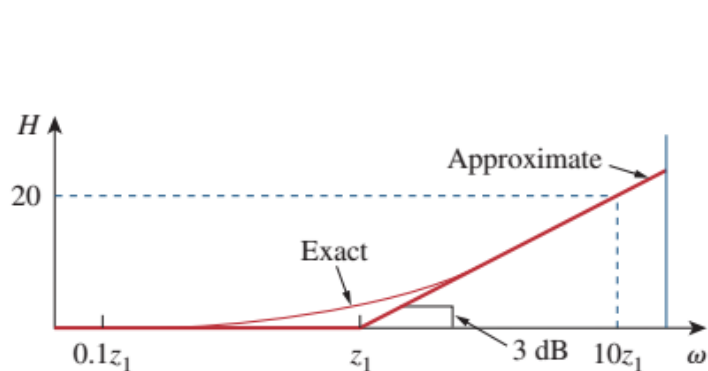



(a)

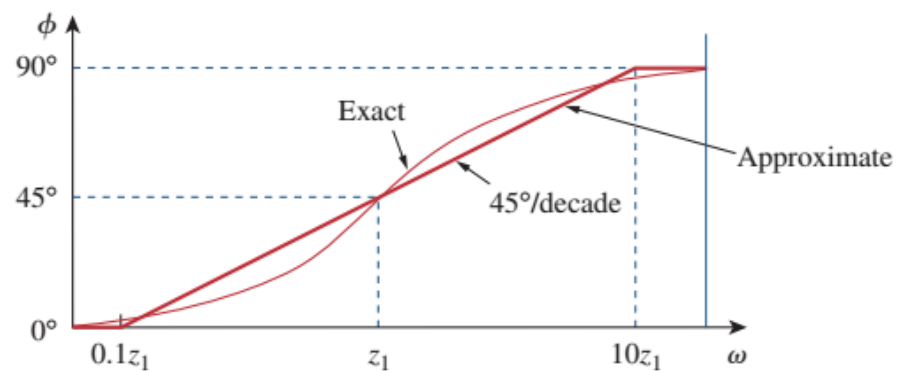

(b)



$$1/(1+j\omega/p_1)$$

	H_{dB}	φ
$\omega \rightarrow 0$	0	0
$\omega \gg p_1$	$-20(\log_{10} \omega - \log_{10}p_1)$	90°

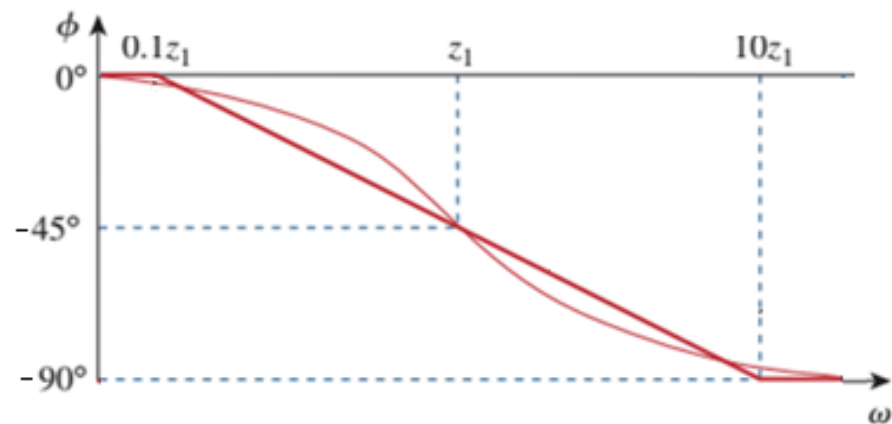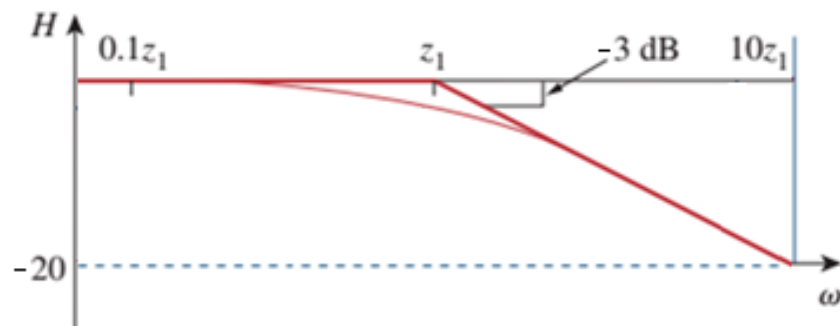

$$1/[1+2j\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2]$$

	H_{dB}	φ
$\omega \rightarrow 0$	0	0
$\omega \gg \omega_n$	$-40(\log_{10} \omega - \log_{10}\omega_n)$	-180°

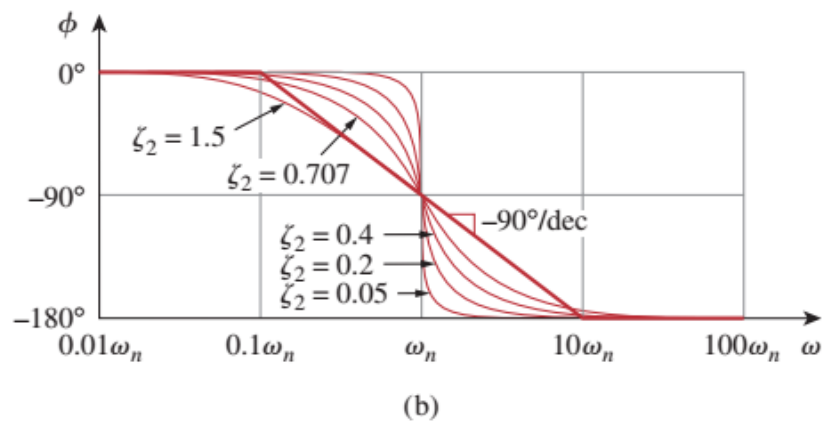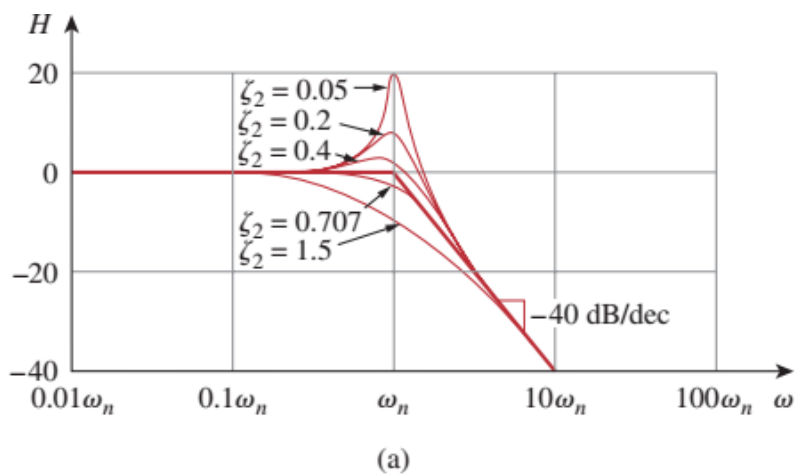



Condition for the presence of a peak/dip

$$|H|^{-2} = \left(1 - \frac{\omega^2}{\omega_n^2}\right)^2 + \left(\frac{2\zeta\omega}{\omega_n}\right)^2$$

$$\frac{d|H|^{-2}}{d\omega} = -2\left(1 - \frac{\omega^2}{\omega_n^2}\right)\frac{2\omega}{\omega_n^2} + \frac{8\zeta^2\omega}{\omega_n^2} = 0$$


$$-\left(1 - \frac{\omega^2}{\omega_n^2}\right) + 2\zeta^2 = 0$$

$$\omega^2 = \omega_n^2(1 - 2\zeta^2) > 0$$

$$|\zeta| < 0.707$$


$|H|^2$ shows a peak at $\omega = \omega_n\sqrt{1 - 2\zeta^2}$, when $\zeta^2 < \frac{1}{2}$ or $|\zeta| < 0.707$

When $\zeta^2 = \frac{1}{2}$, $|H|^2 = \frac{1}{1 + \left(\frac{\omega}{\omega_n}\right)^4}$, 2nd order Butterworth low pass filter.

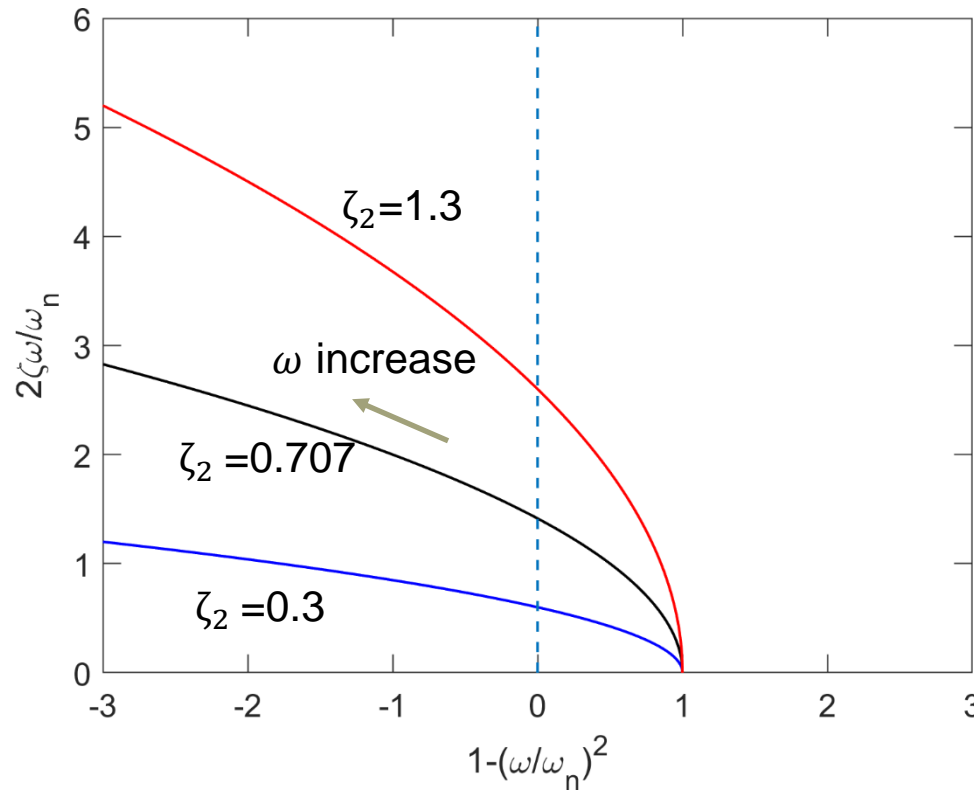

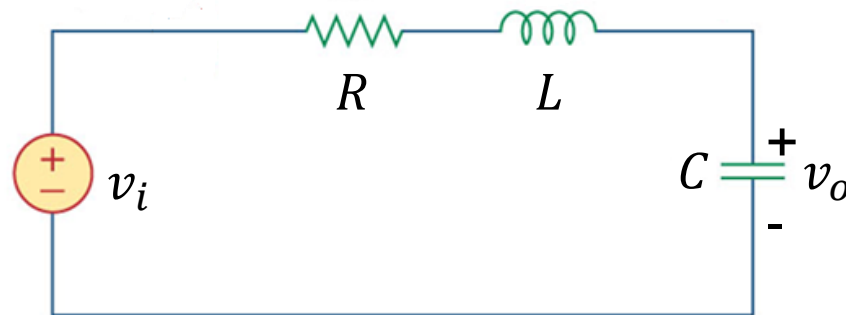Exercise

Compare the condition for the presence of a peak and the underdamping condition in the series RLC circuit.





$$H(\omega) = \frac{\frac{1}{j\omega C}}{j\omega L + \frac{1}{j\omega C} + R} = \frac{1}{1 + j\omega RC + (j\omega LC)^2}$$


$$\omega_n = \frac{1}{\sqrt{LC}}; \frac{2\zeta}{\omega_n} = RC \rightarrow \zeta = \frac{\omega_n RC}{2} \leq \frac{\sqrt{2}}{2}$$

Underdamping for RLC circuit: $\frac{R}{2L} < \omega_n \rightarrow \frac{\omega_n RC}{2} < 1$. No ripple
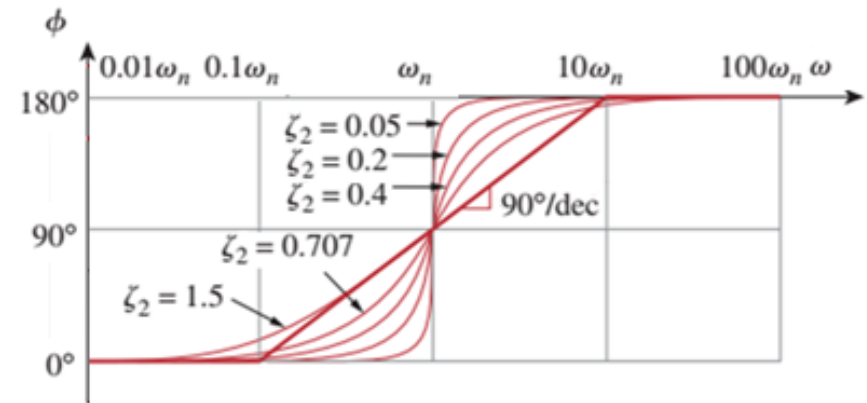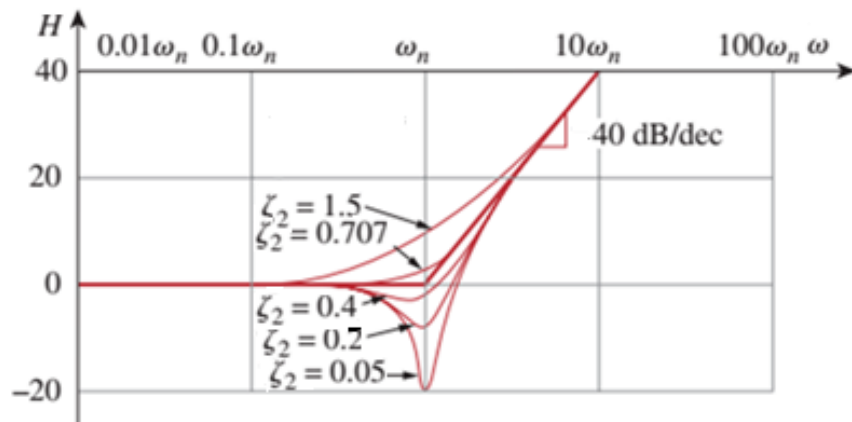
$$1 + 2j\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2$$



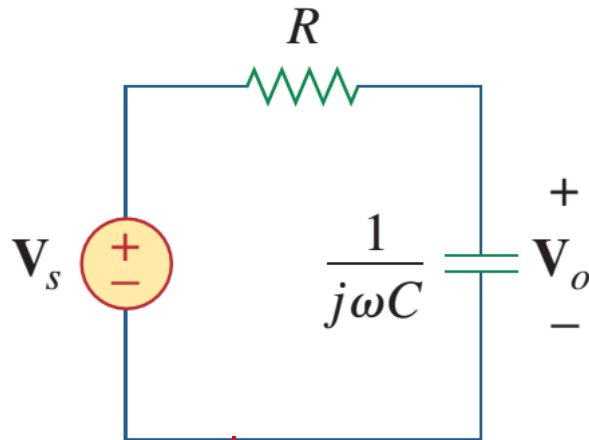Example: Bode Plot of First-Order Lowpass Filter



$$V_o = \frac{1}{j\omega/\omega_B + 1} V_s$$

$$= \frac{1}{jf/f_B + 1} V_s$$

$$\omega_B = \frac{1}{RC}$$

$$f_B = \frac{1}{2\pi RC}$$

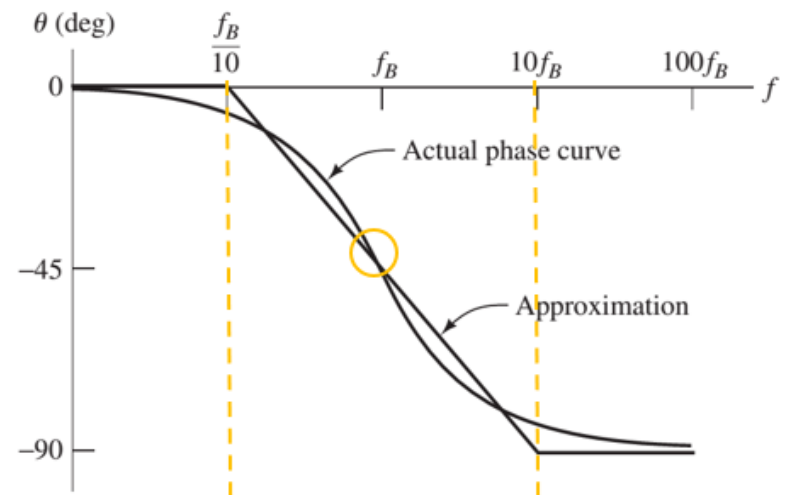
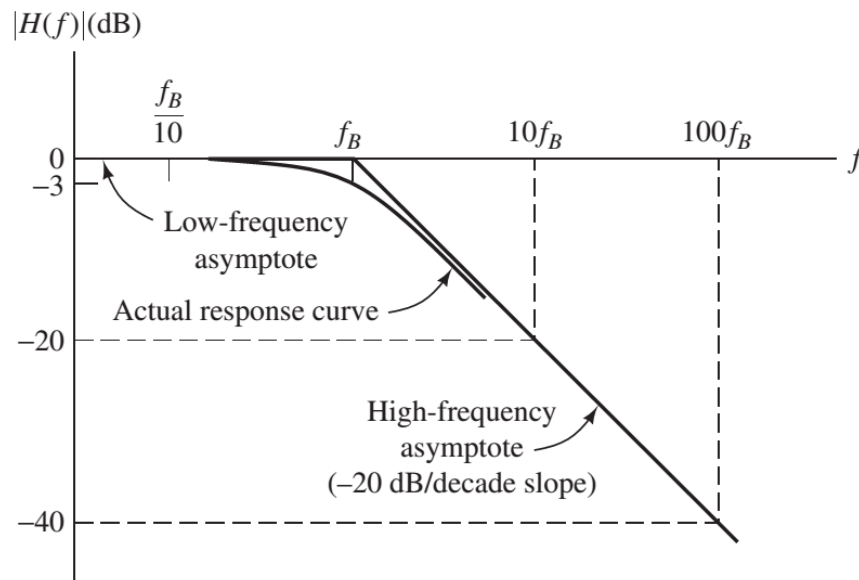


TABLE 14.3

Summary of Bode straight-line magnitude and phase plots.

Factor	Magnitude	Phase
K		
$(j\omega)^N$		
$\frac{1}{(j\omega)^N}$		
$\left(1 + \frac{j\omega}{z}\right)^N$		
$\frac{1}{(1 + j\omega/p)^N}$		
$\left[1 + \frac{2j\omega\zeta}{\omega_n} + \left(\frac{j\omega}{\omega_n}\right)^2\right]^N$		
$\frac{1}{[1 + 2j\omega\zeta/\omega_k + (j\omega/\omega_k)^2]^N}$		

Constant; K = vertical coordinate at $\omega = 1$

Linearly increase/decrease; determine N from initial slope in magnitude plot

Flat for $\omega \rightarrow 0$, determine N from change in slope and determine ω_n from turning point in magnitude plot




Example--Standard Form

$$\mathbf{H}(\omega) = \frac{200j\omega}{(j\omega + 2)(j\omega + 10)} = \frac{10j\omega}{(1 + j\omega/2)(1 + j\omega/10)}$$

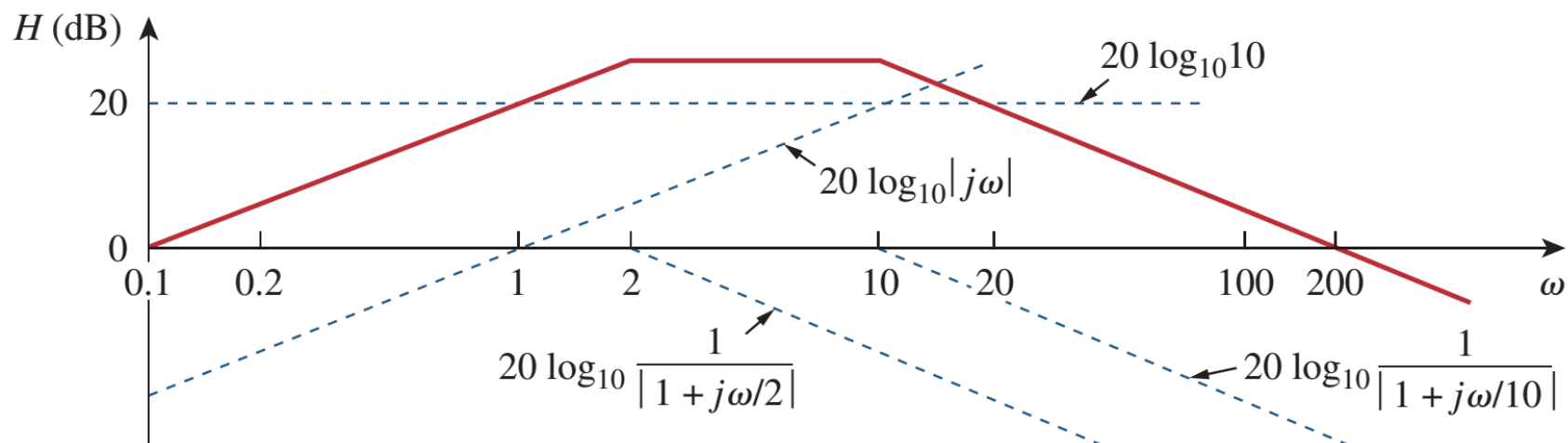Example - Magnitude

$$\mathbf{H}(\omega) = \frac{10j\omega}{(1 + j\omega/2)(1 + j\omega/10)}$$




$$H_{\text{dB}} = 20 \log_{10} 10 + 20 \log_{10} |j\omega| - 20 \log_{10} \left| 1 + \frac{j\omega}{2} \right| - 20 \log_{10} \left| 1 + \frac{j\omega}{10} \right|$$

Example - Phase

$$\begin{aligned}\mathbf{H}(\omega) &= \frac{10j\omega}{(1 + j\omega/2)(1 + j\omega/10)} \\ &= \frac{10|j\omega|}{|1 + j\omega/2||1 + j\omega/10|} \angle \frac{90^\circ - \tan^{-1} \omega/2 - \tan^{-1} \omega/10}\end{aligned}$$
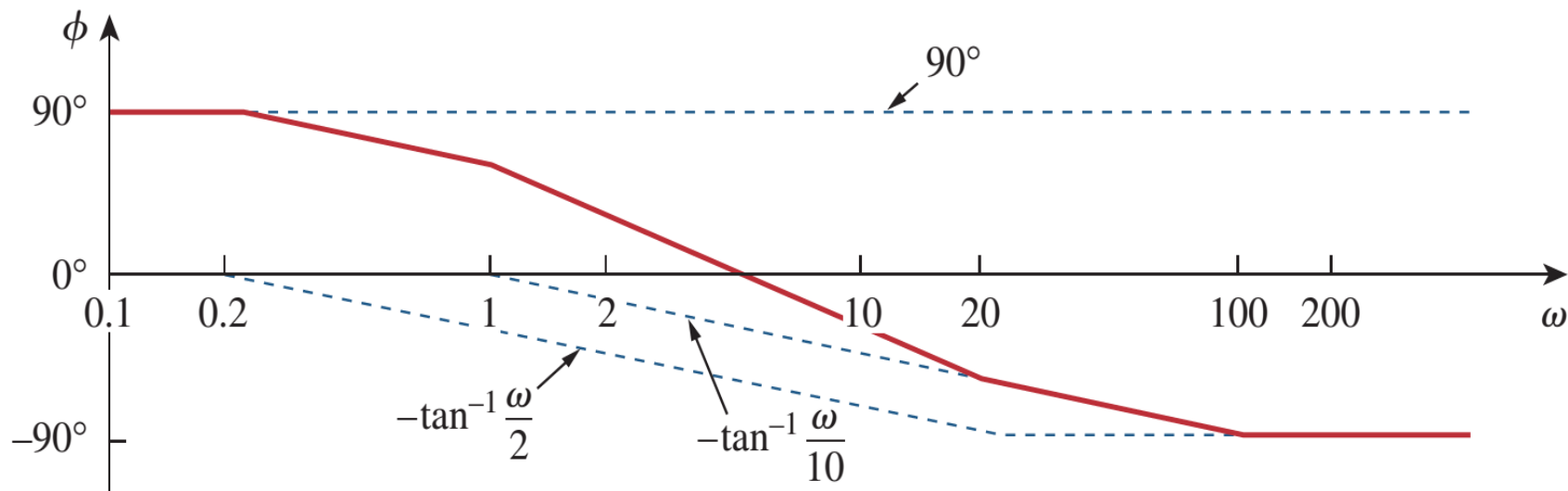
$$\phi = 90^\circ - \tan^{-1} \frac{\omega}{2} - \tan^{-1} \frac{\omega}{10}$$






Exercises

- $\mathbf{H}(\omega) = \frac{(20 + j4\omega)^2}{j40\omega(100 + j2\omega)}$
- $\mathbf{H}(\omega) = \frac{(j10\omega + 30)^2}{(300 - 3\omega^2 + j90\omega)}$




$$\mathbf{H}(\omega) = \frac{(20 + j4\omega)^2}{j40\omega(100 + j2\omega)} = \frac{\left(1 + \frac{j\omega}{5}\right)^2}{j10\omega\left(1 + \frac{j\omega}{50}\right)}$$

$|\mathbf{H}(\omega)|$ (dB)

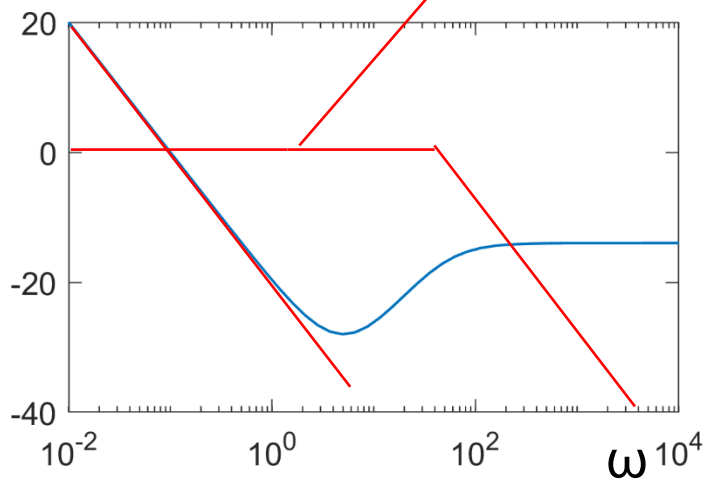



Φ (degree)

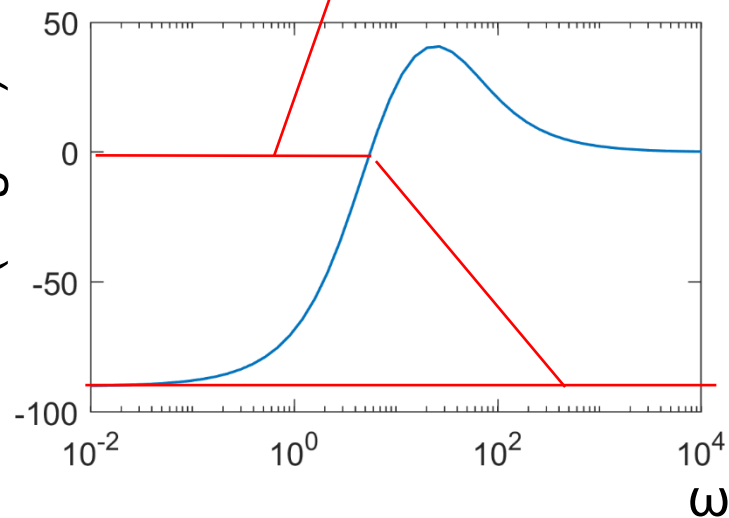




$$\mathbf{H}(\omega) = \frac{(j10\omega + 30)^2}{(300 - 3\omega^2 + j90\omega)} = \frac{3(1 + \frac{j\omega}{3})^2}{1 + j\frac{3\omega}{10} + (\frac{j\omega}{100})^2}$$

$|H(\omega)|$ (dB)

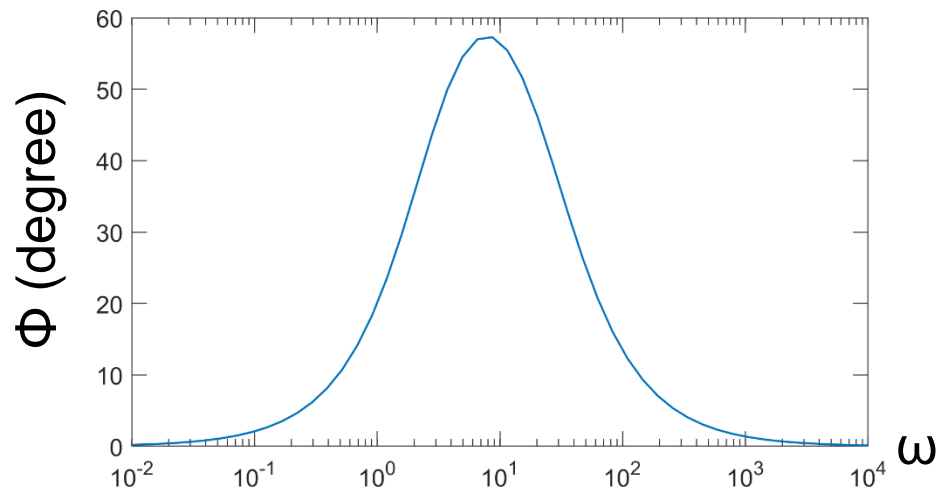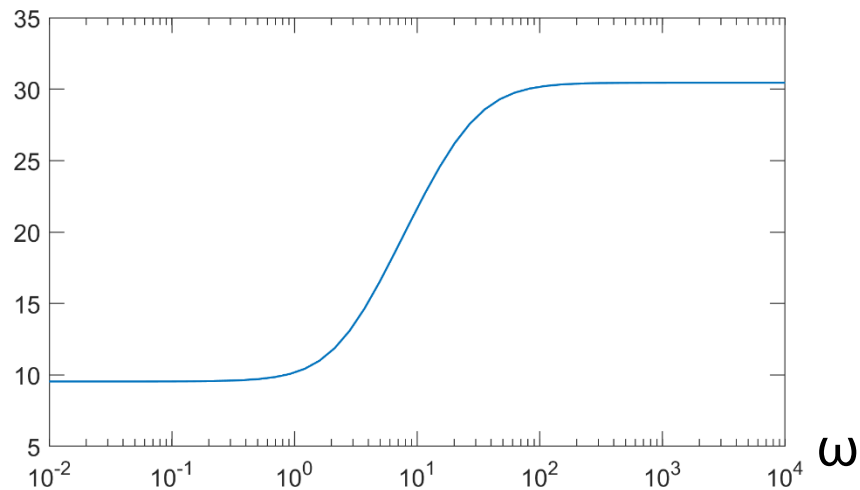

Obtain the transfer function

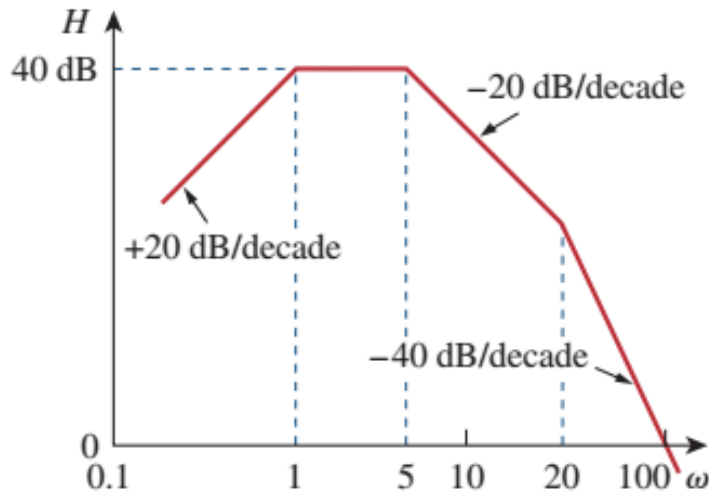Exercise: find the transfer function represented by the following plot.



$$H(\omega) = \frac{100j\omega}{(1 + j\omega)(1 + \frac{j\omega}{5})(1 + \frac{j\omega}{20})}$$



Outline

- Frequency response
- Transfer function
- Bode plots (or diagram)
- Resonance
 - Introduction
 - Series RLC (Resonance frequency, Q factor, bandwidth)
 - Parallel RLC
- Filters

What is resonance


- From Latin resonantem: to sound again, resound, re-echo
- Chinese: 共振/谐振 (describes the mechanism for resound to occur);
 - 激发信号的相位与系统响应的相位一致。
 - 激发能量的持续累积可大大增加其震荡幅度。

B_1 field
generation



$$B_0 \sim 1000000 B_1$$

核磁共振

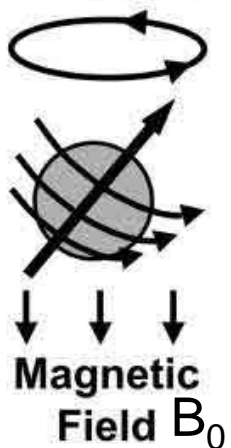

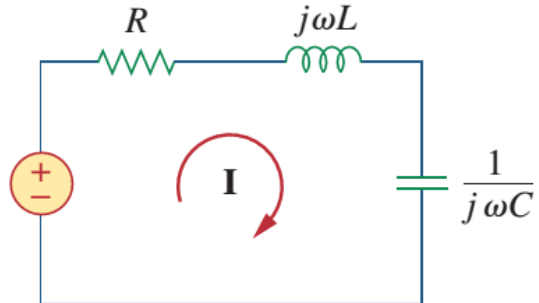
1940 Tacoma Narrows Bridge collapse



Photo Credit: Keystone/Getty Images

Series Resonance

- A series resonant circuit consists of an inductor and capacitor in series.

$$H(\omega) = \frac{V}{I} = \mathbf{Z} = R + j\left(\omega L - \frac{1}{\omega C}\right) \quad \mathbf{V}_s = V_m \angle \theta$$


- Resonance occurs when the imaginary part of Z is zero ($|Z|$ is minimum).
- The value of ω that satisfies this is called the resonant frequency.

$$\omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/s}$$




Series Resonance

- At resonance:
 - The impedance is purely resistive
 - The voltage V_s and the current I are in phase
 - The magnitude of the impedance is **minimum**
 - The inductor and capacitor voltages can be much larger than that of the source

$$|V_L| = |V_C| = \frac{V_m}{R} \frac{1}{\omega_0 C}$$

Bandwidth

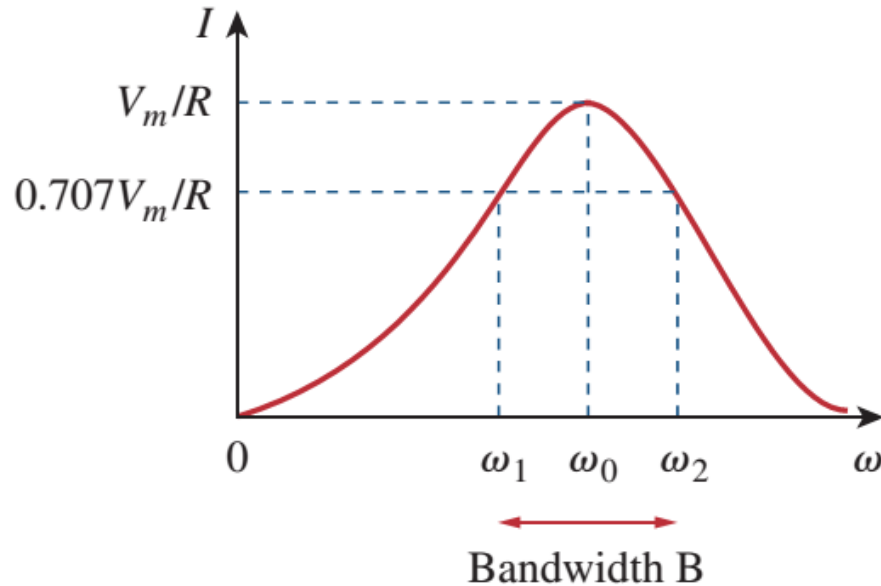

$$I = |\mathbf{I}| = \frac{V_m}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}}$$

$$P = \frac{1}{2} I^2 R = \frac{1}{2} \frac{V_m^2 R}{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

- Bandwidth: the difference between the two half-power frequencies

$$P_{\max} = \frac{1}{2} \frac{V_m^2}{R}$$

Bandwidth

$$\text{When } P = \frac{1}{2P_{\max}},$$

$$\left(\omega L - \frac{1}{\omega C}\right)^2 = R^2$$

$$\omega L - \frac{1}{\omega C} = \pm R$$

$$\omega^2 LC \mp \omega CR - 1 = 0$$

$$\omega_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$B = \omega_2 - \omega_1 = \frac{R}{L}$$


Useful relationship:

$$\omega_0 = \frac{1}{\sqrt{LC}} = \sqrt{\omega_1 \omega_2}$$

The other two solutions are negative.


Quality Factor Q

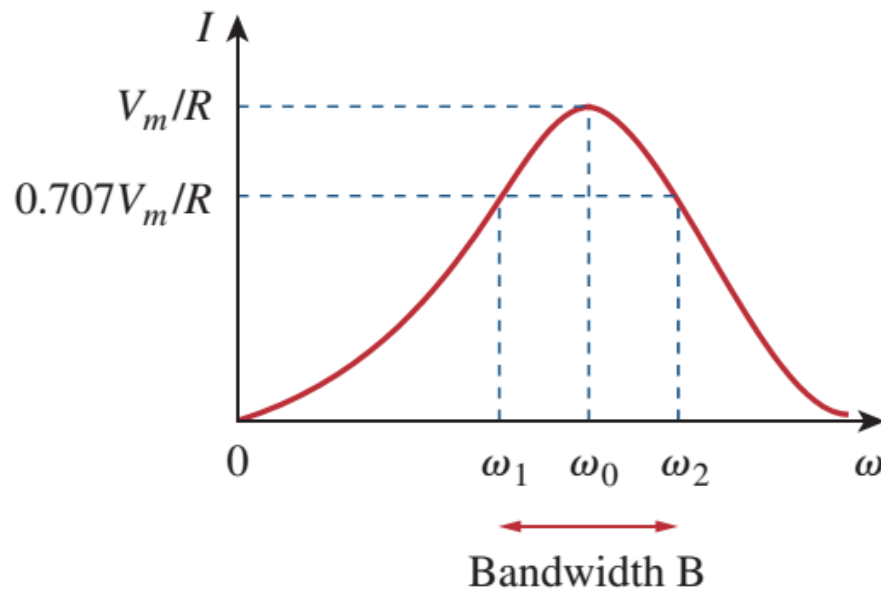- Quality factor Q : measure the “sharpness” of the resonance.



The smaller the B , the higher the Q .
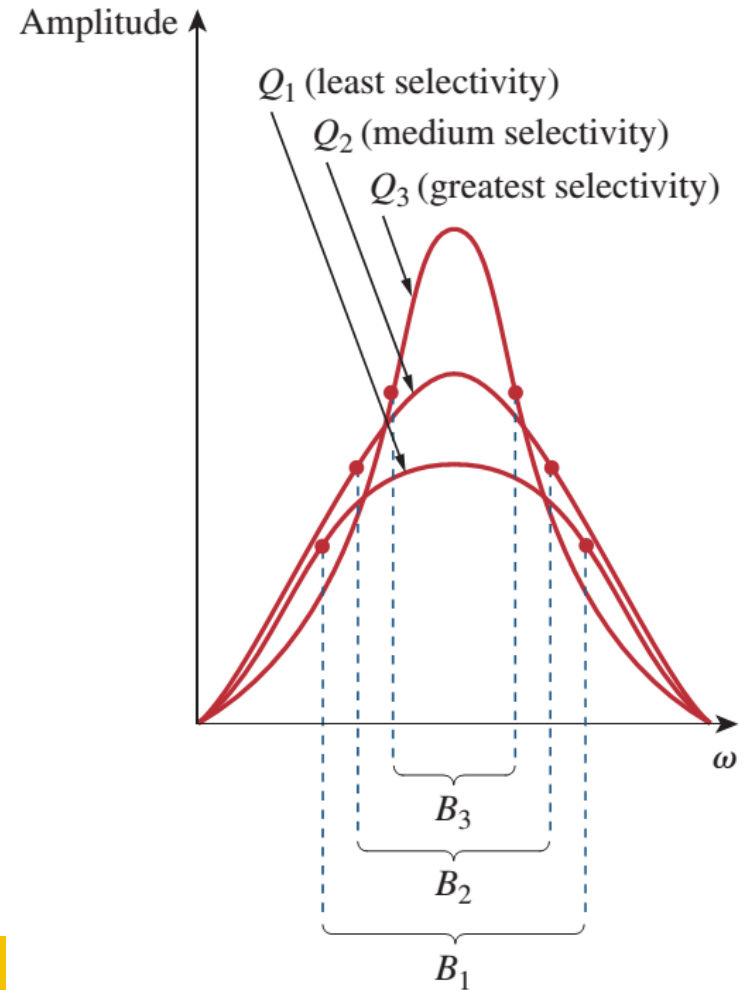
$$Q = \frac{\omega_0}{B} \quad \omega_0 = \frac{1}{\sqrt{LC}} \quad B = \omega_2 - \omega_1 = \frac{R}{L}$$



$$Q = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 C R}$$




Definition of Q in terms of energy dissipation

Q = Peak stored energy: Energy dissipated in $\frac{1}{2\pi}$ period at resonance.

$$Q = \frac{\frac{1}{2} L I^2}{\left[\left(\frac{1}{2} I^2 R \right) \frac{1}{\omega_0} \right]} = \frac{L \omega_0}{R}$$

Positions of Half-Power Frequencies

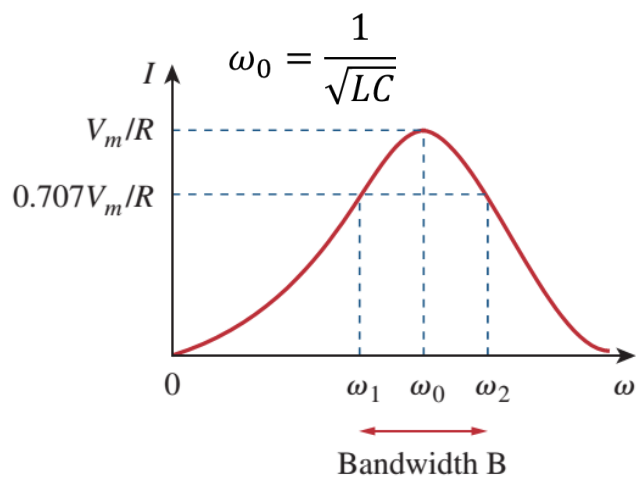

$$\omega_{1,2} = \mp \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

Note that the half power frequencies are centered around $\sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$, but not the resonance frequency ω_0 .

$$\sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} = \omega_0 \sqrt{1 + \frac{1}{4Q^2}}$$

- For high-Q ($Q \geq 10$) circuits,

$\sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \approx \omega_0$ and $\omega_{1,2} \approx \omega_0 \mp \frac{\omega_0}{2Q}$, i.e. approximately center around ω_0 .

Example

In the circuit, $R = 2\Omega$, $L = 1\text{mH}$
and $C = 0.4\mu\text{F}$


- Find resonant frequency ω_0 .
- Calculate Q and bandwidth B .
- Find half-power frequencies.
- Determine the amplitude of the current at ω_0 , ω_1 and ω_2 .

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-3} \times 0.4 \times 10^{-6}}} = 50 \text{ krad/s}$$

$$B = R/L = 2 \text{ krad/s}$$

$$Q = \frac{\omega_0}{B} = \frac{50}{2} = 25$$
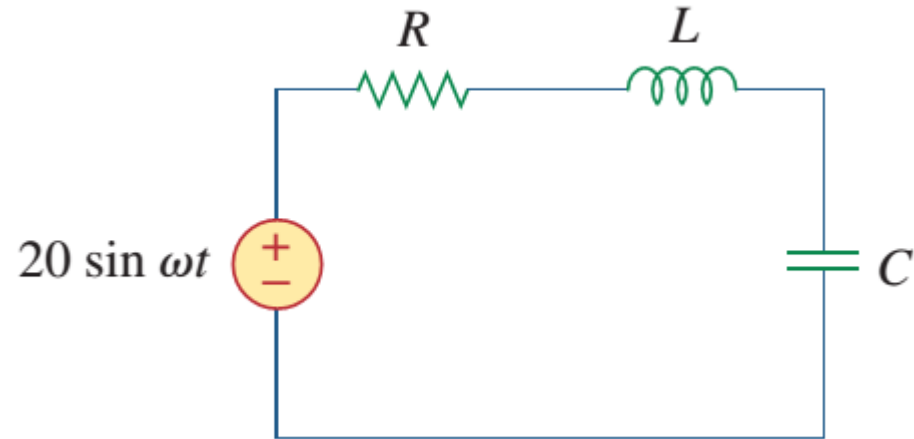
$$\omega_1 = 49 \text{ krad/s}, \omega_2 = 51 \text{ krad/s}$$





At $\omega = \omega_0$,

$$I = \frac{V_m}{R} = \frac{20}{2} = 10 \text{ A}$$

At $\omega = \omega_1, \omega_2$,

$$I = \frac{V_m}{\sqrt{2}R} = \frac{10}{\sqrt{2}} = 7.071 \text{ A}$$

Parallel resonance

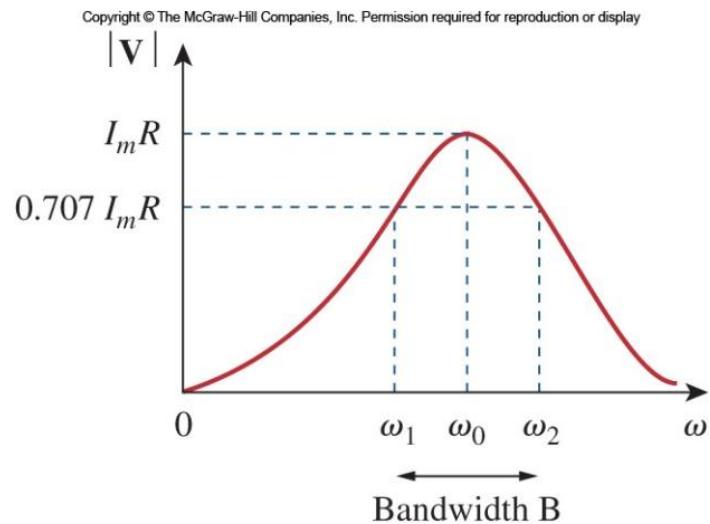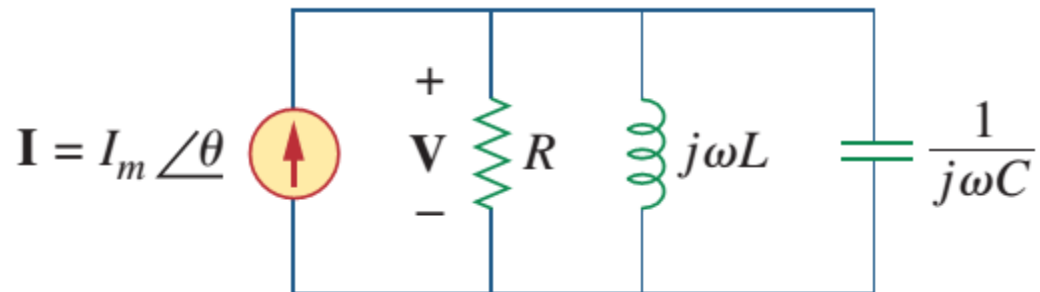

Parallel resonance

Parallel circuit

$$Y = \frac{1}{R} + j\omega C + \frac{1}{j\omega L} \quad V = \frac{I}{Y}, \quad P = \frac{V^2}{R}$$


Series circuit

$$Z = R + j\omega L + \frac{1}{j\omega C} \quad I = \frac{V}{Z}, \quad P = RI^2$$

We can get the results for parallel resonance after the following replacements in the series resonance results

$$R \rightarrow 1/R; \quad L \rightarrow C; \quad C \rightarrow L, \quad I \rightarrow V, \quad V \rightarrow I$$

RLC Circuit

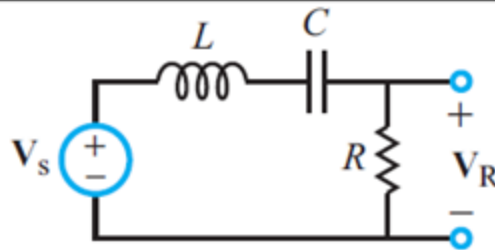

Transfer Function

$$H = \frac{V_R}{V_s}$$

Resonant Frequency, ω_0

$$\frac{1}{\sqrt{LC}}$$

Bandwidth, B

$$\frac{R}{L}$$

Quality Factor, Q


$$\frac{\omega_0}{B} = \frac{\omega_0 L}{R}$$

Lower Half-Power Frequency, ω_1

$$\left[-\frac{1}{2Q} + \sqrt{1 + \frac{1}{4Q^2}} \right] \omega_0$$


Upper Half-Power Frequency, ω_2
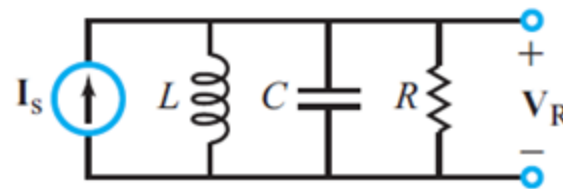
$$\left[\frac{1}{2Q} + \sqrt{1 + \frac{1}{4Q^2}} \right] \omega_0$$



$$H = \frac{V_R}{I_s}$$

RLC Circuit

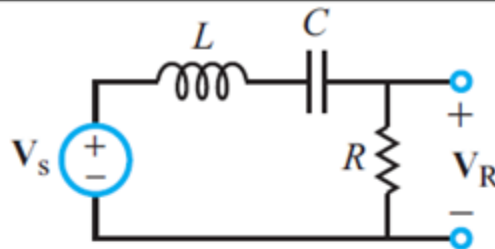

Transfer Function

$$H = \frac{V_R}{V_s}$$

Resonant Frequency, ω_0

$$\frac{1}{\sqrt{LC}}$$

Bandwidth, B

$$\frac{R}{L}$$

Quality Factor, Q


$$\frac{\omega_0}{B} = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 RC}$$

Lower Half-Power Frequency, ω_1

$$\left[-\frac{1}{2Q} + \sqrt{1 + \frac{1}{4Q^2}} \right] \omega_0$$

Upper Half-Power Frequency, ω_2
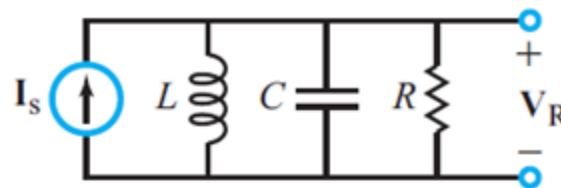
$$\left[\frac{1}{2Q} + \sqrt{1 + \frac{1}{4Q^2}} \right] \omega_0$$



$$H = \frac{V_R}{I_s}$$

$$\frac{1}{\sqrt{LC}}$$

$$\frac{1}{RC}$$

$$\frac{\omega_0}{B} = \omega_0 RC = \frac{R}{\omega_0 L}$$

$$\left[-\frac{1}{2Q} + \sqrt{1 + \frac{1}{4Q^2}} \right] \omega_0$$


$$\left[\frac{1}{2Q} + \sqrt{1 + \frac{1}{4Q^2}} \right] \omega_0$$

Notes: (1) The expression for Q of the series RLC circuit is the inverse of that for Q of the parallel circuit. (2) For $Q \geq 10$, $\omega_1 \simeq \omega_0 - \frac{B}{2}$, and $\omega_2 \simeq \omega_0 + \frac{B}{2}$.



Resonance frequency of RF coil (transmit mode)

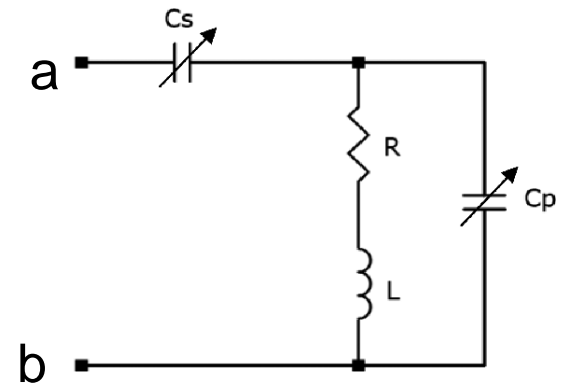The following is the equivalent circuit of an MRI coil, find the resonance frequency of the coil.



Solution

$$Z = -j \frac{1}{\omega C_s} + \frac{R + j\omega L}{j\omega C_p R - \omega^2 C_p L + 1}$$

$$\text{Im}(Z) = -\frac{1}{\omega C_s} + \frac{-\omega C_p R^2 + (1 - \omega^2 C_p L)\omega L}{(1 - \omega^2 C_p L)^2 + (\omega C_p R)^2} = 0$$

$$(1 - \omega^2 C_p L)^2 + (\omega C_p R)^2 = (1 - \omega^2 C_p L)\omega^2 L C_s - \omega^2 C_s C_p R^2$$


$$C_p(C_p + C_s)L^2\omega^4 + (C_p^2 R^2 + C_p C_s R^2 - L C_s - 2L C_p)\omega^2 + 1 = 0$$

When $C_p^2 R^2 + C_p C_s R^2 \ll L C_s + 2L C_p$, $\omega_{res} \approx 1/\sqrt{L(C_p + C_s)}$


$$\text{Re}(Z) = \frac{1 - 2\omega^2 C_p R L}{(1 - \omega^2 C_p L)^2 + (\omega C_p R)^2} R.$$

At resonance, $\text{Re}(Z) \approx (1 + \frac{C_p}{C_s})^2$, when $(\omega C_p R)^2 \ll 1$.

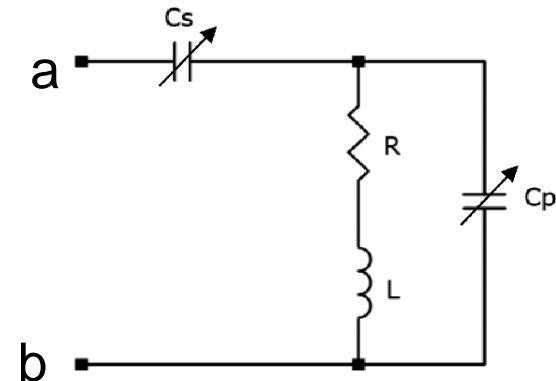One can adjust C_s and C_p values to make the circuit resonate at a specific frequency with equivalent impedance at terminals a - b matched to that of the cable (typically 50 Ω).



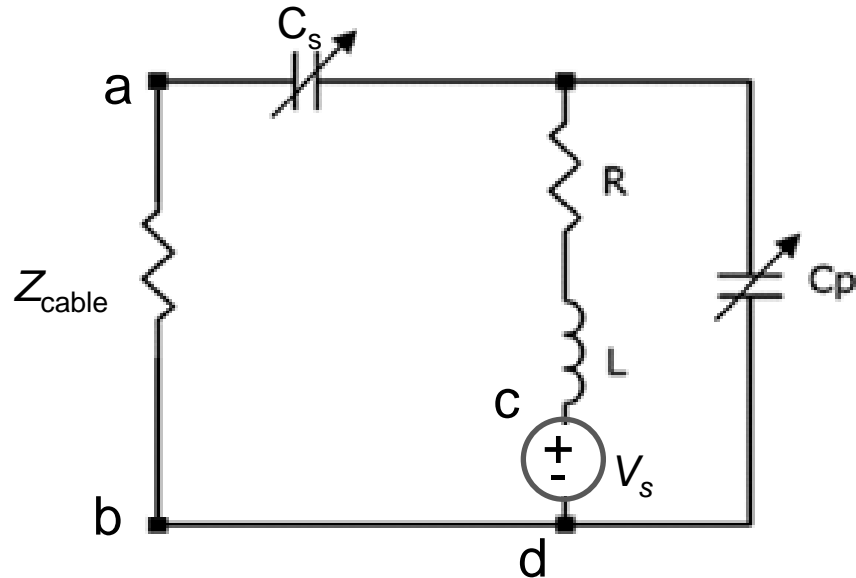Resonance frequency of RF coil (receive mode)



One can show that when the circuit resonates at frequency f with impedance matched with the cable impedance at terminal a-b. It is also on resonance at frequency f in the receive mode, i.e. the equivalent impedance at the two terminals of V_s is real.

Therefore, the same coil can be used as an efficient receiver coil.

When impedance matched, $Z_{\text{cable}} = \frac{R(1-2\omega^2 C_p R L)}{(1-\omega^2 C_p L)^2 + (\omega C_p R)^2}$

$$Z_{cd} = R + j\omega L + \frac{(-j\frac{1}{\omega C_s} + Z_{\text{cable}})(-j\frac{1}{\omega C_p})}{-j\frac{1}{\omega C_s} + Z_{\text{cable}} - j\frac{1}{\omega C_p}}.$$


One can show that $\text{Im}(Z_{cd}) = 0$ at resonance frequency ω_{res} , where ω_{res} is the frequency that satisfies $\text{Im}(Z) = 0$ in the transmit mode.



Summary

$$H(\omega) = \frac{K(j\omega)^{\pm 1} (1 + j\omega/z_1)[1 + j2\zeta_1\omega/\omega_k + (j\omega/\omega_k)^2]\cdots}{(1 + j\omega/p_1)[1 + j2\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2]\cdots}$$

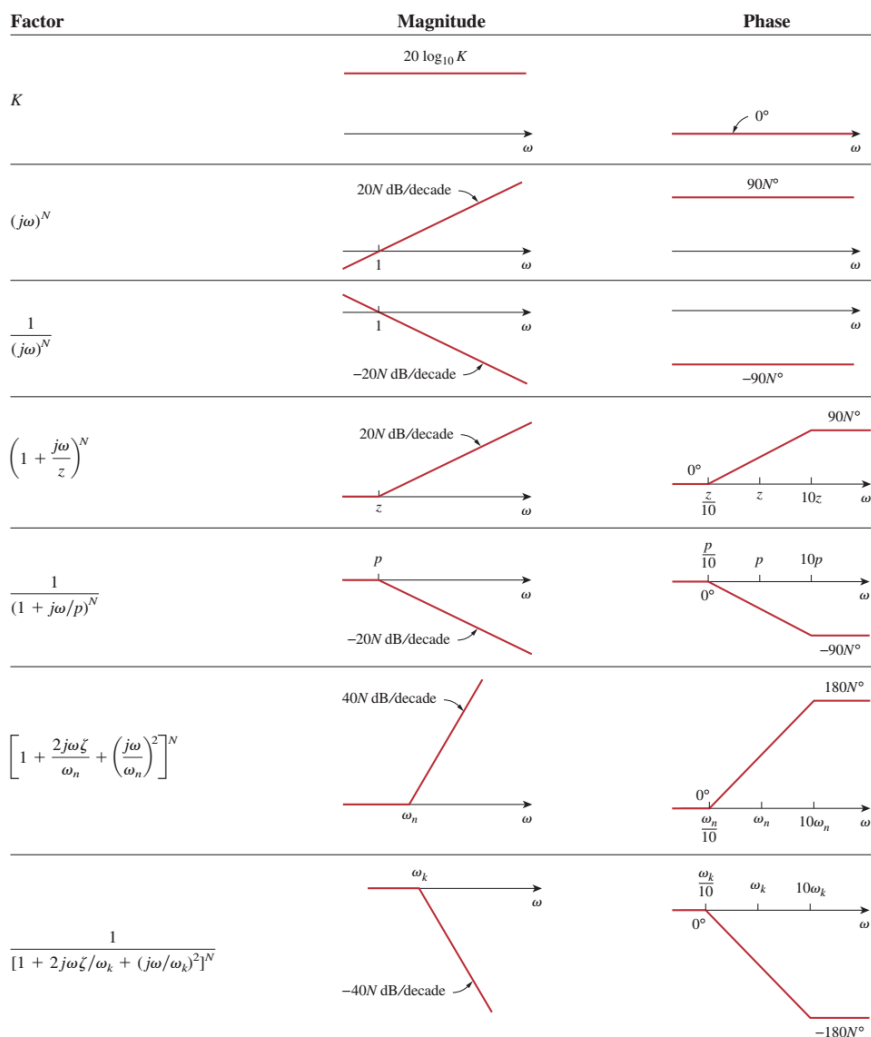Summary of Bode straight-line magnitude and phase plots.




Power P in decibels = $10 \log_{10} \frac{P}{P_{\text{reference}}}$

$H(\omega)$ in decibels = $20 \log_{10}(|H(\omega)|)$

Resonance condition: $\text{Im}(Z) = 0$

RLC Circuit

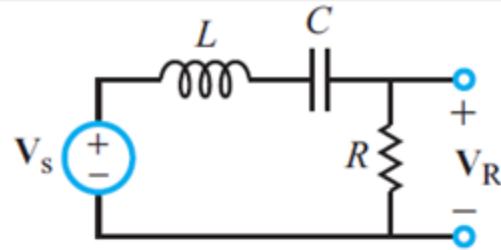

Transfer Function

$$H = \frac{V_R}{V_s}$$

Resonant Frequency, ω_0

$$\frac{1}{\sqrt{LC}}$$

Bandwidth, B

$$\frac{R}{L}$$

Quality Factor, Q


$$\frac{\omega_0}{B} = \frac{\omega_0 L}{R}$$

Lower Half-Power Frequency, ω_1

$$\left[-\frac{1}{2Q} + \sqrt{1 + \frac{1}{4Q^2}} \right] \omega_0$$

Upper Half-Power Frequency, ω_2
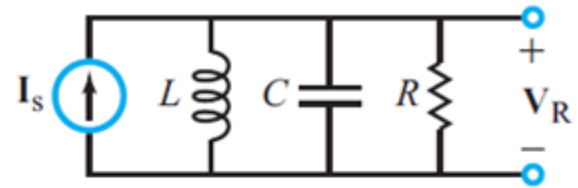
$$\left[\frac{1}{2Q} + \sqrt{1 + \frac{1}{4Q^2}} \right] \omega_0$$



$$H = \frac{V_R}{I_s}$$

$$\frac{1}{\sqrt{LC}}$$

$$\frac{1}{RC}$$


$$\frac{\omega_0}{B} = \frac{R}{\omega_0 L}$$

$$\left[-\frac{1}{2Q} + \sqrt{1 + \frac{1}{4Q^2}} \right] \omega_0$$


$$\left[\frac{1}{2Q} + \sqrt{1 + \frac{1}{4Q^2}} \right] \omega_0$$

RF coil

Transmit mode

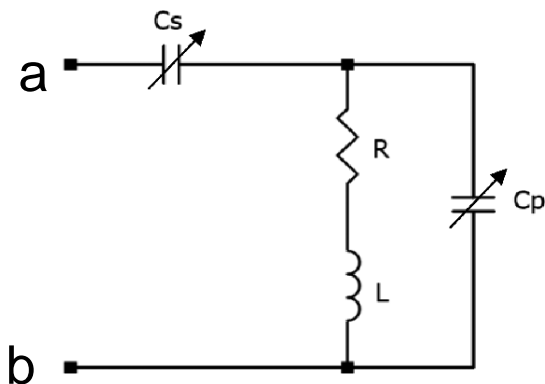

Receive mode

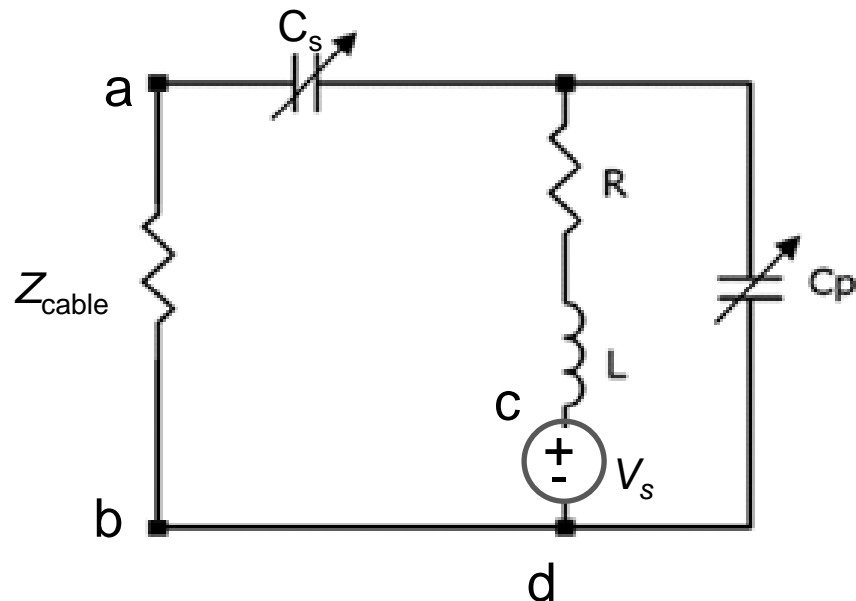

$\omega_{res} \approx \frac{1}{\sqrt{L(C_p + C_s)}}$ in both case when R is small, i.e.

$$C_p^2 R^2 + C_p C_s R^2 \ll LC_s + 2LC_p$$

$$R \ll \sqrt{\frac{LC_s + 2LC_p}{C_p(C_p + C_s)}}$$