



Chapter 5

- Operational Amplifiers



Outline

- Operational amplifier (op amp)
- Basic operations
- DAC
- Instrumentation amplifier






The Op Amp

- Behaves like a voltage-controlled voltage source with very high amplification factor
- When combined with resistors, capacitors, and inductors, can perform various functions:
 - amplification/scaling
 - sign changing
 - addition/subtraction
 - integration
 - differentiation
 - analog filtering

Op Amp Terminals

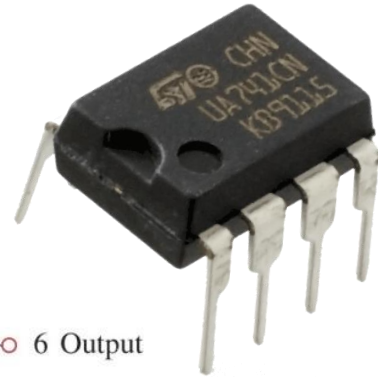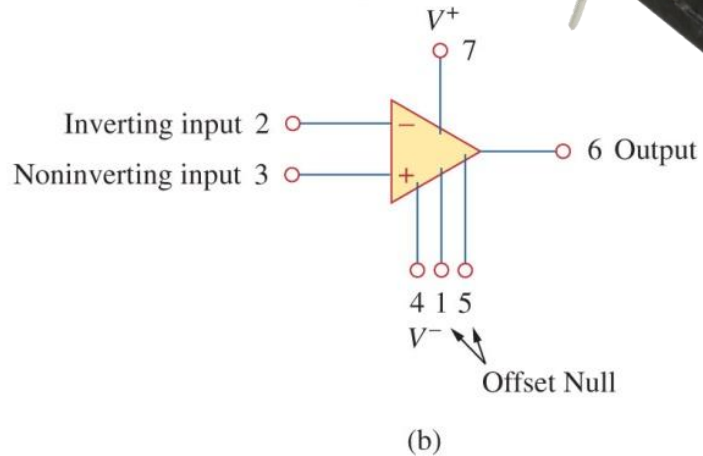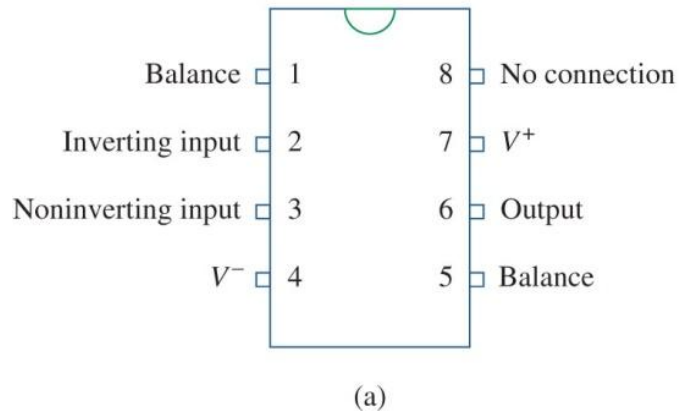Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



- Five important terminals

- The inverting input
- The noninverting input
- The output
- The positive (+) power supply
- The negative (-) power supply


- The rest three terminals

- 2 Offset Null (Balance)
 - May be used to compensate for performance degradation due to aging etc.
- 1 No Connection (NC)
 - Unused, not connected to the amplifier circuit.

Output Voltage

- The voltage output of an op-amp is proportional to the difference between the noninverting and inverting inputs

$$v_o = A v_d = A(v_2 - v_1)$$

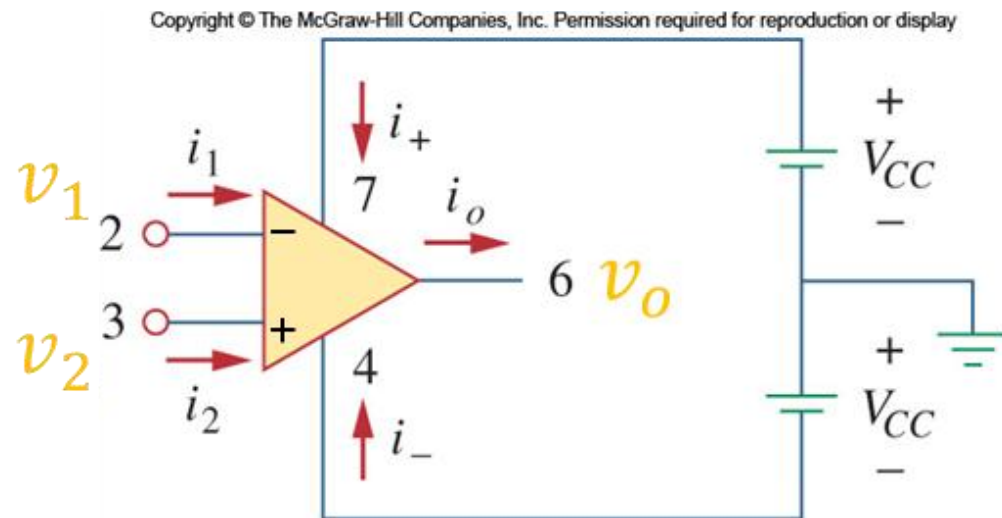

Op Amp in the real world

$$v_o = A_d(v_2 - v_1) + A_c(v_2 + v_1)/2$$


共模抑制比: $\frac{A_d}{A_c}$ or $20 \log_{10} \frac{A_d}{A_c}$ (dB)



The circuit diagram illustrates a precision rectifier. It features two op-amp comparators and a differential amplifier. The first comparator's non-inverting input is connected to V_{CC+} and its inverting input to $IN+$. The second comparator's non-inverting input is connected to V_{CC+} and its inverting input to $IN-$. The outputs of these comparators are connected to the inputs of a differential amplifier. The differential amplifier's non-inverting input is connected to V_{CC+} and its inverting input to V_{CC-} . The output of the differential amplifier is connected to OUT . The circuit also includes several resistors and a capacitor for timing or filtering.

Copyright © 2017, Texas Instruments Incorporated

Equivalent Circuit of an Op Amp


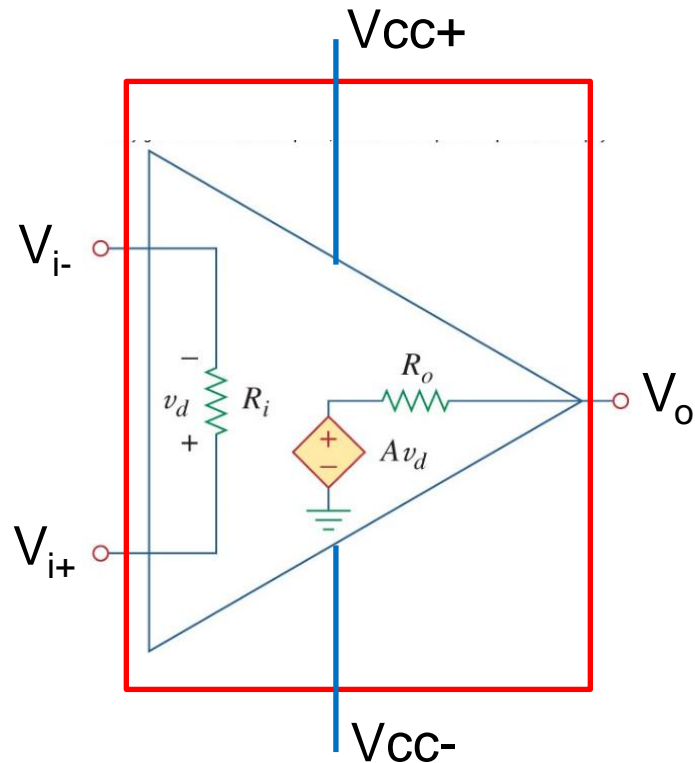


The total current into the three terminals (V_{i+} , V_{i-} , and V_o) of an amp is nonzero.

KCL can still be applied to each node, but not to the model circuit as a whole (the red box) because V_{CC+} and V_{CC-} are not part of the model circuit.

Voltage Saturation

- Is the output voltage unlimited?

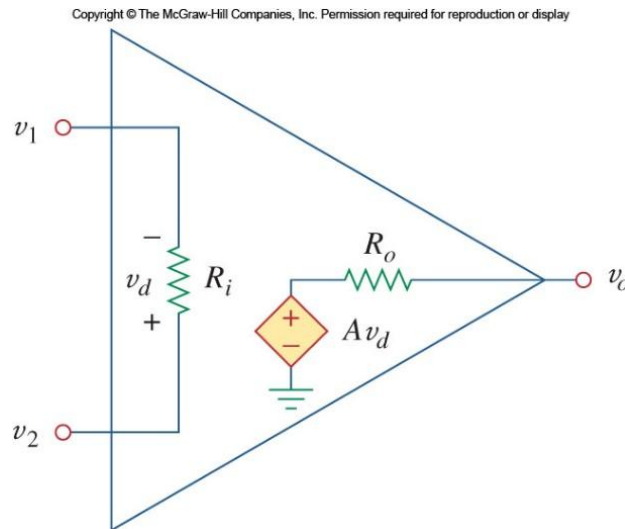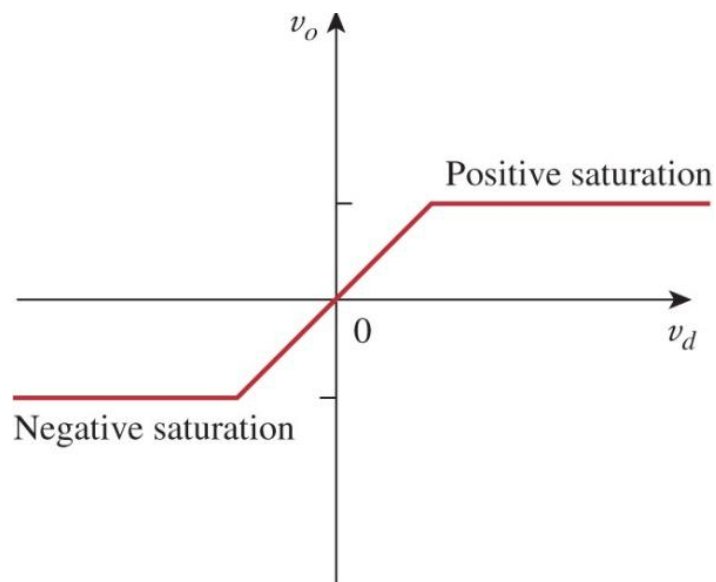

$$v_o = A v_d = A(v_2 - v_1)$$

6.4 Electrical Characteristics: $\mu A741C$


at specified virtual junction temperature, $V_{CC\pm} = \pm 15\text{ V}$ (unless otherwise noted)

V_{OM}	Maximum peak output voltage swing	$R_L = 10\text{ k}\Omega$	25°C	± 12	± 14	V
		$R_L \geq 10\text{ k}\Omega$	Full range	± 12		
		$R_L = 2\text{ k}\Omega$	25°C	± 10		
		$R_L \geq 2\text{ k}\Omega$	Full range	± 10		



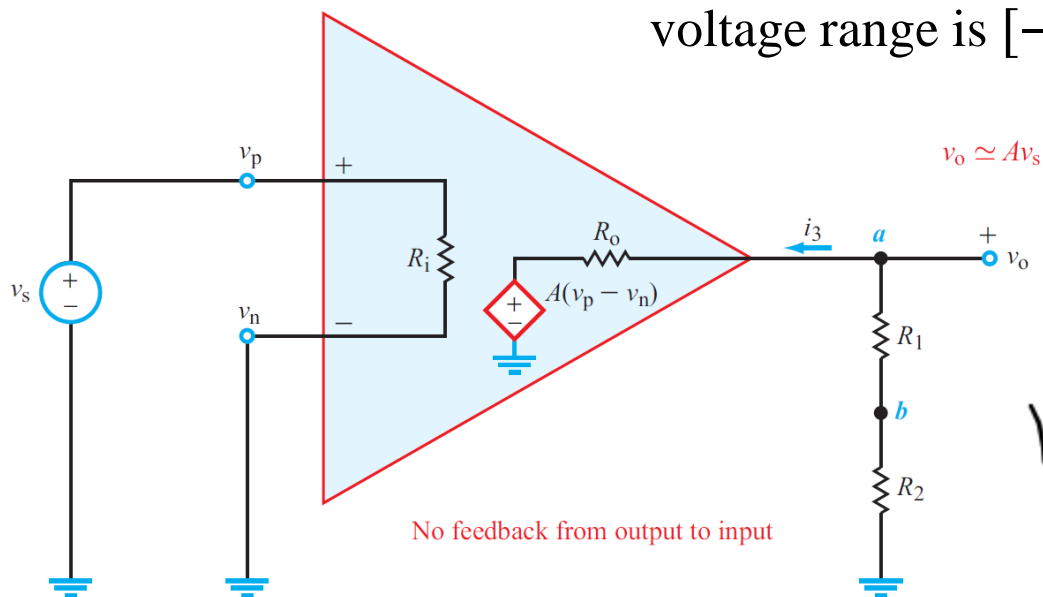Example 1

For $V_{cc} = 10\text{ V}$, $A = 10^6$, $R_i = 10^7\ \Omega$, $R_o = 10\ \Omega$, $R_1 = 80\text{ k}\Omega$, and $R_2 = 20\text{ k}\Omega$, find v_o , assuming the output voltage range is $[-V_{cc}, V_{cc}]$.



$$V_o = A V_s \cdot \frac{R_1 + R_2}{R_o + R_1 + R_2}$$

$$= 0.9999 A V_s$$

$$\approx 10^6 V_s$$

$$\approx 10\text{ V}$$

$$-10\text{ V}$$



$$V_s \leq 10\text{ mV}$$

$$V_s \geq 10\text{ mV}$$

$$V_s < -10\text{ mV}$$

假设输出电压的工作范围为

Feedback

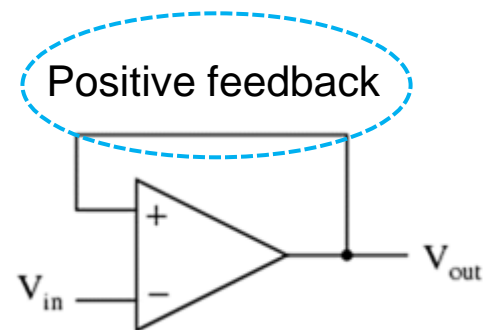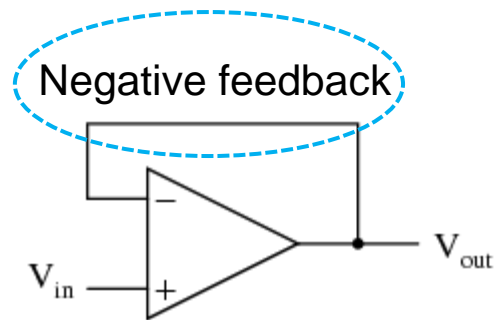

$V_{out} \uparrow \Rightarrow \text{voltage difference} \downarrow \Rightarrow V_{out} \downarrow$

$V_{out} \uparrow \Rightarrow \text{voltage difference} \uparrow \Rightarrow V_{out} \uparrow$


负反馈：当输出端电压变化通过外部电路反馈至输入端时，反馈信号引起的输出端电压变化方向与原变化方向相反且通常幅度更大，从而能抵消输出电压的变化，维持输出电压稳定。

正反馈：当输出端电压变化通过外部电路反馈至输入端时，反馈信号引起的输出端电压变化方向与原变化方向相同，从而加剧输出电压的变化。



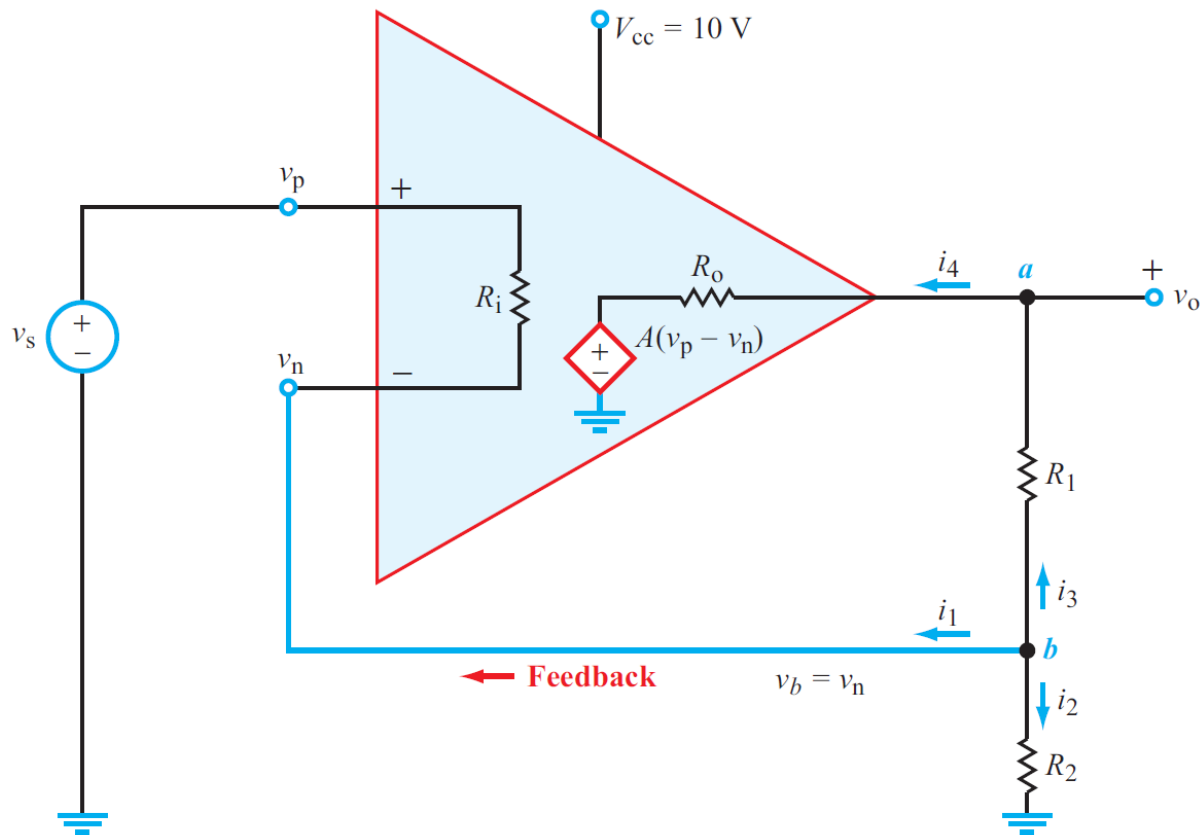Example 2

For $V_{cc} = 10\text{ V}$, $A = 10^6$, $R_i = 10^7\ \Omega$, $R_o = 10\ \Omega$,
 $R_1 = 80\text{ k}\Omega$, and $R_2 = 20\text{ k}\Omega$, Find v_o/v_s





Example 2 (solution)

$$n = 5 \quad \left. \begin{array}{l} \\ n_{V_S} = 2 \end{array} \right\} \therefore 2 \text{ independent voltage}$$

$$\frac{V_b - V_o}{R_1} + \frac{V_b}{R_2} + \frac{(V_b - V_s)}{R_i} = 0$$

$$\frac{V_b - V_o}{R_1} - \frac{V_o - A(V_s - V_b)}{R_o} = 0$$

$$\begin{pmatrix} -\frac{1}{R_1} & \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_i} \\ -\frac{1}{R_1} - \frac{1}{R_o} & \frac{1}{R_1} - \frac{A}{R_o} \end{pmatrix} \begin{pmatrix} V_o \\ V_b \end{pmatrix} + \begin{pmatrix} -\frac{V_s}{R_i} \\ \frac{AV_s}{R_o} \end{pmatrix} = 0$$

$$Mx + b = 0 \quad x = -M^{-1} \cdot b$$


$$\begin{aligned} V_o &= +V_s \frac{A R_i (R_1 + R_2) + R_2 R_o}{R_i (A R_2 + R_1 + R_2 + R_o) + R_1 R_2 + R_2 R_o} \\ &\approx V_s \frac{A R_i (R_1 + R_2)}{A R_i R_2} = V_s \frac{R_1 + R_2}{R_2} \\ &= 5V_s \end{aligned}$$

$$V_s = V_o \cdot \frac{R_2}{R_1 + R_2}$$

注意：当 $A = -10^6$ 时（正反馈），同样可以得到 $V_s \approx V_o \frac{R_2}{R_1 + R_2}$ ，但此时电压不稳定。

Attributes of an Ideal Op Amp

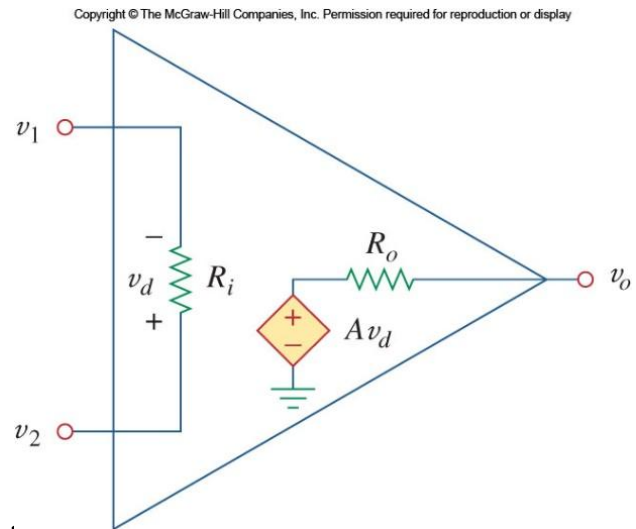- ✓ infinite input resistance: $R_i \approx \infty \Omega$
- ✓ infinite open-loop gain: $A \cong \infty$
- ✓ zero output impedance: $R_o \approx 0 \Omega$ (not necessary for applying the golden rules)




Ideal Op-Amp Analysis

When there exists negative feedback,

Property 1: Gain is infinite \Rightarrow The **potential** between the op-amp input terminals, $v_{(+)} - v_{(-)}$, equals **zero**.

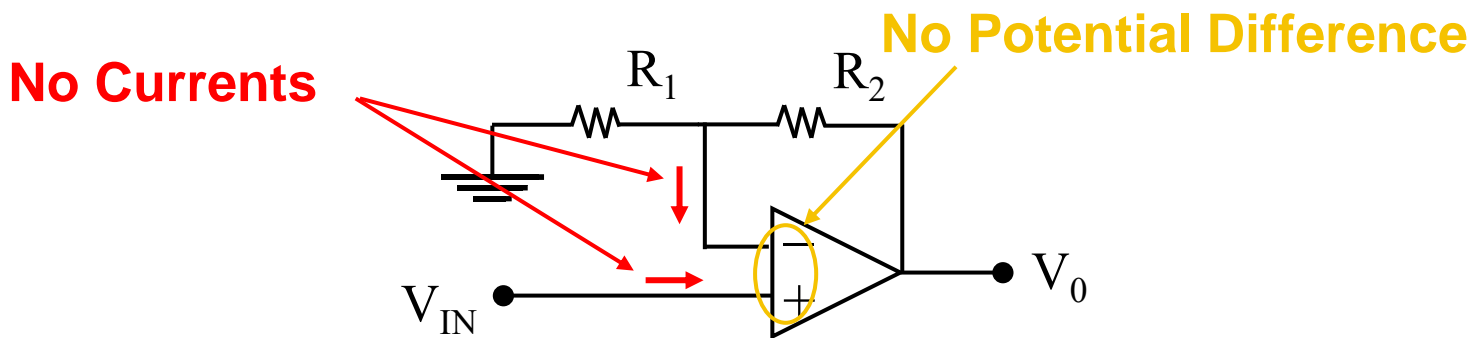Property 2: Input resistance is infinite \Rightarrow The **currents** flowing into the op-amp's two input terminals both equal **zero**.




Property 1 introduces an additional equation which replaces the KCL equation at the output node.




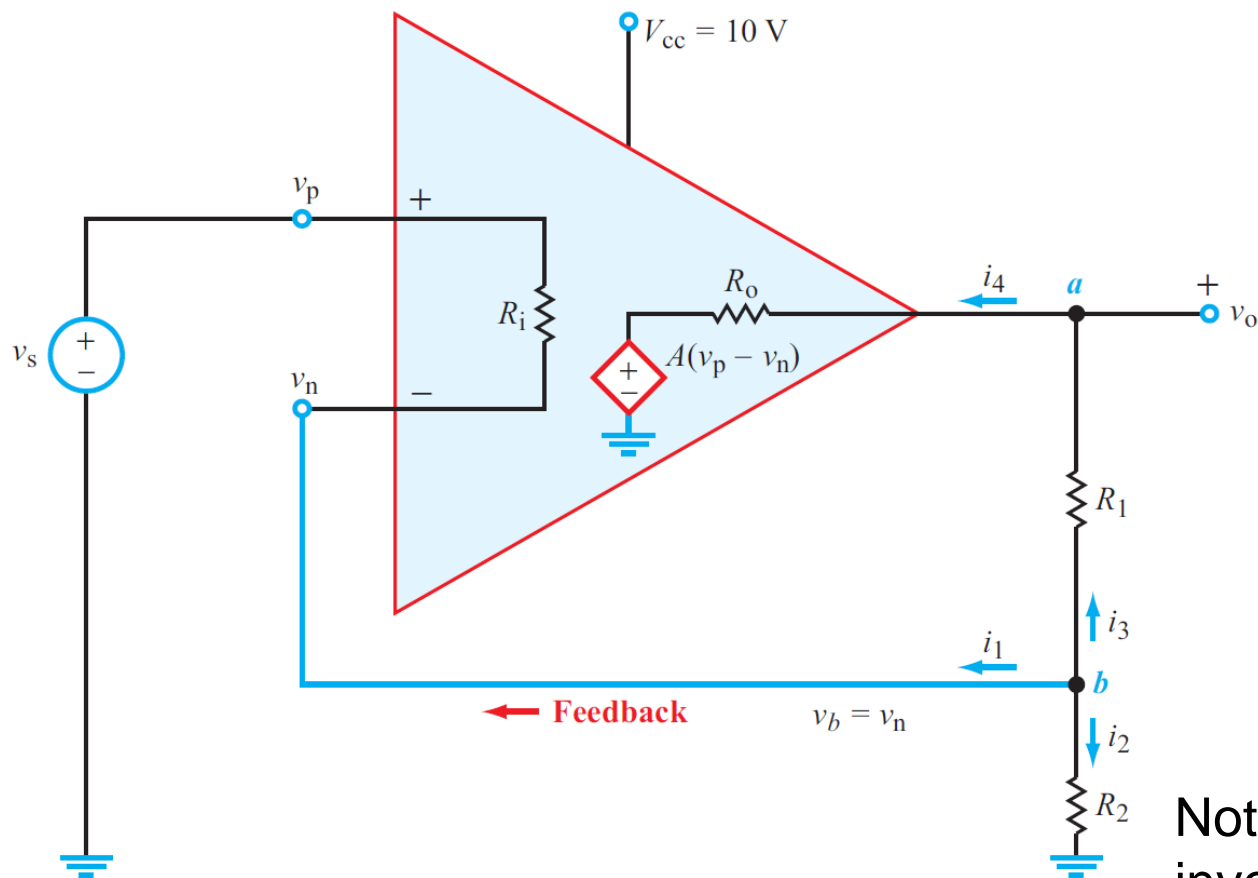Example 3

For $V_{cc} = 10\text{ V}$, $A = 10^6$, $R_i = 10^7\ \Omega$, $R_o = 10\ \Omega$,
 $R_1 = 80\text{ k}\Omega$, and $R_2 = 20\text{ k}\Omega$, Find v_o/v_s



Equivalent circuit

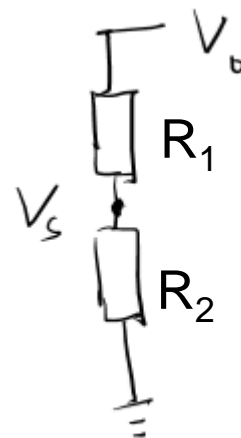

$$V_s = V_o \cdot \frac{R_2}{R_1 + R_2}$$

Note: there is no involvement of R_o in the analysis.




Outline

- Operational amplifier (op amp)
- Basic operations
 - sign changing
 - amplification/scaling
 - addition/subtraction
 - integration
 - differentiation
 - analog filtering
- DAC
- Instrumentation amplifier



Inverting Amplifier

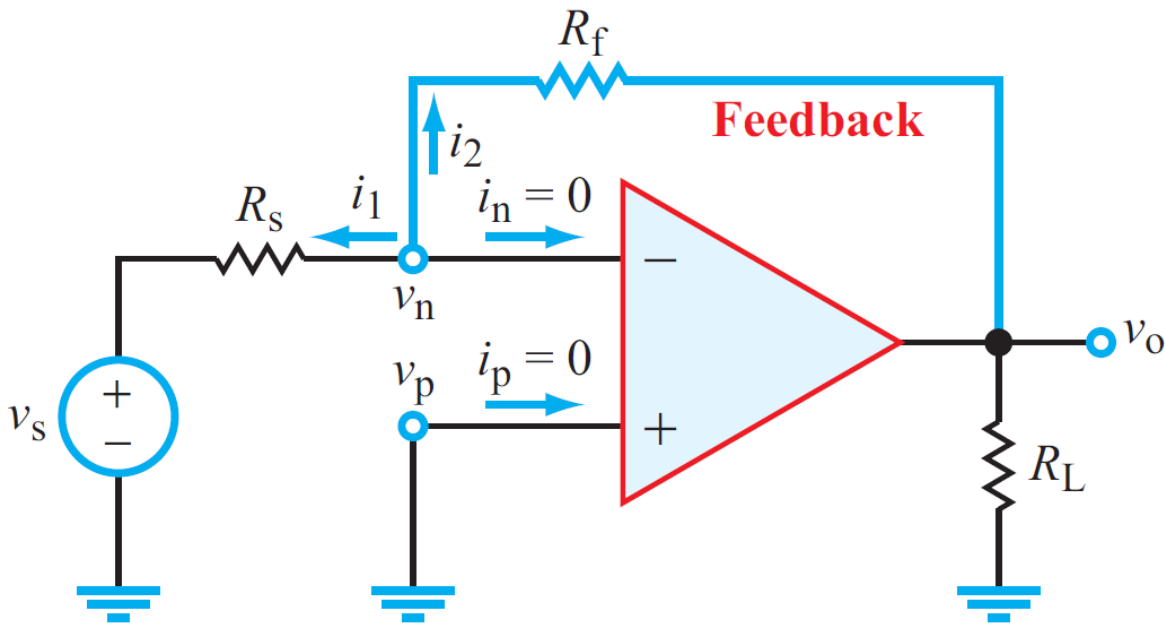


Apply KCL at node $-$,

we have

$$\frac{v_o}{R_f} = -\frac{v_s}{R_s}$$

$$v_o = -\frac{R_f}{R_s} v_s$$

Non-inverting Amplifier

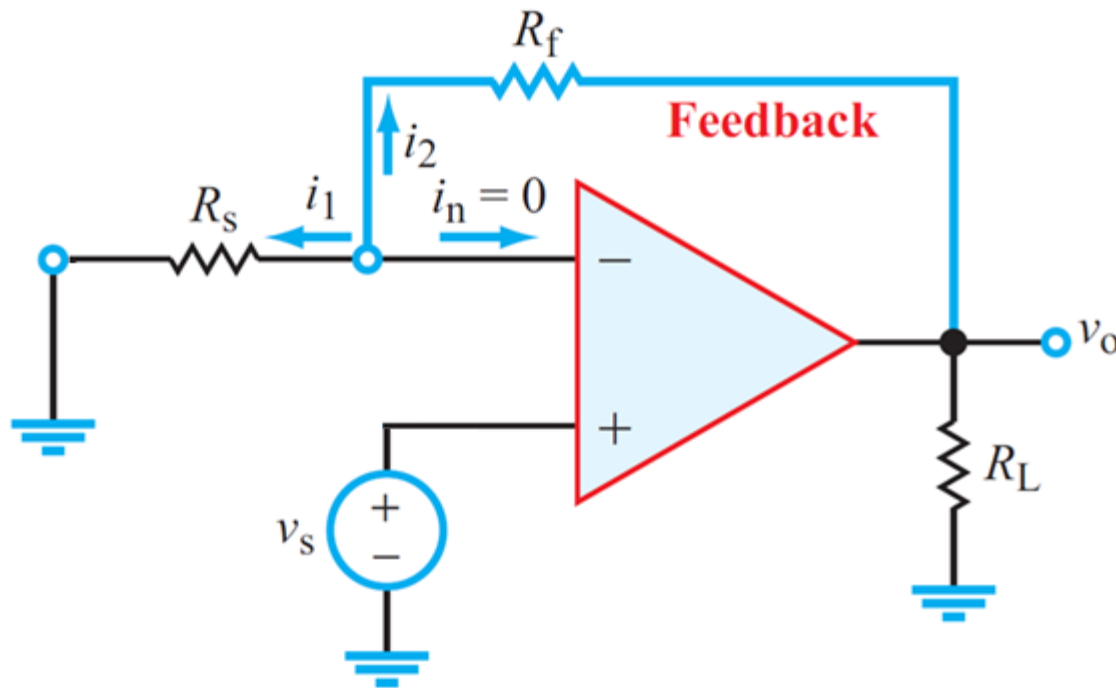

Apply KCL at node -,
we have

$$\frac{v_s - v_o}{R_f} + \frac{v_s}{R_s} = 0$$


$$v_o = v_s \left(1 + \frac{R_f}{R_s} \right)$$

When $R_f = 0$ and $R_s = \infty$, we get $v_o = v_s$, i.e. a voltage follower.



Application: Voltage Follower

Voltage follower

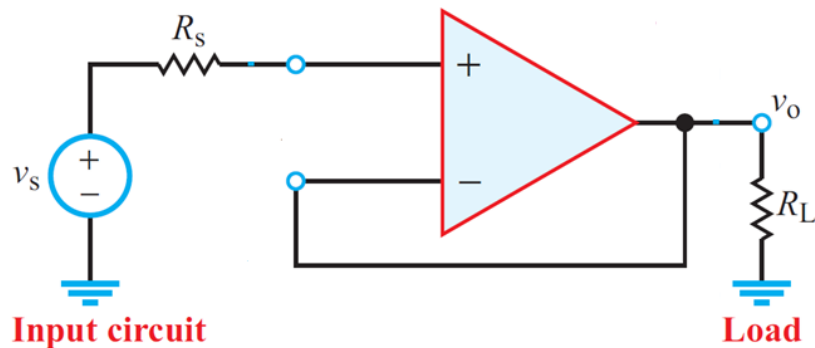

Direct connection



Equivalent Thevenin circuit:

Input side: $V_{Th}=V_s$; $R_{Th} \approx R_s$, load ∞

Output side: $V_{Th}=V_s$; $R_{Th} \approx 0$, load R_L

Equivalent Thevenin circuit:


$V_{Th}=V_s$; $R_{Th} = R_s$, load R_L



Practice 1

- Determine v_o in the circuit shown below

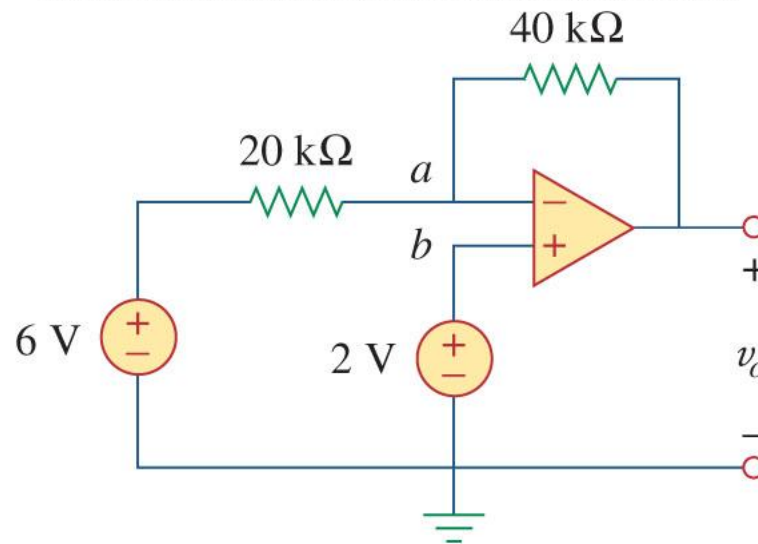
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



Answer: $(V_o - 2)/40 = -4/20$; $V_o = -6$ V;

Practice 2

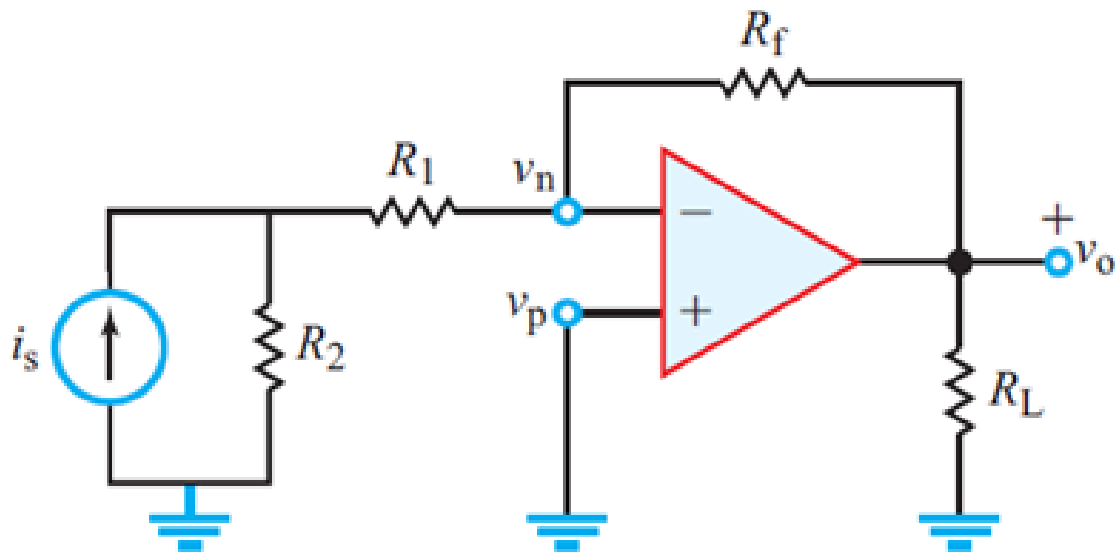- Determine v_o in the circuit shown below.




$$V_o/R_f = -[(i_s * R_2)/(R_1 + R_2)]$$

右边[..]内可理解为：
并联电路分流或
电源等效变换后串联电路的电流



Summing Amplifier

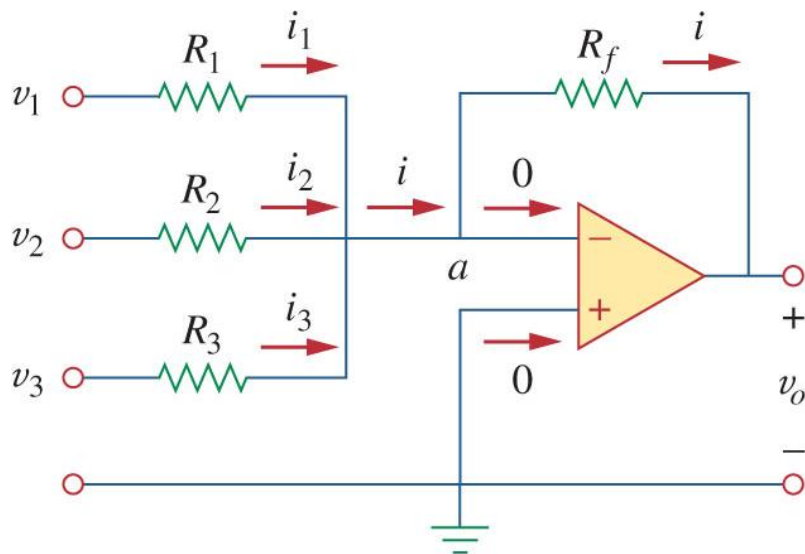- Aside from amplification, the op-amp can be made to do addition readily.




$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} = \frac{-V_o}{R_f}$$

$$V_o = -R_f \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

Practice

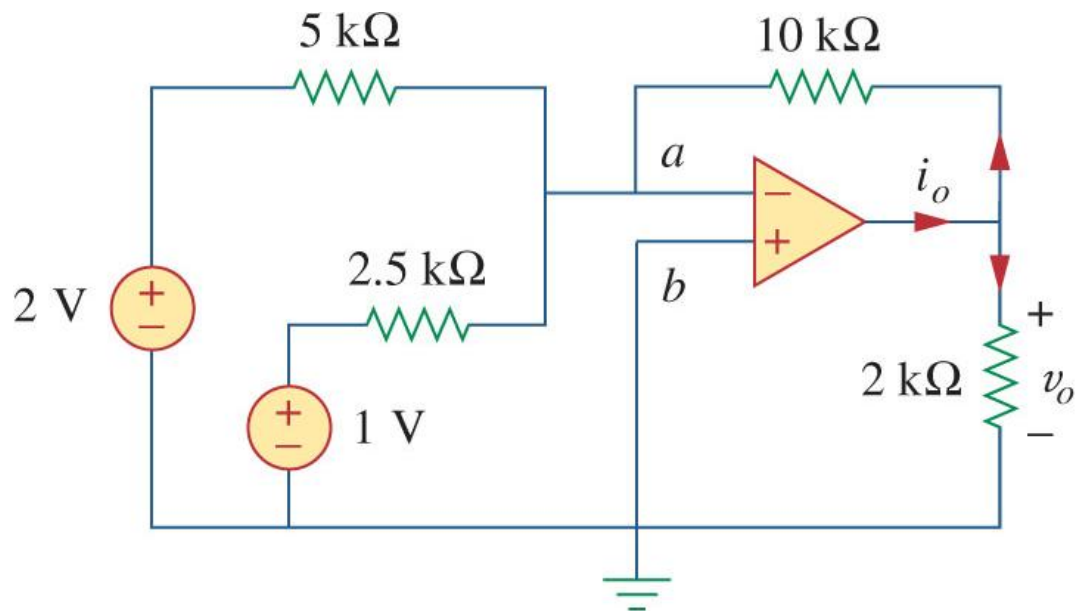- Find v_o and i_o in the circuit shown below





$$\frac{v_o}{10 \text{ K}} + \frac{2}{5 \text{ K}} + \frac{1}{2.5 \text{ K}} = 0$$

$$v_o = -8 \text{ V}$$

$$i_o = -4 - 0.8 = -4.8 \text{ mA}$$

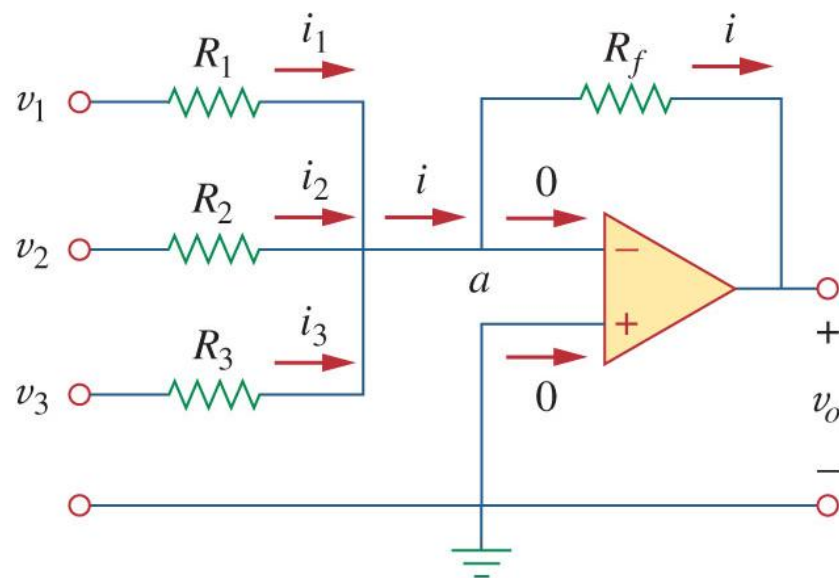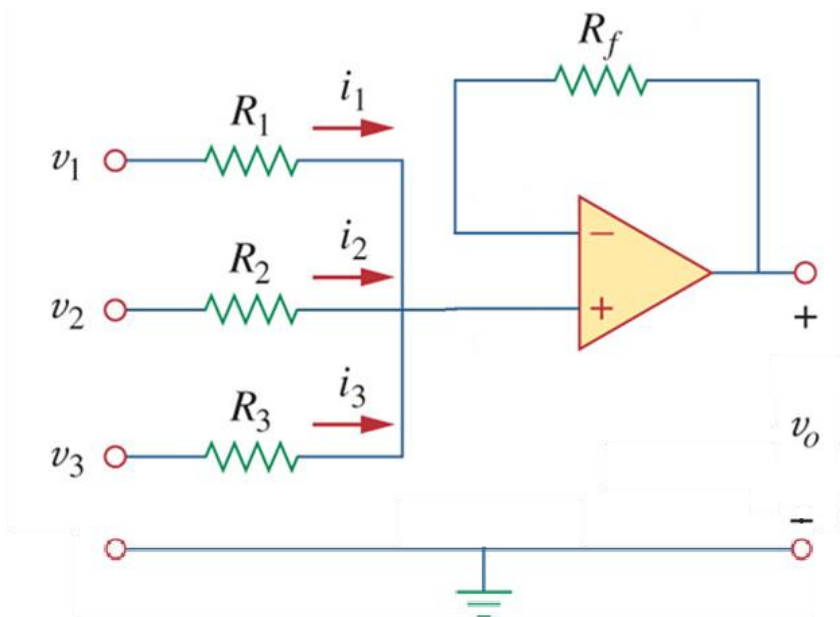Exercise: find the relationship between v_o and input voltages v_1 , v_2 , and v_3 . What is the disadvantage of such a summing amplifier compared to the one in the previous slide?





Answer:

$$V_0 = \frac{\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right) (R_1 \parallel R_2 \parallel R_3)$$

However, the current into each terminal is affected by the voltages at the other input terminals, which is not desirable and should be avoided.


Remember: for non-ideal voltage source, the output voltage varies with output current.

Ideal Op-Amp Analysis

When there exists negative feedback,

Property 1: Gain is infinite \Rightarrow The **potential** between the op-amp input terminals, $v_{(+)} - v_{(-)}$, equals **zero**.

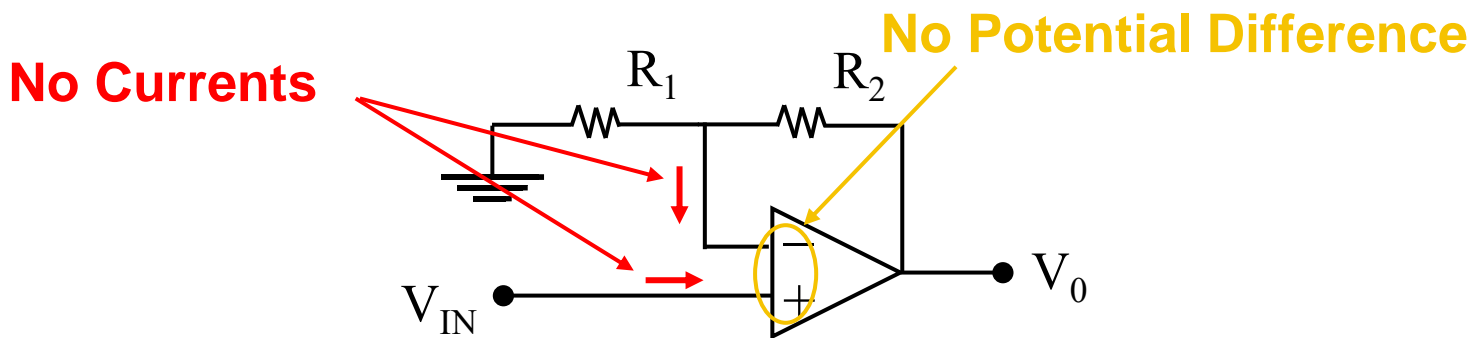
Property 2: Input resistance is infinite \Rightarrow The **currents** flowing into the op-amp's two input terminals both equal **zero**.



Property 1 reduces the number of unknown voltages by 1 which compensates the lack of KCL equation at the output node.



Difference Amplifier

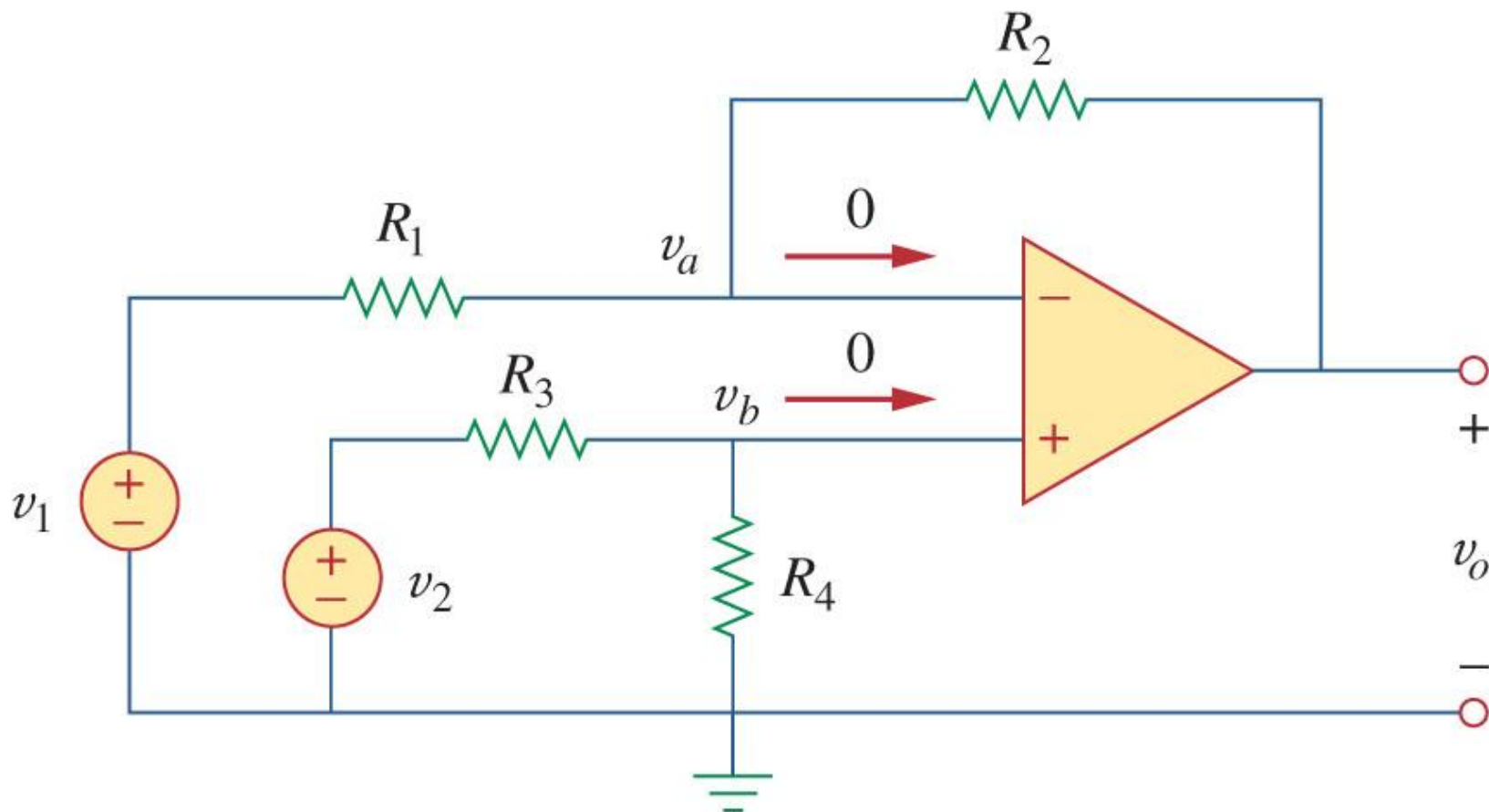



Difference Amplifier (solution)

$$V_a = V_b = V_2 \cdot \frac{R_4}{R_3 + R_4}$$

$$\frac{V_1}{R_1} - V_a \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = - \frac{V_o}{R_2}$$

$$\frac{V_1 - V_a}{R_1} = \frac{V_a - V_o}{R_2}$$


$$\frac{V_1}{R_1} - V_2 \frac{R_4}{R_3 + R_4} \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = - \frac{V_o}{R_2}$$

$$\begin{aligned} V_o &= - \frac{R_2}{R_1} V_1 + \frac{\left(\frac{R_2}{R_1} + 1 \right) V_2}{\left(\frac{R_3}{R_4} + 1 \right)} \\ &= \frac{R_2}{R_1} \left[\frac{\left(1 + \frac{R_1}{R_2} \right)}{\left(1 + \frac{R_3}{R_4} \right)} V_2 - V_1 \right] \end{aligned}$$

Note: current from voltage source 1 is affected by v_2 , but not the other way around.

Differentiator

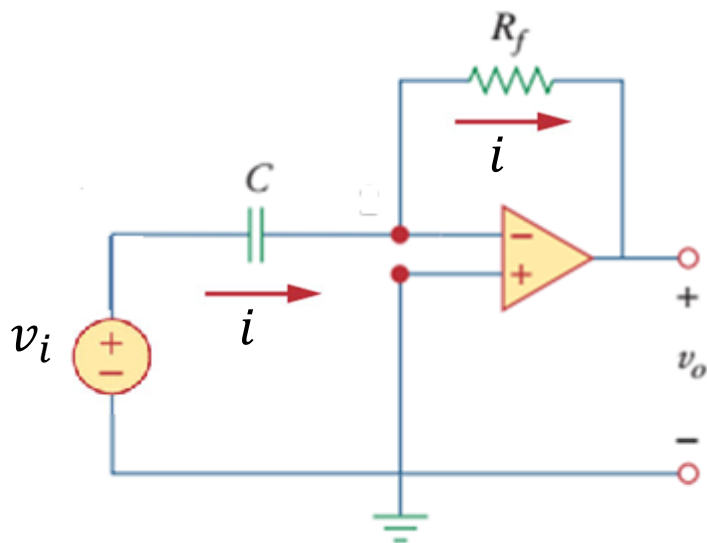Find the relationship between v_o and v_i in the circuit shown below




$$v_o = -R_f i = -R_f C \frac{dv_i}{dt}$$

For this equation to be valid, the response time of the op-amp must be much shorter than $R_f C$.

Integrator

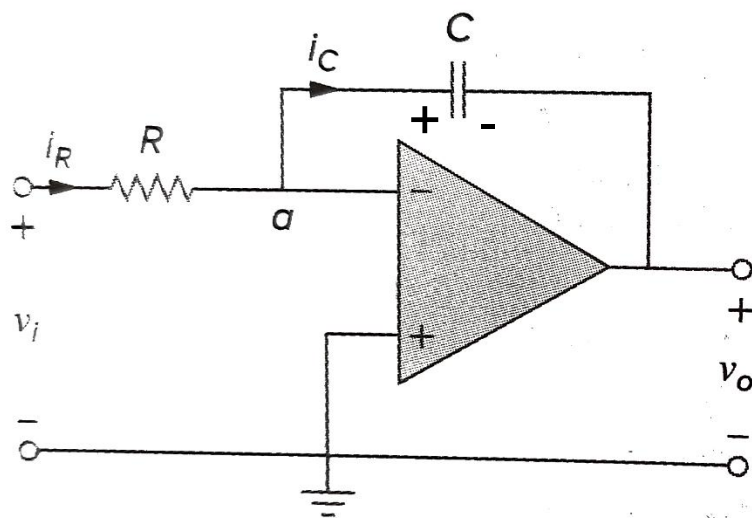Find the relationship between v_o and v_i in the circuit shown below.
What if the capacitor is replaced by a inductor?



$$\begin{aligned} v_o &= -\frac{Q}{C} = -\frac{1}{C} \int_0^t I dt + v_{0,i} \\ &= -\frac{1}{C} \int_0^t \frac{v_i}{R} dt + v_{0,i} \\ &= -\frac{1}{RC} \int_0^t v_i dt, \text{ if } v_{0,i} = 0. \end{aligned}$$


If C is replaced by an inductor,

$$v_o = -L \frac{dI}{dt} = -\frac{L}{R} \frac{dv_i}{dt}$$

Note: both RC and $\frac{L}{R}$ have the dimension of time.

Practice 3

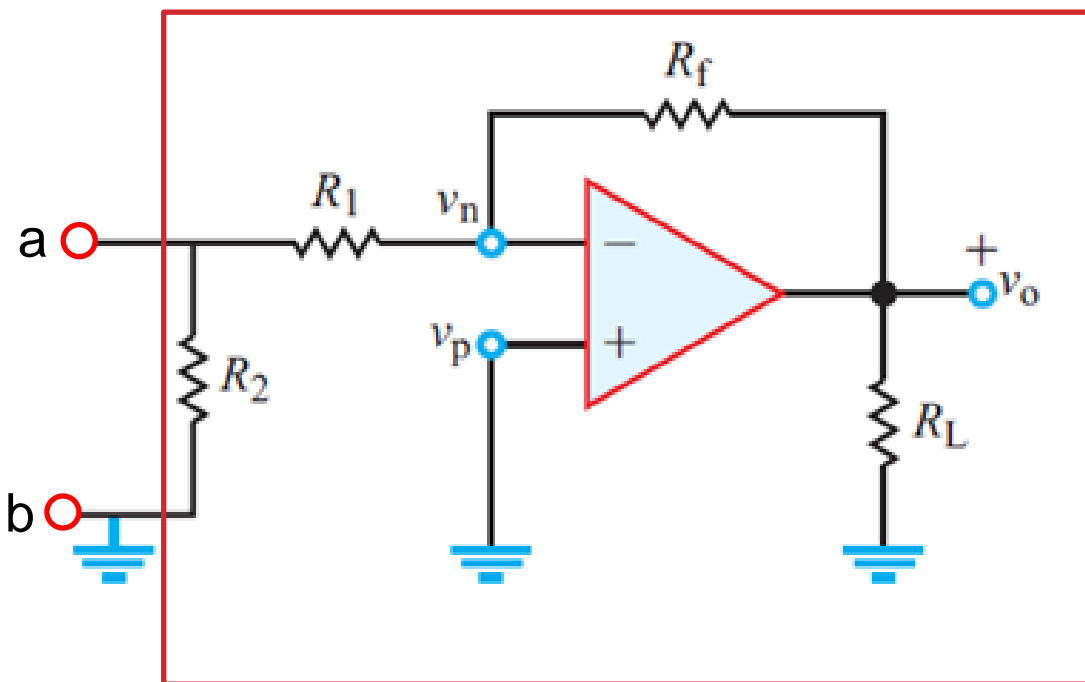Determine the equivalent resistance at terminals a-b.



Answer:


$$I = \frac{V_{ab}}{R_1} + \frac{V_{ab}}{R_2}$$

$$R_{eq} = \frac{V_{ab}}{I} = \frac{R_1 R_2}{R_1 + R_2} = R_1 || R_2$$



Practice 4

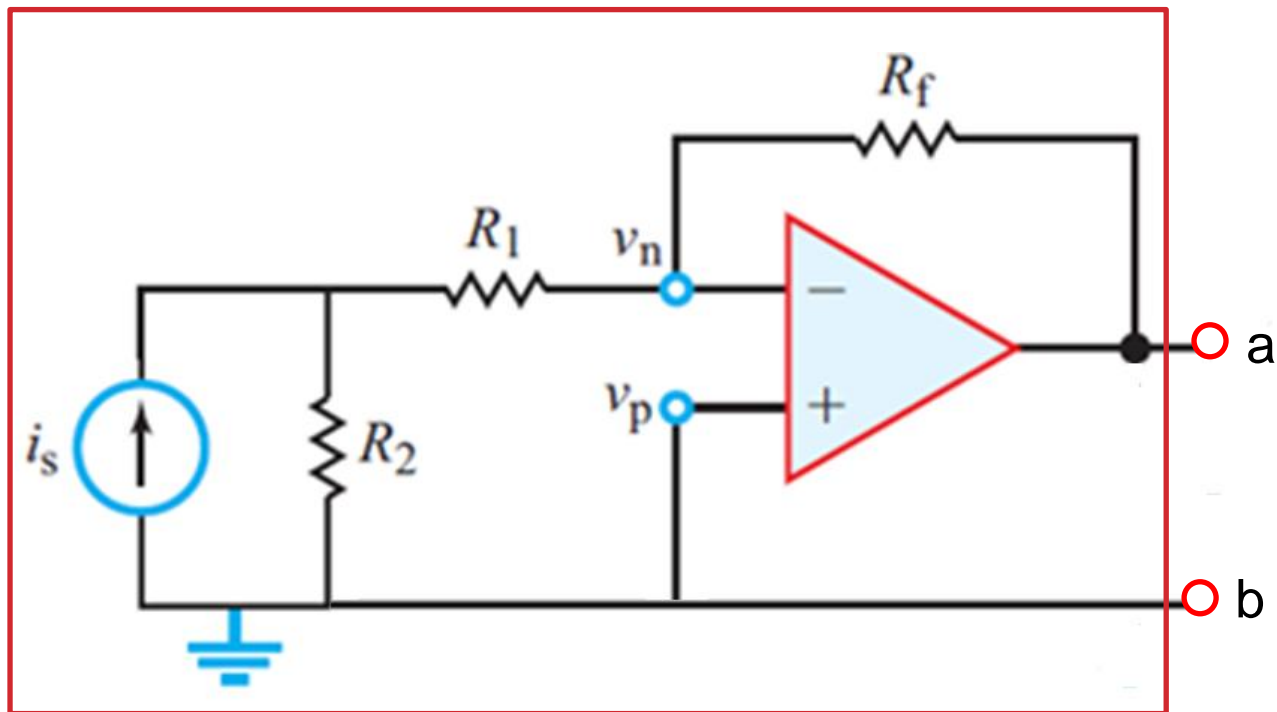
Determine the Thevenin's equivalent resistance at terminals a-b.






Practice 4 (solution)

Open circuit

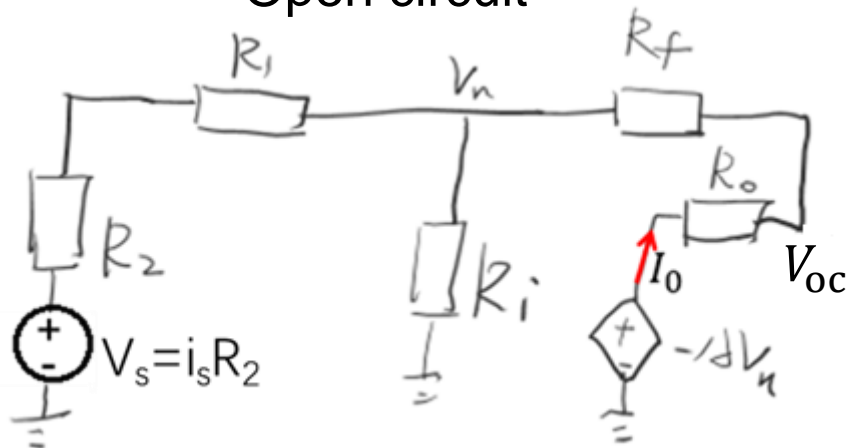

From ideal op-amp approximation,
we have $V_{oc} = \frac{-i_s R_2 R_f}{R_1 + R_2}$

Short circuit

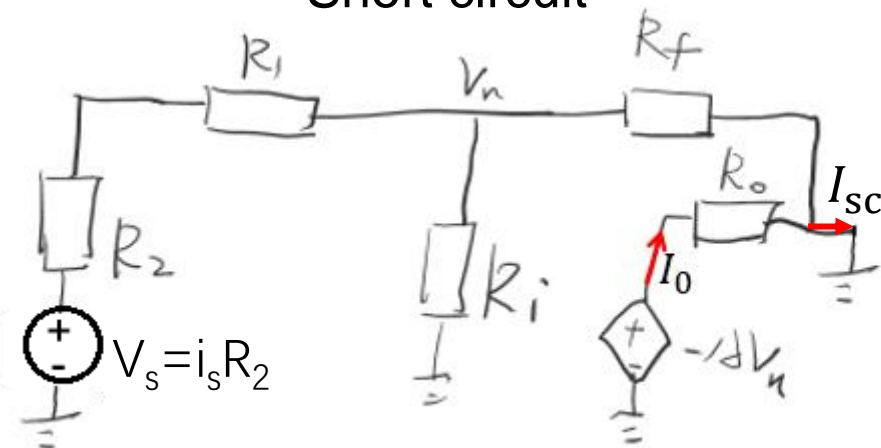


$$V_n = \frac{(i_s R_2) R_f}{R_1 + R_2 + R_f}, \quad (R_i \sim \infty)$$

$$I_{sc} = -\frac{A V_n}{R_o} + \frac{V_n}{R_f} \approx \frac{-A (i_s R_2) R_f}{R_o (R_1 + R_2 + R_f)}$$

$$R_{Th} = \frac{V_{oc}}{I_{sc}} = \frac{R_o (R_1 + R_2 + R_f)}{A (R_1 + R_2)} \sim \frac{R_o}{A}$$



Application - DAC

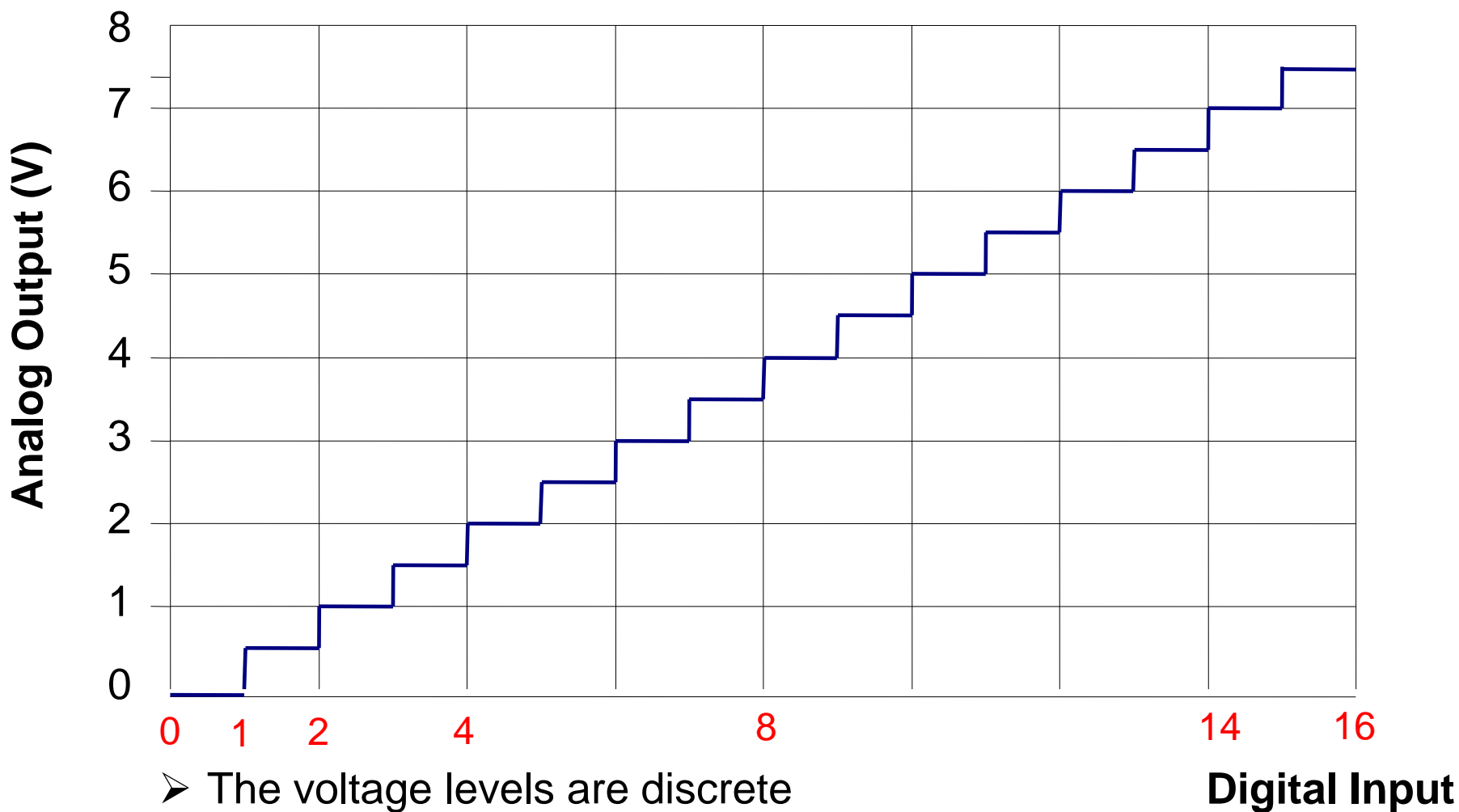



Binary representation

$$[v_n \dots \dots v_3 v_2 v_1], v_i = 0 \text{ or } 1.$$



MSB

LSB

$$\text{Digital value} = v_1 + 2v_2 + 4v_3 + \dots 2^{n-1}v_n$$



DAC

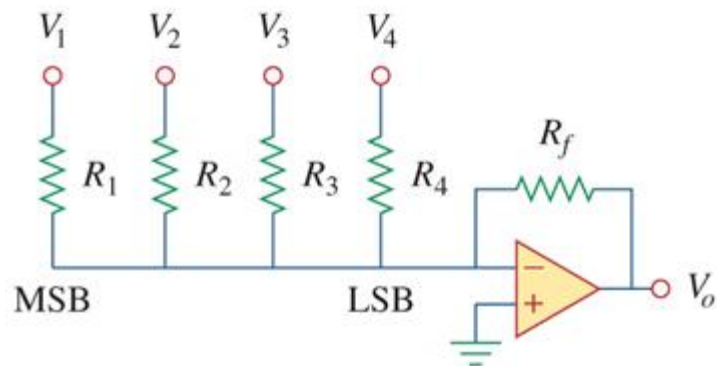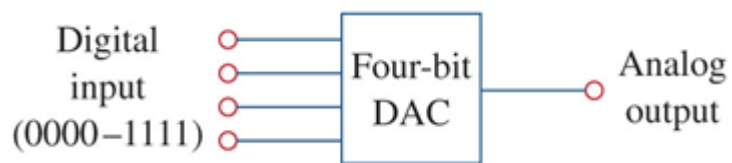


$$-V_o = \frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 + \frac{R_f}{R_4} V_4 = \frac{R_f}{R_1} \left(V_1 + \frac{R_1}{R_2} V_2 + \frac{R_1}{R_3} V_3 + \frac{R_1}{R_4} V_4 \right)$$

$$\text{If } \frac{R_1}{R_2} = 2, \quad \frac{R_1}{R_3} = 4, \quad \frac{R_1}{R_4} = 8, \quad \text{then } V_o = -\frac{R_f}{R_1} \underbrace{(V_1 + 2V_2 + 4V_3 + 8V_4)}_{\text{二进制数字的值}}$$



DAC

“Weighted-adder D/A converter”

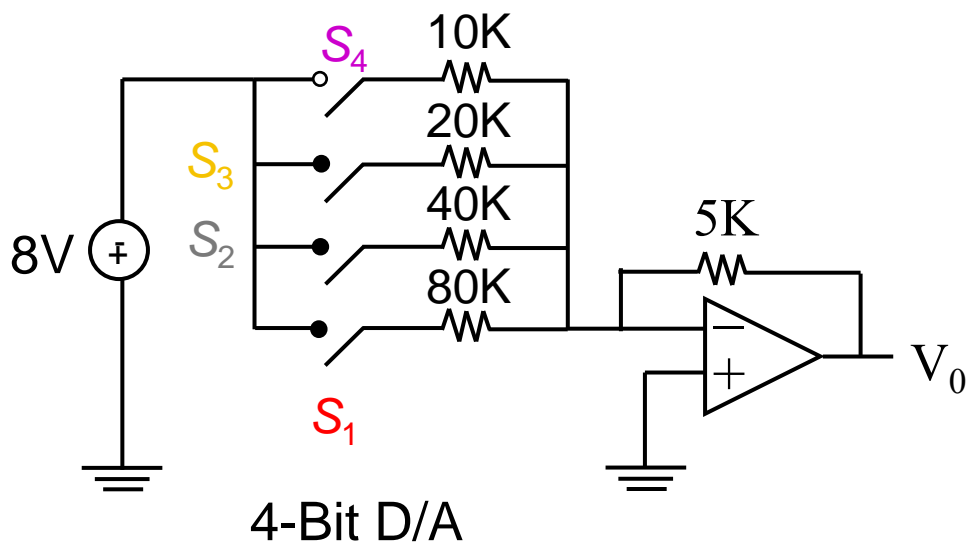

(Transistors are used
as electronic switches)

$$V_i = -8S_i$$

$$V_o = -\frac{R_f}{R_1} (V_1 + 2V_2 + 4V_3 + 8V_4) = 0.5(S_1 + 2S_2 + 4S_3 + 8S_4)$$



Instrumentation Amplifier

1. The amplification factor controllable and not too large to allow a sufficient dynamic range. → multiple resistance options.
2. The input signal often has an unknown offset → differential amplifier.
3. The Thevenin resistance of the input signal is not negligible. → two stage design.

Instrumentation Amplifier

Ad8231

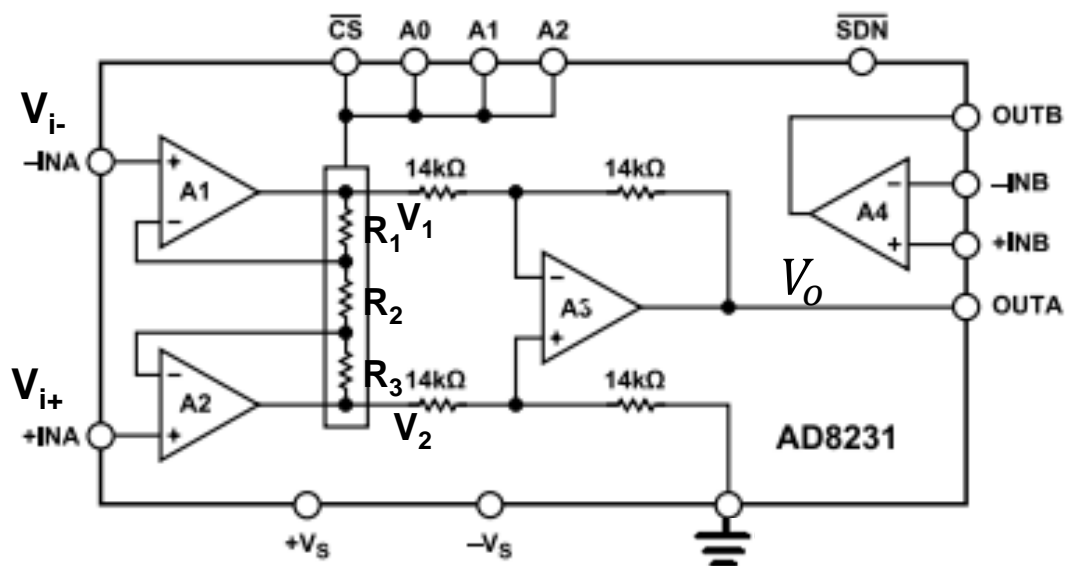


Table 7. Truth Table for AD8231 Gain Settings

CS	A2	A1	A0	Gain
Low	Low	Low	Low	1
Low	Low	Low	High	2
Low	Low	High	Low	4
Low	Low	High	High	8
Low	High	Low	Low	16
Low	High	Low	High	32
Low	High	High	Low	64
Low	High	High	High	128
High	X	X	X	No change

The circuit can be separated into 2 stages


$$\text{Stage 1: } (V_{i+} - V_{i-}) = (V_2 - V_1) \frac{R_2}{R_1 + R_2 + R_3}$$

$$\text{Stage 2: } V_o = (V_2 - V_1)$$



Instrumentation Amplifier (practice 5)

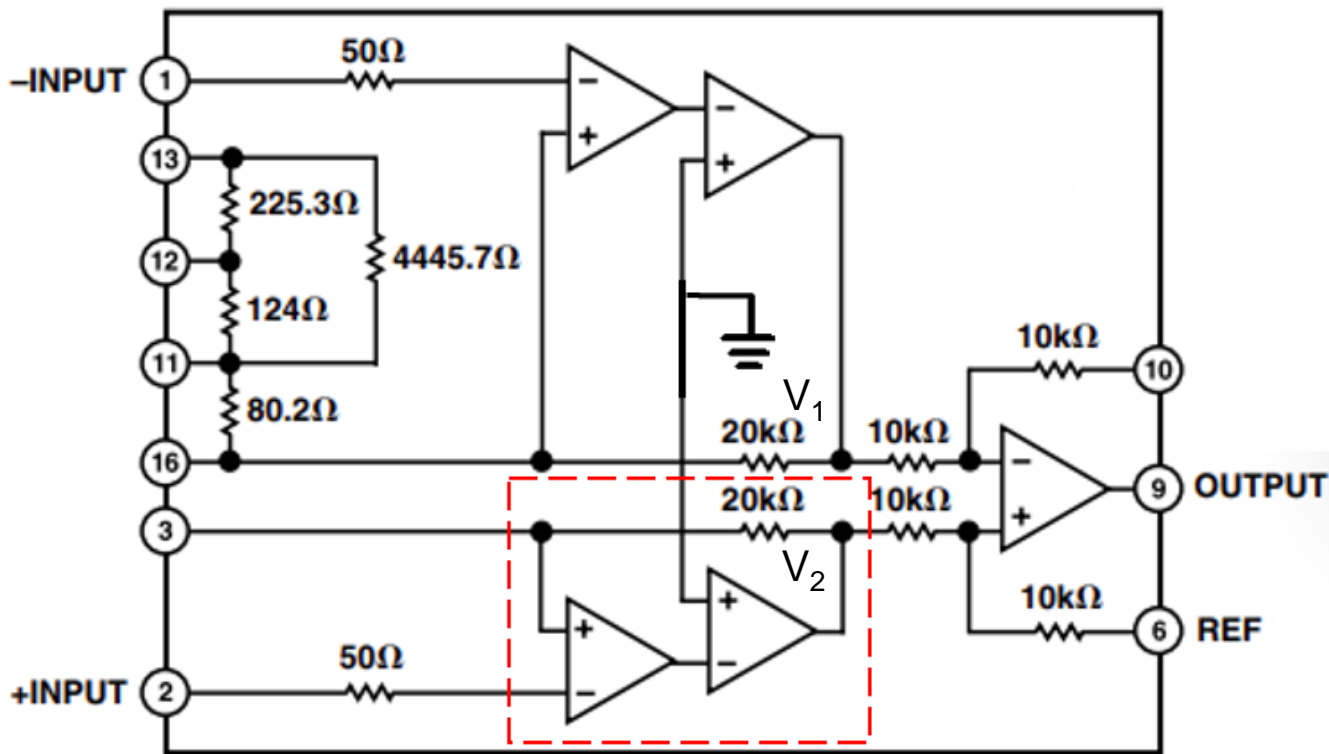下图为某仪表放大器的内部电路图，如果将端口12与3相连，端口9与10相连，端口6接地。求 OUTPUT(端口9)的电压与“+input”(端口2)-“-input”(端口1)间电压差的关系。





practice 5 solution

$$V_{\text{output}} = V_2 - V_1$$

$$\begin{aligned} & V_{+\text{input}} - V_{-\text{input}} \\ &= (V_2 - V_1) \frac{R_{3,16}}{40000 + R_{3,16}} \end{aligned}$$

$$V_{\text{output}} = (V_{+\text{input}} - V_{-\text{input}}) \left(1 + \frac{40000}{R_{3,16}} \right)$$

$$R_{3,16} = 80.2 + \frac{124 \cdot (225.3 + 4445.7)}{124 + 225.3 + 4445.7} = 200.99$$

$$V_{\text{output}} = 200(V_{+\text{input}} - V_{-\text{input}})$$